

MEHAR ALI KHAN

17PWELE5074

SECTION A

ELECTRICAL ENGINEERING

DEPARTMENT

5TH SEMESTER

POWER ELECTRONICS

LAB REPORT

SIR FAHEEM ALI

EXPERIMENT NO 1:

TITLE:

INTRODUCTION TO POWER ELECTRONICS

POWER ELECTRONICS:

Power electronic deals with the conversion of power from one form to another. Typical application of power electronics include conversion of ac to dc (Rectification), conversion of dc to ac (Inversion) and conversion of an ac power from one frequency & amplitude to another (cyclo-conversion). It is use to control speed of induction motor.

MAIN OBJECTIVE OF POWER ELECTRONICS:-

The purpose of power electronic circuit is to match load (V & I) to that of the source. Power Electronic circuit convert one level of voltage or current waveform to another and hence are called converters.

POWER ELECTRONICS CONTROL UNIT

PE 481:

It is use in power electronics lab. We implement ~~our~~ power electronics circuit on control unit. It has two positions for inserting other circuits

- 1) Power module position
- 2) Control module position

It consist of three ammeters and two voltmeters. We can take constant DC power supply as well as variable. We can also take ac power supply from control unit. The maximum dc output which we can take from this unit is 30V and 1A.

Basically control unit provides platform for the implementation of ckt.

POWER ELECTRONIC LCR LOAD

UNIT PE 481:

Load unit consist of passive elements i-e variable resistor, variable inductor and Electrolytic capacitor. We change the value of ^{up}

resistance and inductance by knob.

SINGLE THYRISTOR CIRCUITS

PE 481A:

This circuit consist of full wave bridge rectifier, sensitive gate thyristor. We insert this circuit in power module position of control unit.

BASIC TRIGGER CIRCUITS PE 4810:

It is a triggering circuit consist of DIAC characteristic circuit. We insert this circuit in control module position of control unit. It is use to control other electronic circuits.

EXPERIMENT NO 2:

TITLE: DC Test of SCR
To study switching of an SCR (DC test).

APPARATUS:

Power Electronics LCR LOAD UNIT PE-481
Single Thyristor circuits PE 481A
Voltmeter +
Ammeter +
Connecting wires +


THEORY:

Thyristor is an electronic switch use in power electronic devices for switching purpose. It is a three terminal device and has three types.

- a) Silicon Control Rectifier (SCR)
- b) Gate turn-off rectifier (GTO)
- c) MOS-controlled rectifier (MCT)

Thyristor carry large currents. It has high breakdown voltage. It is use for high power applications. It is not suitable for high frequency because reverse recovery current flows in it for time t_{rr} .

CIRCUIT DIAGRAM

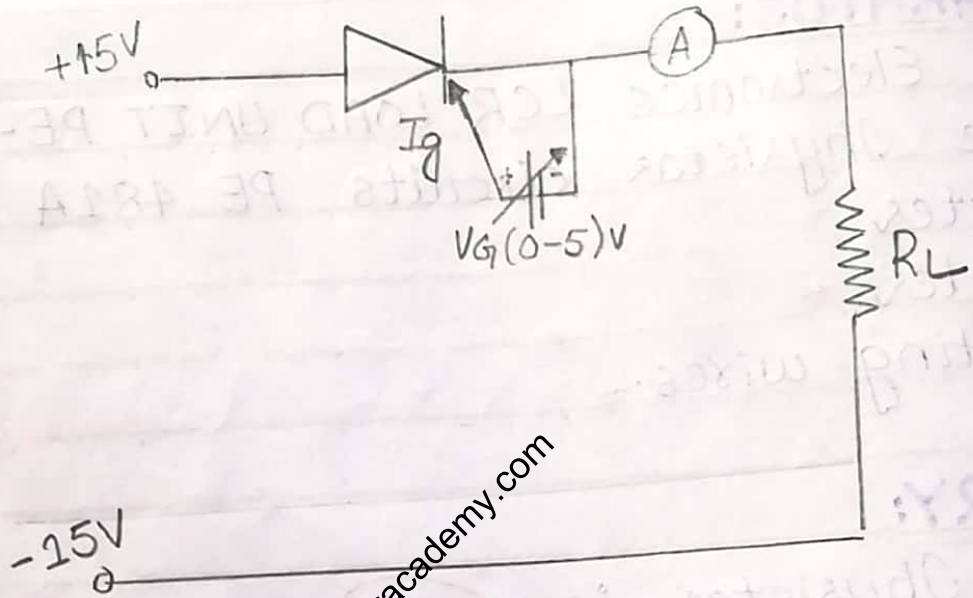

SCR is a type of thyristor, use for switching purpose in power electronic devices.

For SCR to begin to conduct, it must have a gate current applied while it has positive anode to cathode voltage. After conduction is established the gate signal is no longer required to maintain anode current. The SCR will continue to conduct as long as anode current is positive and above a minimum value called the holding level.

SCR can be only turn-on by providing the gate current.

PROCEDURE:

To implement the circuit I use Power electronic control unit, single thyristor circuits, Power Electronics LCR load unit, ammeter, voltmeter and connecting wires. I insert single thyristor circuit in PE control unit.

Then I implement the circuit according to the circuit diagram.

OBSERVATION:

S.No	I_g (mA)	V_g (V)	I_L (A)
1	0.02A	0.634V	2.55A
2	0.02	0.634V	1.3A
3	0.02	0.634V	1.2A

PROCEDURE:

Implement the circuit & use electronic control unit, single phase thyristor, power electronics SCR load unit, ammeter, voltmeter, connecting wires & insert thyristor circuit in PE control unit. Implement the circuit.

I then I connected voltmeter and ammeter to measure gate current and gate voltage.

PRECAUTIONS:-

- 1) Connection must be tight.
- 2) Properly insert the thyristor ckt in control unit.
- 3) Take readings accurately.

CONCLUSION:

I concluded that how we use SCR for switching purpose. To turn ON SCR, two conditions must be fulfilled

- 1) Anode should be positive with respect to cathode.
- 2) Short duration gate current.
Once the SCR is turned ON and we remove gate current it will be still turned ON.

EXPERIMENT NO 3:

5074

TO STUDY SWITCHING OF AN SCR (AC TEST)

95

APPARATUS:

- Power Electronics Control Unit PE 482
- Power Electronics LCR Load unit PE 481
- Single thyristor circuits PE 481A

SCR Characteristics

THEORY:

Thyristor is an electronic switch used in power electronics. It is a three terminal device and has three types

- 1 Silicon Control Rectifier (SCR)
- 2 Gate turn-off transistor (GTO)
- 3 MOS-controlled rectifier (MCR)

Thyristor carry large currents. It has high breakdown voltage. It is use for high power applications. It is not suitable for high frequency because reverse recovery current flows in it for time t_{rr} .

SCR is a type of transistor use for switching purpose in power electronic devices.

For SCR to begin to conduct, it must have a gate current applied

while it has positive anode to cathode voltage. After conduction is established the gate signal is no longer required to maintain anode current. The SCR will continue to conduct as long as anode current is positive and above a minimum level called the holding level.


SCR can be only turn-ON by providing gate current.

NOTE:- For SCR to conduct the above mentioned two conditions must be fulfilled. In case of DC test when we apply +ve voltage (i.e. anode is positive w.r.t cathode) and provide a gate signal the SCR start conduction. If we remove the gate signal the SCR continue to conduct.

In case of AC test when we apply AC voltage to the ckt and gate signal is constantly provided to SCR, so we get half wave rectified ~~to~~ at output (across R_L). This is because for the positive half cycle of the AC voltage anode is +ve w.r.t cathode & gate pulse is also provided. The SCR will act as short ckt and we get waveform

CIRCUIT DIAGRAM

SILICON CONTROL RECTIFIER (SCR)

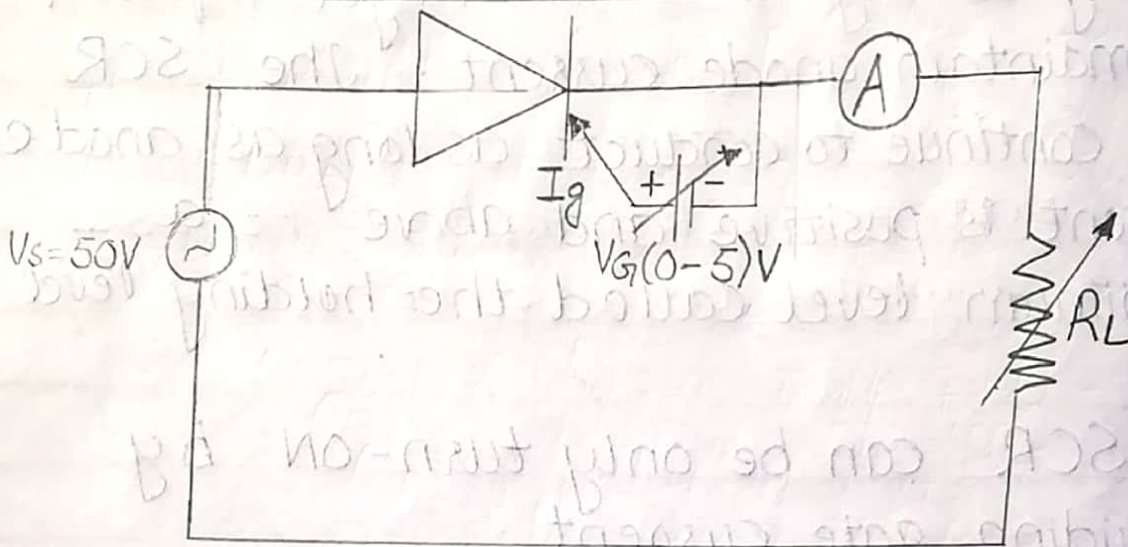

similar to that of input waveform across R_L . ($V_s = V_L$).

For the negative half cycle the first condition does not fulfilled and SCR will be reverse biased. Although gate pulse is provided, the SCR will act as an open switch and we get nothing at the output.

If gate pulse is constantly provided in case of AC test we get half wave rectified output across R_L . If we remove gate pulse we get 0 volts across R_L (as SCR will act as an open switch).

PROCEDURE:

To implement the circuit I use power electronics control unit, single thyristor ckt, power electronics LCR load unit and connecting wires. I insert single thyristor circuit in power electronic control unit then I implement the circuit according to the circuit diagram.


PRECAUTIONS:

- 1) Connections must be tight.
- 2) Properly insert the thyristor circuit in control unit.
- 3) Take readings accurately.

CONCLUSION:

I concluded from this experiment that in case of AC test if we remove the gate pulse the SCR will act as an open switch and we get 0 volt across RL. And if gate pulse is constantly provided we get half wave rectified output across RL.

In case of DC test once the SCR is turn ON and we remove gate current it will be still turn ON.



EXPERIMENT NO 4:

5074

To study single phase control of an SCR (Resistive load)

APPARATUS:





- Power Electronic control unit PE 481.
- Power Electronic LCR load unit PE 481.
- Single thyristor circuits PE 481A.
- Basic trigger circuits PE 4810.

THEORY:

We have two types of rectifiers. Uncontrolled Half Wave Rectifier and Controlled Half Wave Rectifier. When we use diode in half wave rectifier so it is uncontrolled half wave rectifier. Its average value is given by

$$V_o = \frac{V_p}{\pi}$$

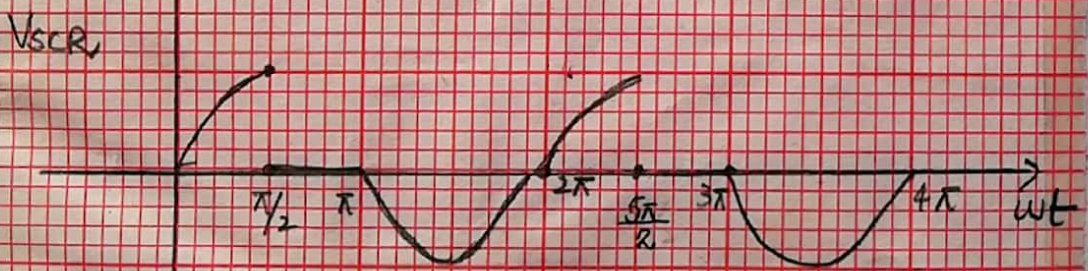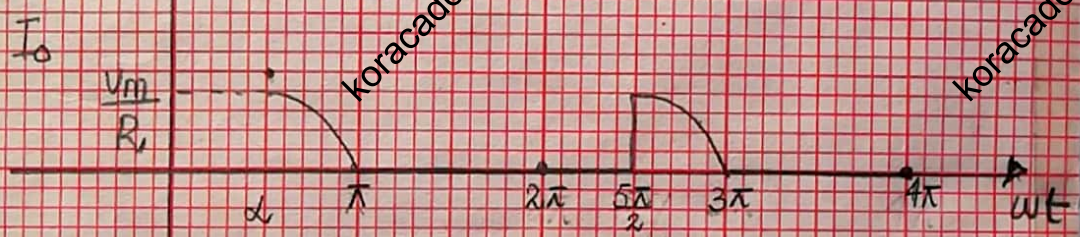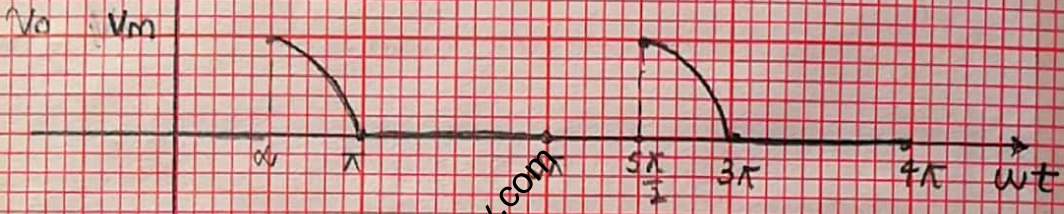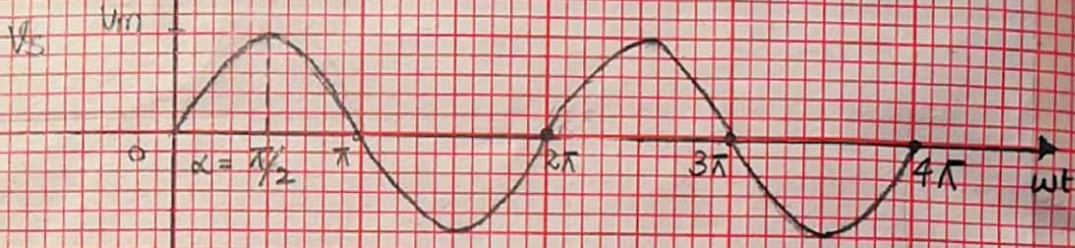A way to control output of a half wave rectifier is to use an SCR instead of a diode. Fig shows a basic controlled half wave rectifier with a resistive load. Two conditions must be met before the SCR can conduct.



HALF-WAVE CONTROLLED RECTIFIER
 VOLTAGE WAVEFORMS

1. The SCR must be forward biased
2. A current must be applied at the gate of SCR.

The average value across the load resistor is

$$V_o = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

In uncontrolled H.W rectifier once the source and load parameters are established, the average value across load is a fixed quantity. But in case of controlled half wave rectifier if we change firing angle (α) so the average or dc voltage across load resistor will change.

PROCEDURE:-

To implement the controlled half wave rectifier circuit I insert Basic trigger circuit in control module position of the Power Electronic control unit. I insert the Basic Thyristor circuit in power module position. I only

OBSERVATION TABLE

S No	α degree	V_o (V)	V_{rms} (V)	I_o (A)	I_{rms} (A)	V_o (V) Actual	% Error
01	32°	20V	33.4V	0.4A	0.66A	19.7	1.5%
02	42.4°	18V	32V	0.36A	0.64A	16.9	6.5%
03	62.4°	16V	32.1V	0.32A	0.64A	16.7	4.19%

Calculation $V_o = \frac{V_m}{2\pi} (1 + \cos \alpha) \dots \text{--- (1)}$

From oscilloscope: $2 \text{ c/s} = 360^\circ \Rightarrow 1 \text{ c/s} = 180^\circ$

$V_m = 34 \times 2 = 68 \text{ V}$

$\alpha + \pi = 18.5 \Rightarrow \alpha = 18.5 - 14.5$

$\Rightarrow \alpha = 3.5 \times 12.41 \Rightarrow \alpha = 43.4^\circ$

Put α in (1) $\Rightarrow V_o = 16.9 \text{ Volts}$

% Error = $\frac{V_o(m) - V_o(T)}{V_o(T)} \times 100 = 0.3\%$

Calculations:

S No	α degrees	V_{rms} (V)	I_o (A)	I_{rms} (A)	V_o (V) Calculated	V_o (V) Actual	Error
1	32°	33.4V	0.4A	0.66A	20V	19.7V	1.5%
2	47.4°	32V	0.36A	0.64A	18V	16.9V	6.5%
3	63.4°	32.1V	0.32A	0.64A	16V	16.7V	4.19%

connect the ammeter and load to the Basic thyristor circuit.

I calculate V_m and α from the oscilloscope and then I calculate the RMS value of voltage, Average value of voltage.

PRECAUTIONS:

- 1) Insert basic trigger circuit and basic thyristor ckt properly.
- 2) Note α carefully from the oscilloscope.

CONCLUSION:

I concluded from this experiment that once the source and load parameters are established we can change the average or dc voltage across load resistor by changing the firing angle (α).

LAB NO 5:

99/100

To study single phase half wave controlled rectifier (inductive load and without commutating diode).


APPARATUS:

Power Electronics Control unit PE 481.
 Power Electronic LCR Load unit PE 481
 Single thyristor circuits PE 481A
 Basic trigger circuits PE 4810.

THEORY:

In previous experiment we study single phase half wave controlled rectifier (resistive load) and in this experiment the same rectifier with the inductive load). ^{we take} If $\alpha = 0$ so both the rectifiers i.e. having resistive load and inductive load behaves similarly from 0 to π rad. Beyond π rad the rectifier with resistive load blocks the current resulting in zero voltage drop across R_L . But in case of inductive load from π to β there will be V_o . The reason is that in this region the inductor forward biases the diode. So the current will be beyond π i.e. upto β .

CIRCUIT DIAGRAM:-

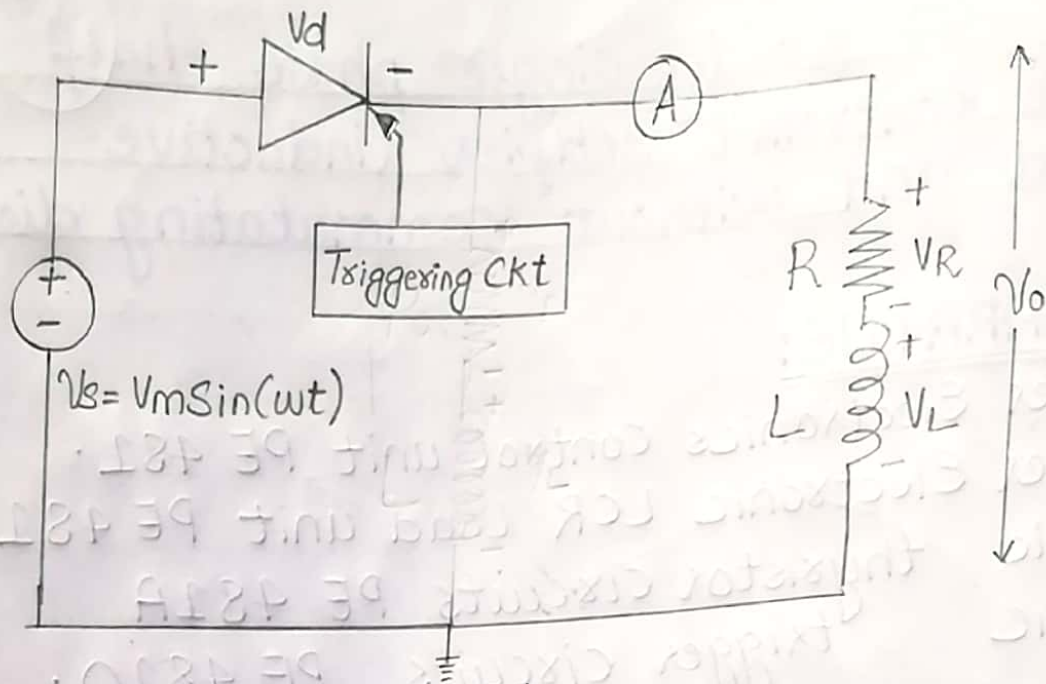

OBSERVATION AND CALCULATION:-

Sr No	α	β	V_{rms}	V_o C (V)	V_o actual	I_o Cal	I_o Actual	Error % I	Error % V
1	24°	222°	35.4°	17.67	0.35	0.41	18.3	11%	3.8%
2	54°	264.5	34.6	10.6	0.212	0.28	11.5	16%	7.8%
3	80.4°	264	33.8	3.2	0.64	0.091	3.46	21%	6.6%

The purpose of SCR is to control the average value of rectifier voltage.

$$V_o = \frac{V_m}{2\pi} (\cos\alpha - \cos\beta)$$

The positive value of ωt that result in zero current is called extinction angle β . α (alpha) is called the firing angle. The angle $\beta - \alpha$ is called the conduction angle γ .

$$i(\omega t) = \begin{cases} \frac{V_m}{Z} (\sin(\omega t - \theta) - \sin(\alpha - \theta) e^{-(\alpha - \omega t)/\omega\tau}) & \alpha \leq \omega t \leq \beta \\ 0 & \text{otherwise} \end{cases}$$

$i(\beta) = 0$

PROCEDURE:

To implement the controlled half wave rectifier circuit & insert basic trigger circuit in control module position of the power electronic control unit. & insert the basic thyristor circuit in power module position & only connect the ammeter and load to basic thyristor circuit.

I calculate V_m and α from the oscilloscope and then I calculate RMS value of voltage, average value of voltage.







PRECAUTIONS:


Note the readings carefully.
Insert basic trigger ckt and basic thyristor ckt properly.
Note α carefully from oscilloscope.

CONCLUSION:




We can change the average or dc voltage across load resistor by changing the firing angle α .

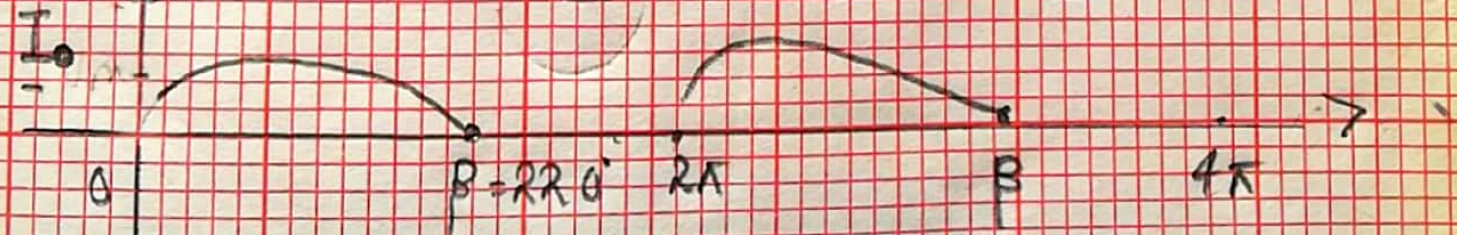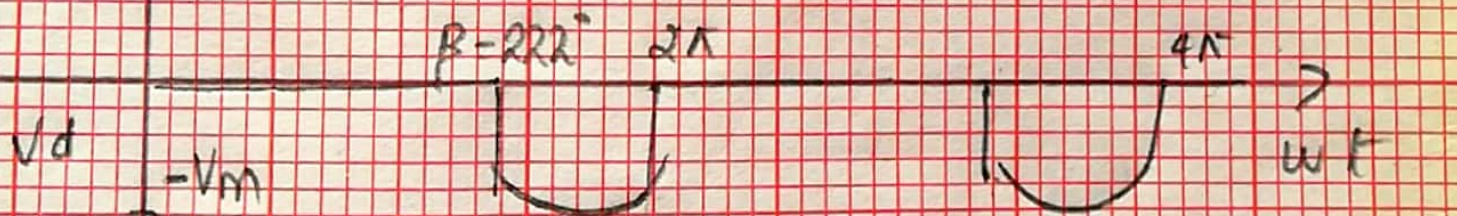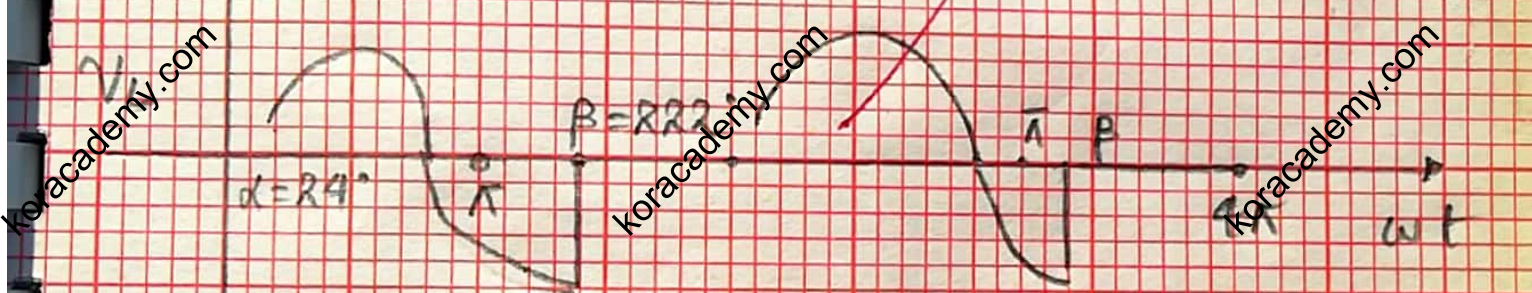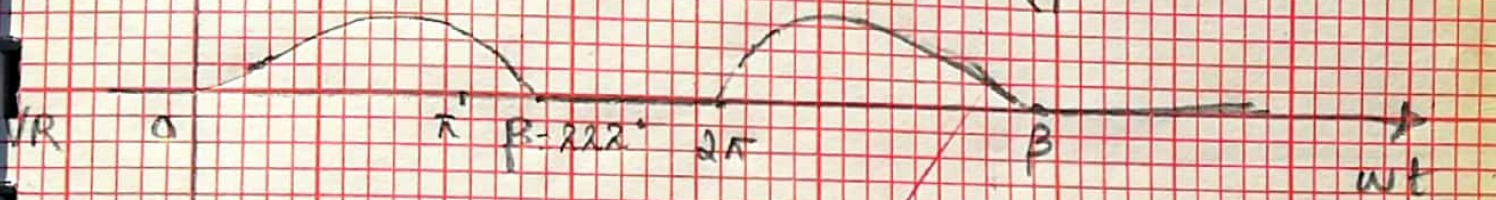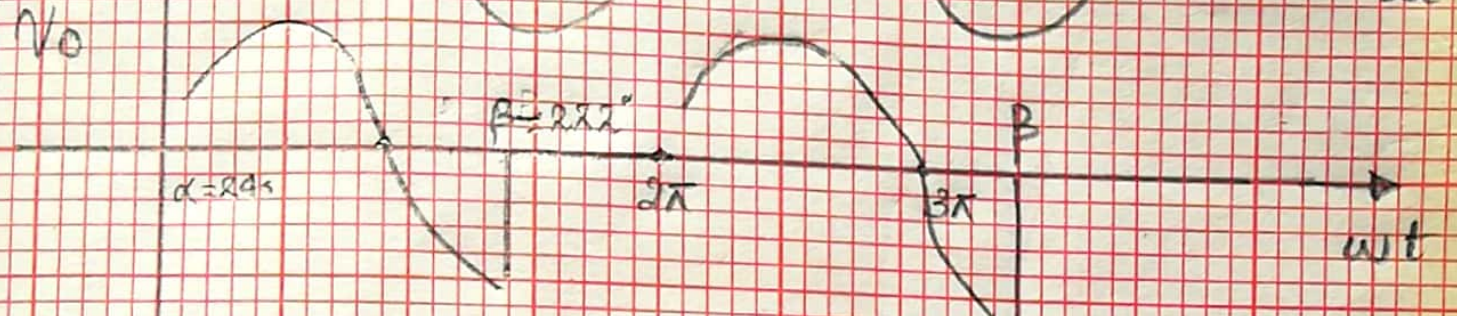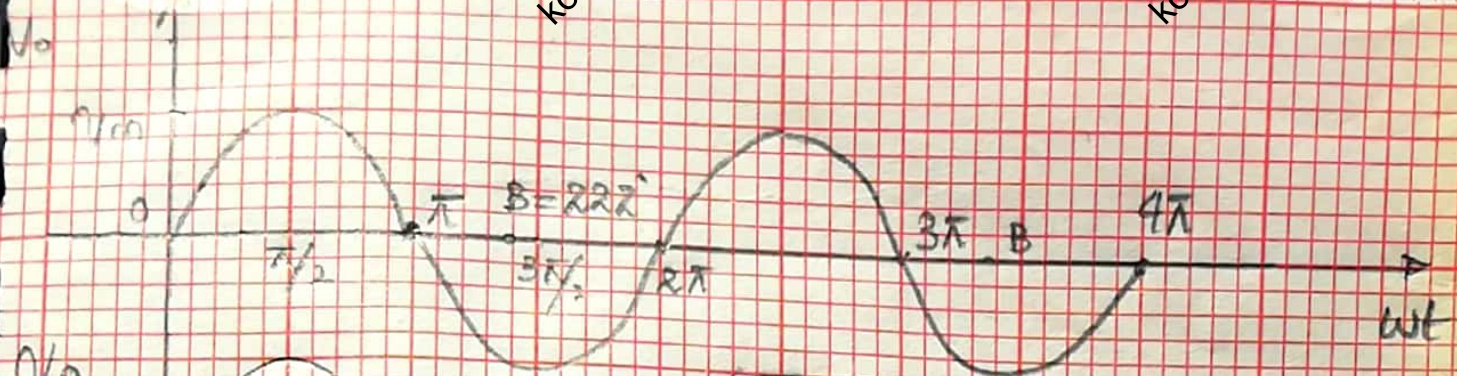In case of inductive load there will be current from α to β .
 α to π because of voltage source as it forward biases the diode and from π to β because of inductor as inductor forward biases diode in this period.






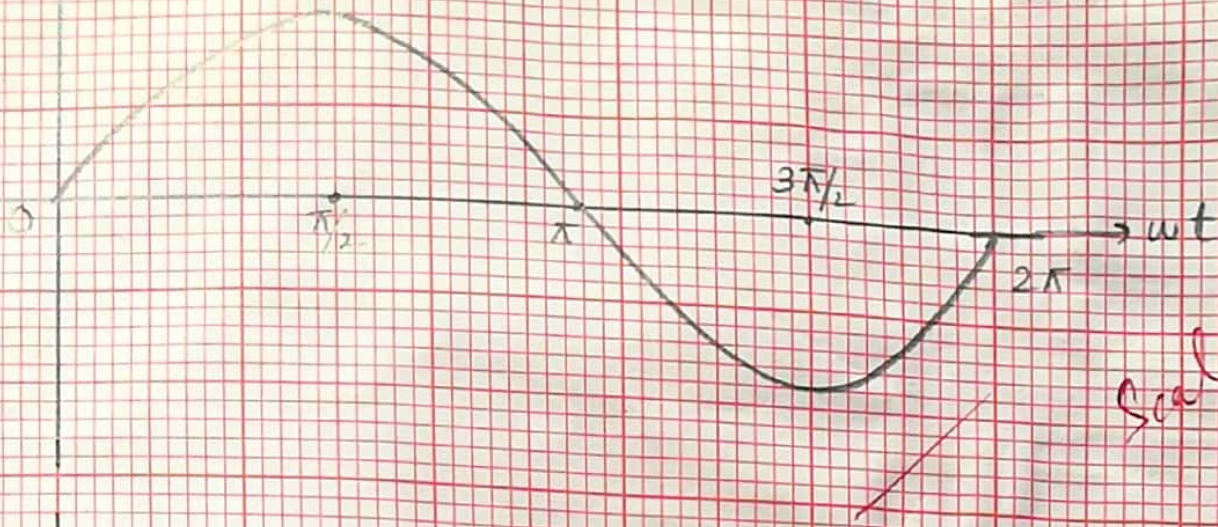

Scale

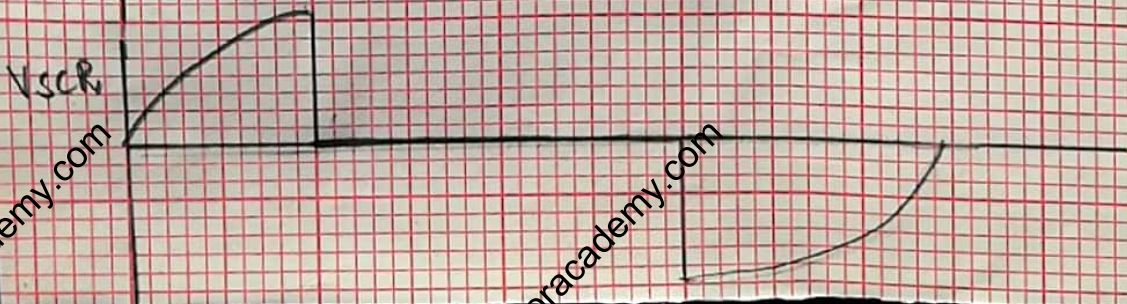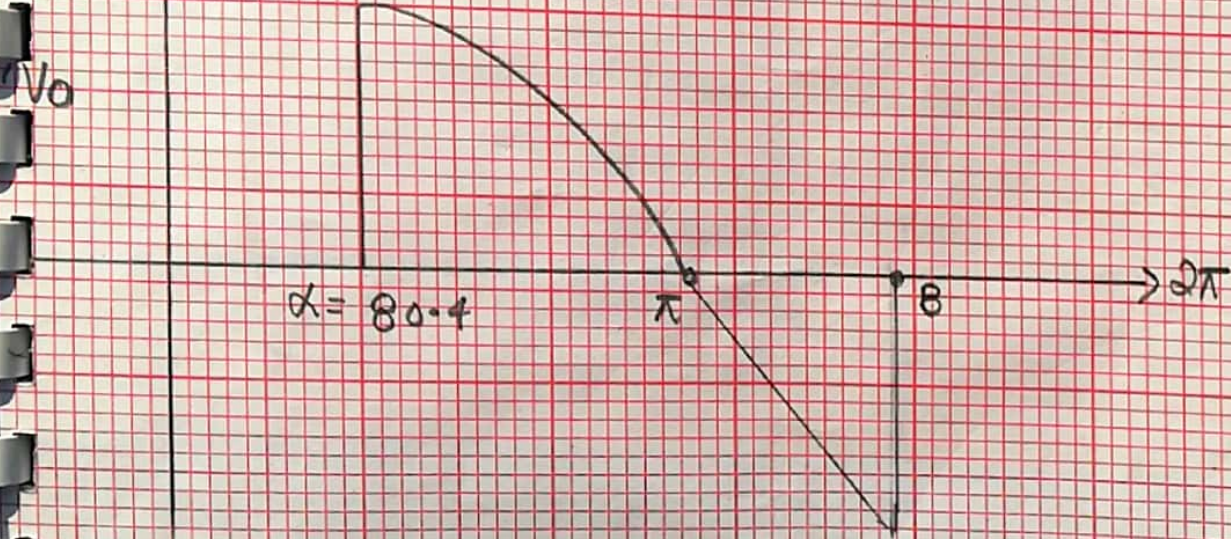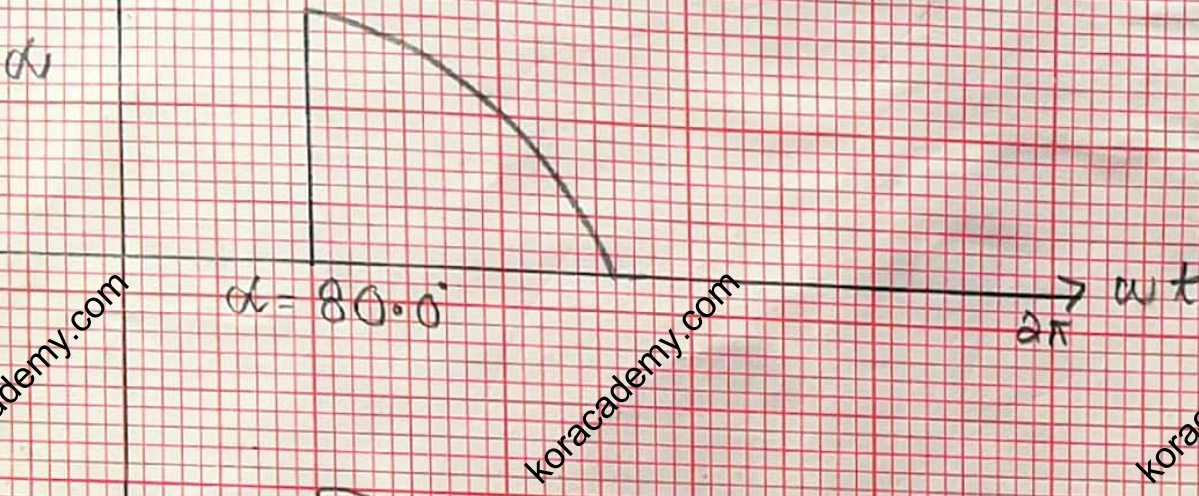

Graph : 1

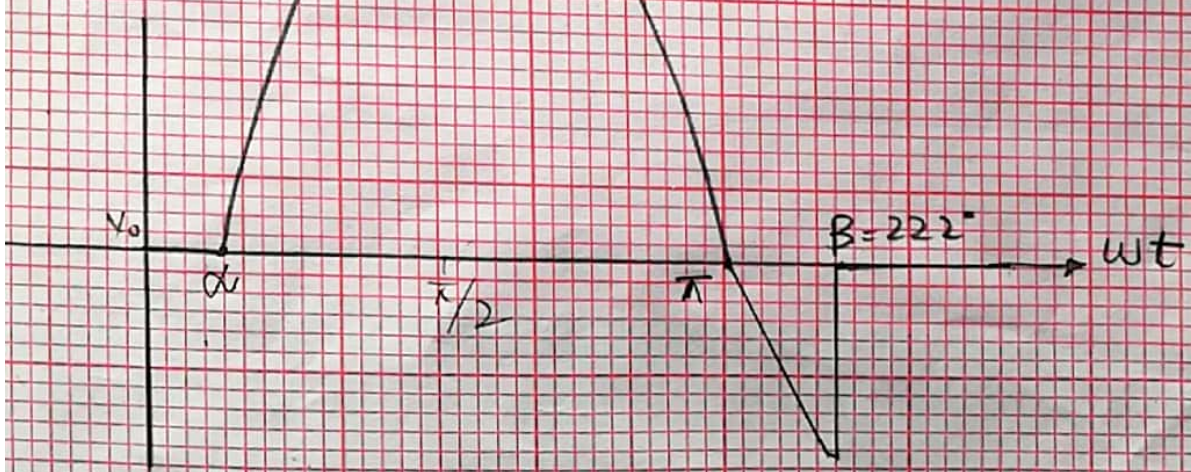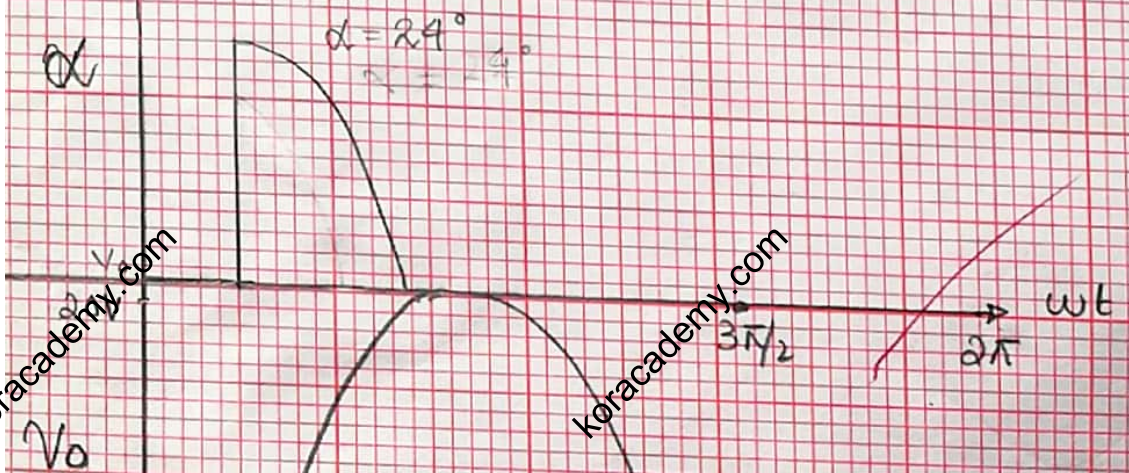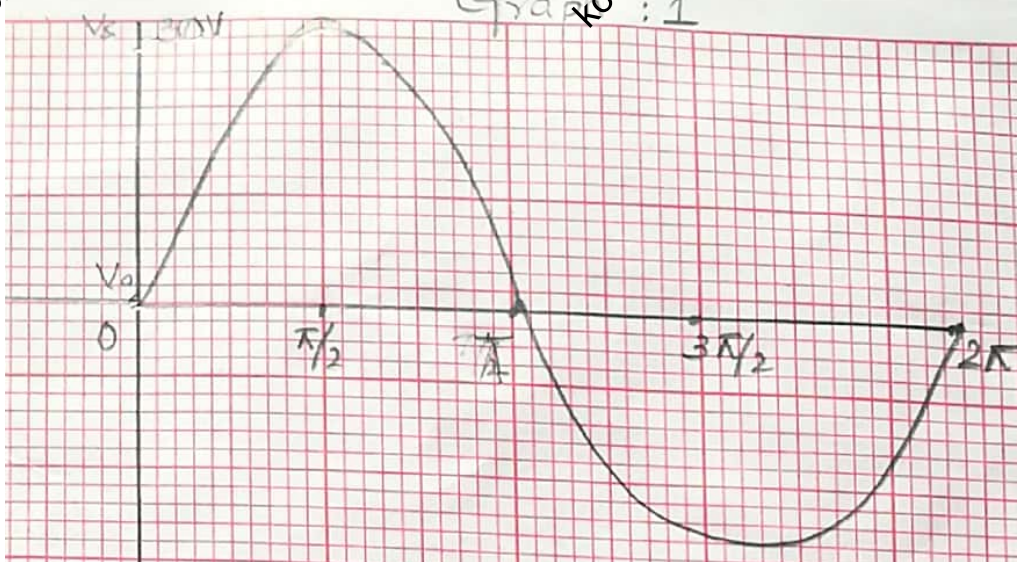

5074

LAB NO 6:

99/106

To study single phase half wave controlled rectifier (inductive load and with commutating diode)

APPARATUS:

Power electronics controlled unit PE 481

LCR load unit PE 481

Single thyristor circuit

Basic triggering circuit

connecting wire



Oscilloscope.

THEORY:


The average value ^(V_0) reduce reduces due to the inductive load. To tackle this problem a diode D_2 is connected an RL load as shown. First it is observed that both diodes cannot be forward biased at the same time.

Diode D_1 will be on when the source is positive and Diode D_2 will be on when the source is negative

CIRCUIT DIAGRAM:-

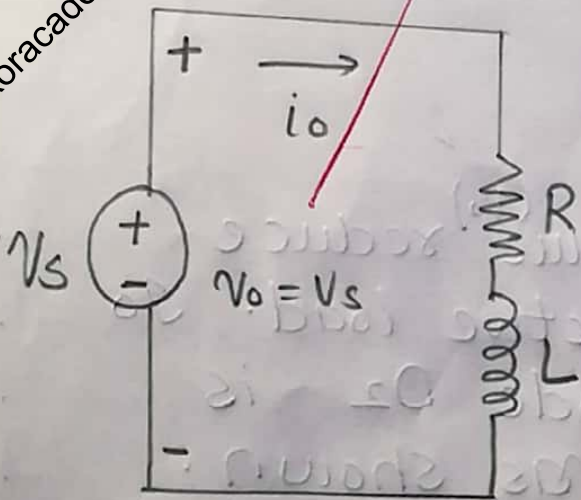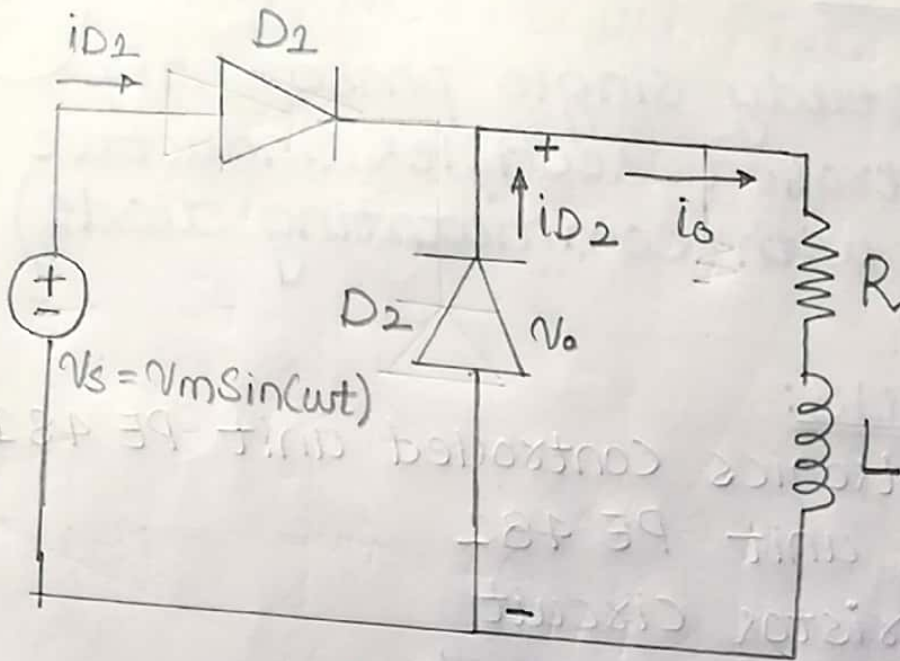

$$V_s > 0$$

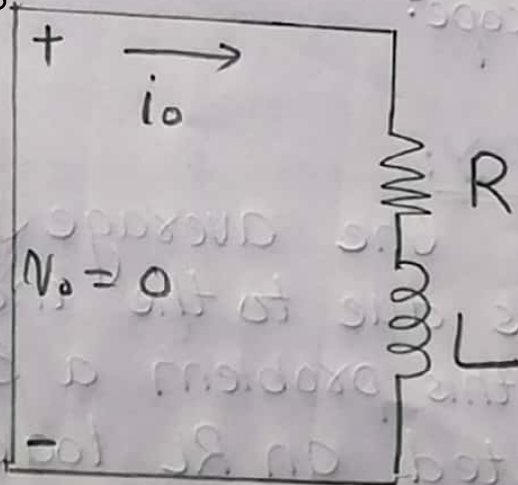

$$V_s < 0$$

HALF WAVE RECTIFIER

WITH FREEWHEELING

DIODE

For a positive source voltage

D_1 is ON

D_2 is OFF (open circuit)

The voltage across RL load is the same as the source.

For a negative source voltage,

D_1 is OFF (open ckt)

D_2 is ON (short ckt)

The voltage across RL load will be zero.

Since the voltage across the RL load is the same as the source voltage when the source is positive and is zero when the source is negative.

The load voltage is **half-wave rectified sine wave**.

PROCEDURE:

I implement the circuit according to the circuit diagram
I just connected diode D_2 across the load. I note V_m , V_{rms} and V_o from oscilloscope

OBSERVATION AND CALCULATION

Sr No	α	V_{rms} (V)	$V_{o\text{ cal}}$ (V)	$V_{o\text{ act}}$ (V)	$I_{o\text{ act}}$ (A)	$I_{o\text{ cal}}$ A	$\% \text{ Error}$ I_o	$\% \text{ Error}$ V_o
1	24°	33.92	20	22	0.4	0.47	17%	9.1%
2	54°	30.7	16	17.4	0.32	0.43	19%	8.04%
3	80.4°	26.1	12.44	13.52	0.25	0.297	13%	8%

PROCEDURE:




To implement the circuit according to the circuit diagram, first connected diode across the load. A meter was connected across the load and the waveform was observed on the oscilloscope.

PRECAUTIONS:-

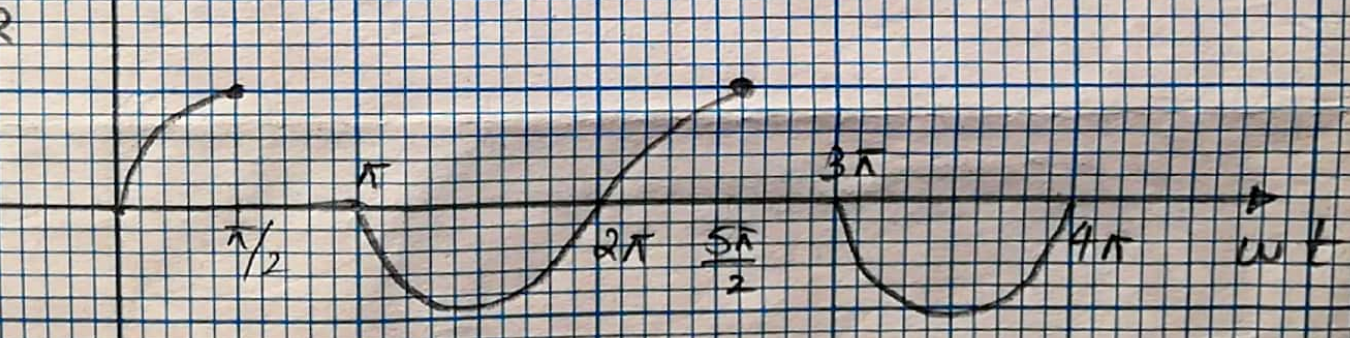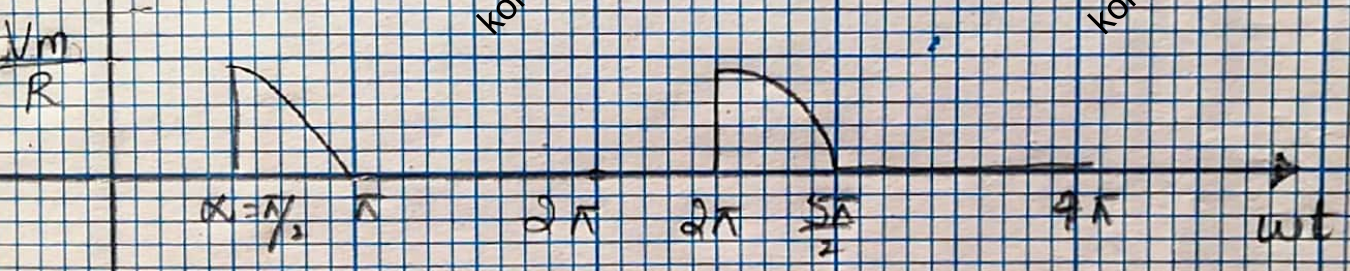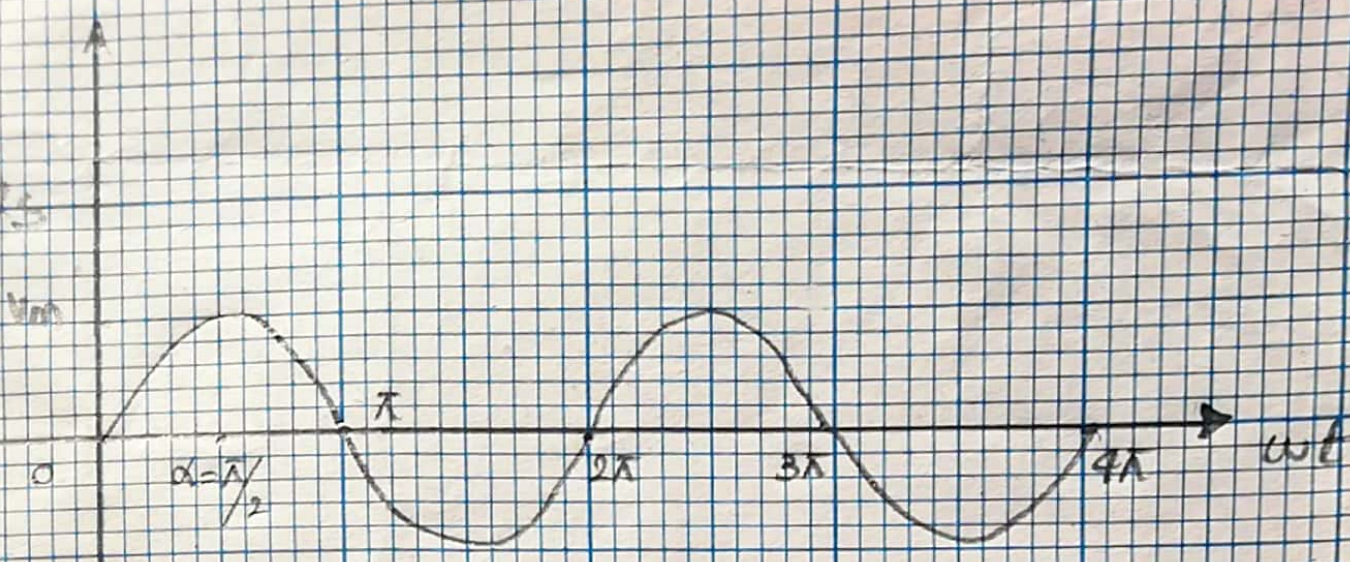
- 1) Note the readings carefully
- 2) Insert ckts properly

CONCLUSION:



I concluded from this experiment that by just connecting Diode D_2 parallel to load we get half wave rectified sine wave at the output.



339

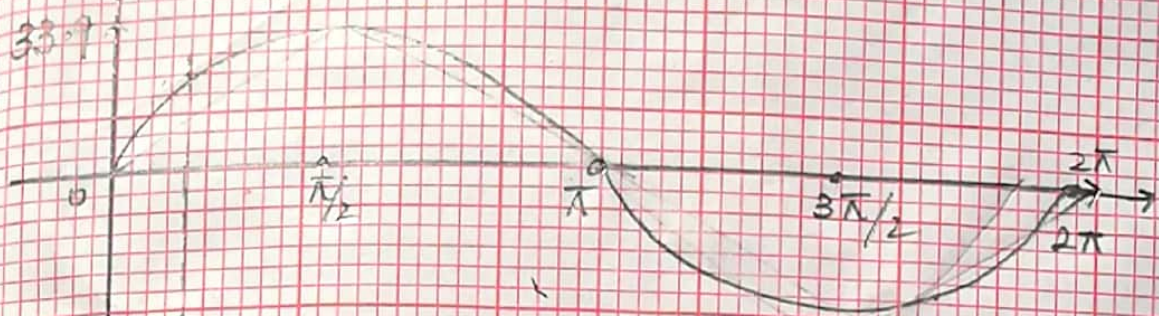

Scale

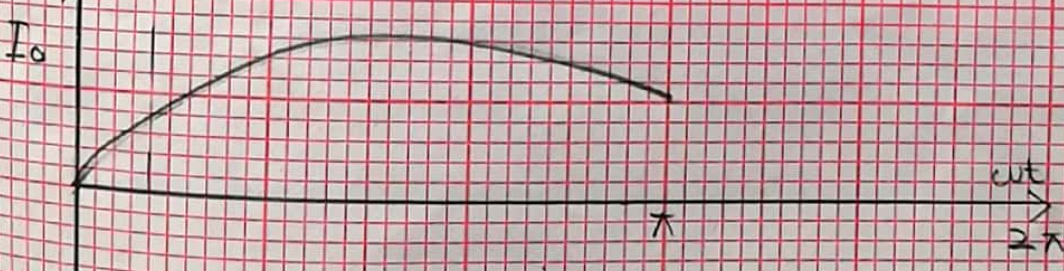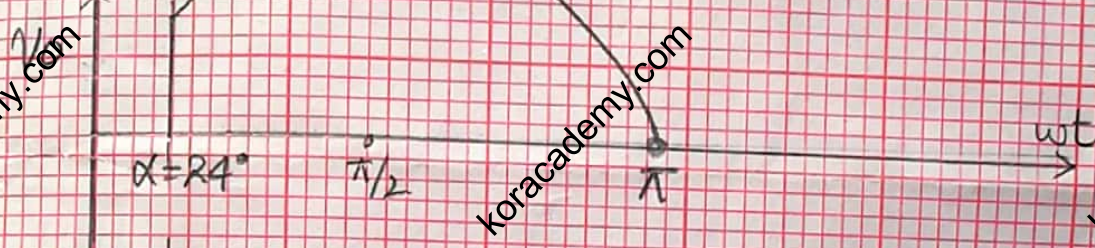

5074

LAB NO 7:

To study single phase full wave uncontrolled rectifier with resistive load.

APPARATUS:

Graphs Missing
File

90/100

Power electronics controlled unit PE 481.

LCR load unit PE 481

Single thyristor circuit


connecting wires

Oscilloscope


THEORY:

In this experiment we study full wave bridge rectifier. Full wave rectifier converts full wave of AC to DC. Therefore the average value increases.

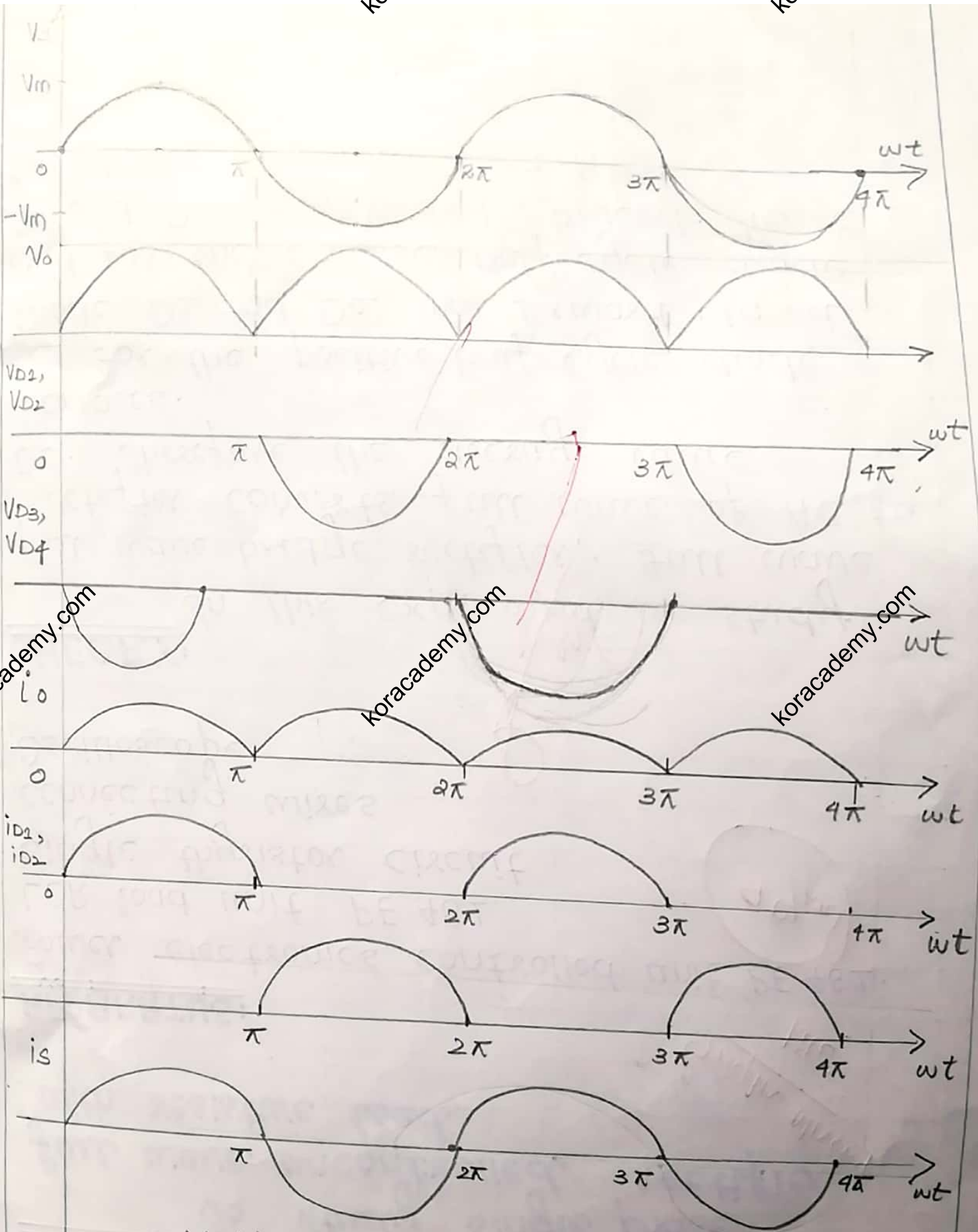
For the positive half cycle diode Diode D1 and D2 are forward biased and for the reverse half cycle diode D3 and D4 are forward biased. Hence two diodes conduct at a time



Voltages & Currents waveforms.

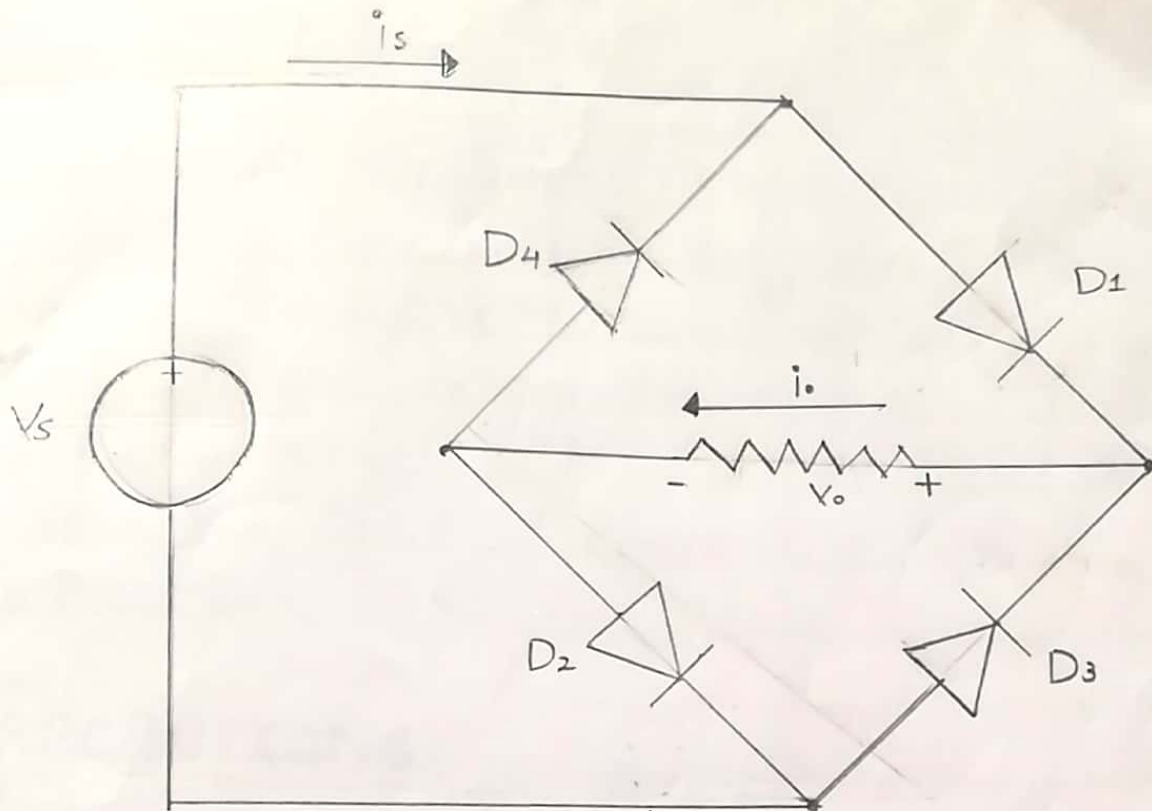

(a)

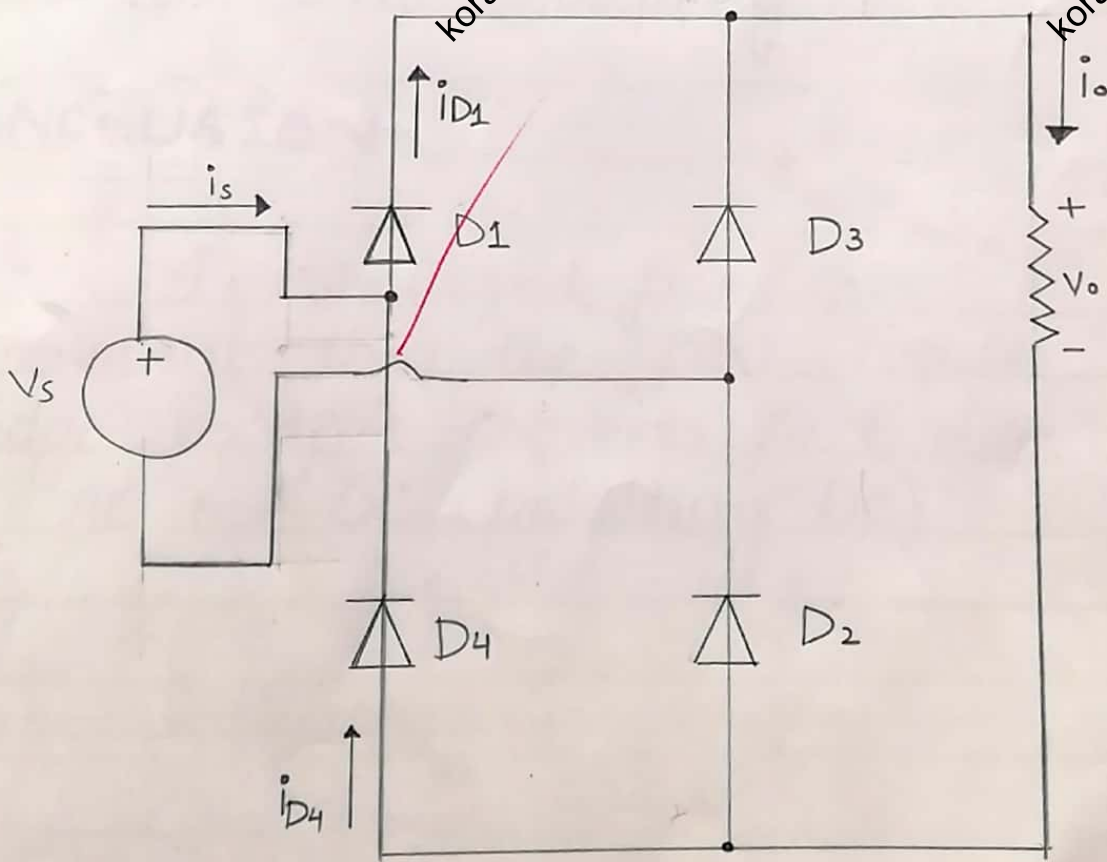

(b)

Full-Wave bridge rectifier (a) Circuit Diagram
 (b) Alternative representation

PROCEDURE:

I implement the circuit according to circuit diagram. The bridge rectifier was already there on the triggering circuit. I just connect it with load and across the load I connect the oscilloscope.

PRECAUTIONS:

Calculate the average value carefully.
Insert the ckt's properly.

CONCLUSION:

I concluded from this experiment that the full wave bridge rectifier converts full wave of AC to DC (pulsating DC).

EXPERIMENT NO 8: 5074

Bi-phase half wave fully controlled rectifier (Resistive load and Inductive load)

OBJECTIVE:

To observe local voltage waveform for bi-phase half-wave fully controlled rectifier.

APPARATUS:

Power Electronics control unit PE-481

Power Electronics LCR load unit PE-481

Full wave thyristor circuits PE-481-B

Oscilloscope CRO GS-1040 and connecting wires.

THEORY:

In this experiment we use a center-tapped transformer which divides the input voltage into V_1 and V_2 which are out of phase by 180° .

PROCEDURE:

- 1) Make the connections as shown in fig.
- 2) Connect the oscilloscope across the load.
- 3) Apply gate pulse to thyristors T_{11} and T_{12} and T_{p_1} and T_{p_2} of uni-junction

OBSERVATION AND CALCULATIONS:-

$$\text{Vertical divisions} = 5.2$$

$$\text{Volt per division} = 1\text{V/div}$$

$$\text{Amplification factor} = 20$$

$$V_m = 5.2 \times 1 \times 20 \Rightarrow \boxed{V_m = 52\text{volts}}$$

$\pi = 20$ div and conduction up to 13 divisions

$$\text{So } \alpha = \pi - 13 = 20 - 13 = 7\text{ div}$$

$$1\text{ div/cycle} = 9^\circ \Rightarrow \alpha = 7 \times 9 \Rightarrow \alpha = 63^\circ$$

For resistive load (R)

$$V_o(\text{calculated}) = \frac{V_m}{\pi} (1 + \cos \alpha) = 15.7\text{V}$$

$$V_o(\text{actual}) = 16.7\text{V}$$

$$V_{\text{rms}}(\text{calc}) = V_m \sqrt{\left(\frac{\pi}{2\pi} - \frac{\alpha}{2\pi} + \frac{\sin 2\pi}{4\pi}\right)}$$
$$= 15\text{Volts.}$$

For inductive Load (RL):-

$$\beta = \alpha + \pi \Rightarrow \beta = 7 + 20 = 27\text{ division}$$

$$\beta = 9 \times 27 \Rightarrow \boxed{\beta = 243^\circ}$$

transistor triggering circuit.

From center tapped transformer get V_1 and V_2 which are 180° out of phase.

During positive half cycle, thyristor T_1 start conduction as gate pulse is applied.

Similarly, T_2 thyristor starts conduction during positive half cycle of V_2 when gate pulse is applied.

Observe the load voltage using oscilloscope and measure " α ".

CONCLUSION:

I concluded from this experiment that when we increase delay angle α the mean voltage across the load decreases and vice versa. As it is also evident from the formula of mean load voltage and also from this experiment I concluded the mean voltage depends on delay angle (α).

$$V_o(\text{calc}) = 24.02V$$

$$V_{rms}(\text{actual}) = 21V$$

2 FOR $\alpha = 25^\circ$

Resistive Load:-

$$V_o(\text{calc}) = 20.8V$$

$$V_o(\text{actual}) = 21V$$

$$V_{rms}(\text{calc}) = 14V$$

$$V_{rms}(\text{actual}) = 12.1V \quad I_o = 0.4A$$

Inductive Load:-

$$V_o(\text{calc}) = 19.9V$$

$$V_o(\text{actual}) = 20V$$

$$V_{rms}(\text{calc}) = 44V$$

$$V_{rms}(\text{actual}) = 46V \quad I_o = 0.3A$$


$$\alpha = 63^\circ$$

Load	$V_o(V)$ calc	$V_o(V)$ actual	ERROR in V_o	$V_{rms}(V)$ calc	$V_{rms}(V)$	ERROR	$I_o(A)$
R	15.7	16.7	5%	15	14.2	6%	0.33
RL	10	12	11%	24.02	21	10%	0.24

$$\alpha = 22.5^\circ$$

Load	$V_o(V)$ calc	$V_o(V)$ actual	ERROR V_o	$V_{rms}(V)$ calc	$V_{rms}(V)$ actual	ERROR	$I_o(A)$
R	20.8	21	15%	14	12.1	8%	0.4
RL	19.9	20	4%	44	46	5%	0.3

$$\alpha = 63^\circ$$

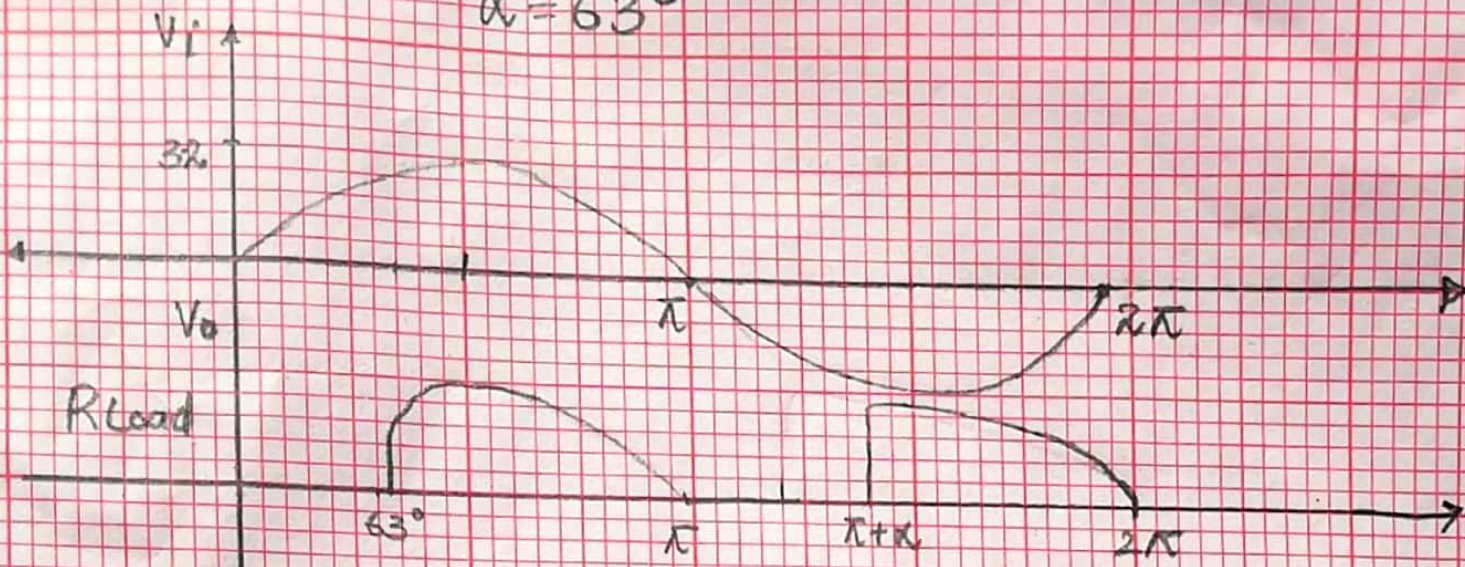


Scale


Y-axis $1sd = 2.6V$

X-axis $1sb = 4.5^\circ$


RL Load

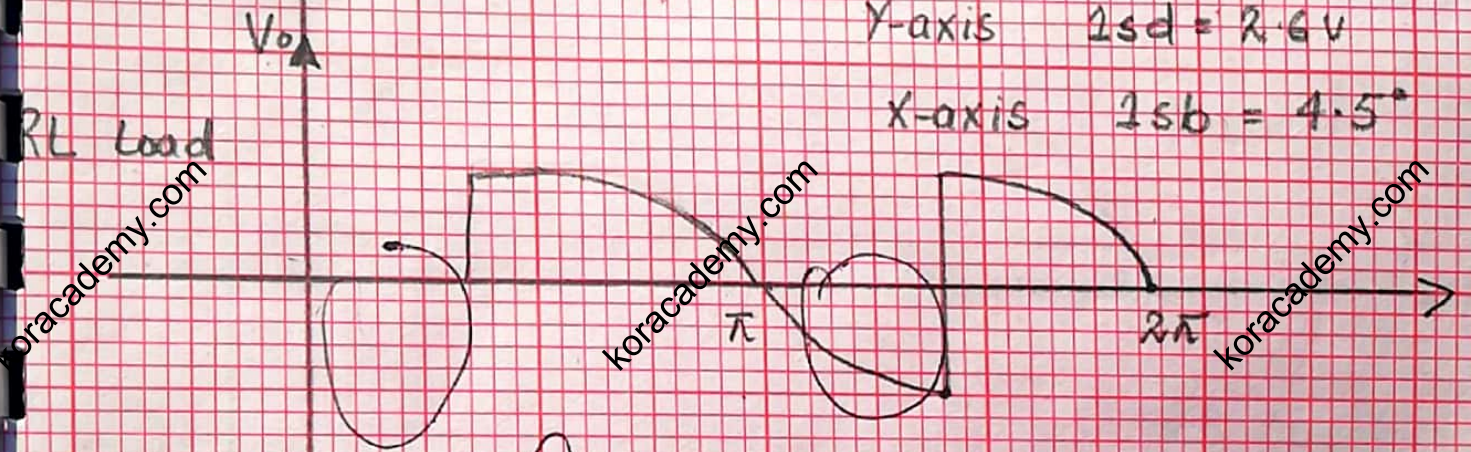

R Load

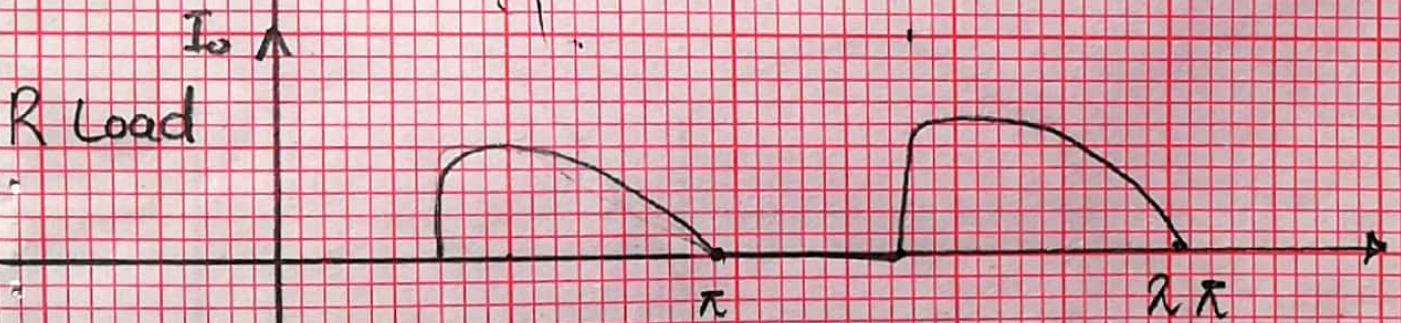

I_o

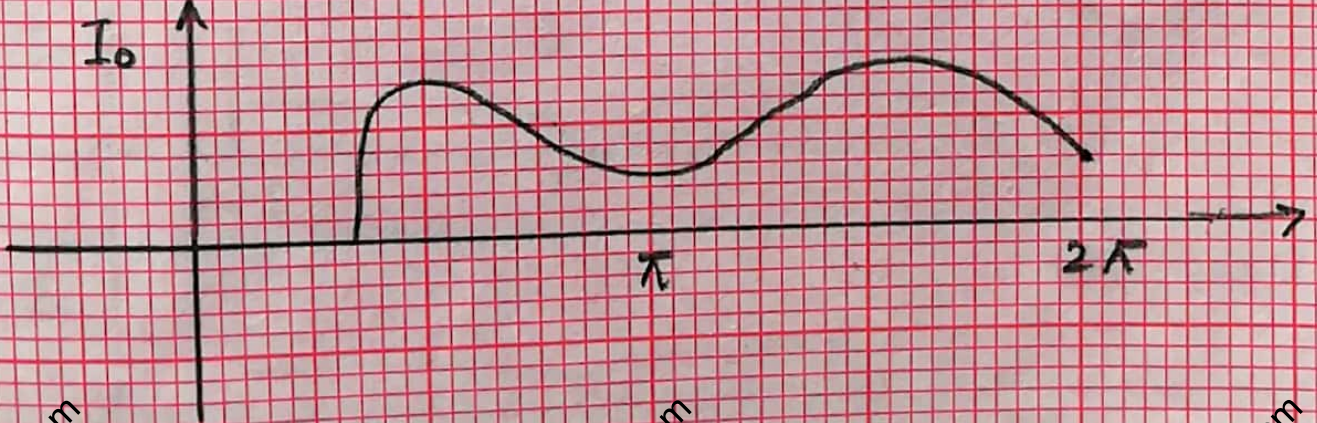

Scale: -

y-axis


$I_{sd} = 2.6V$

x-axis


$I_{sd} = 4.5^\circ$

$\alpha_o = 22.5^\circ$


$V_o \uparrow$

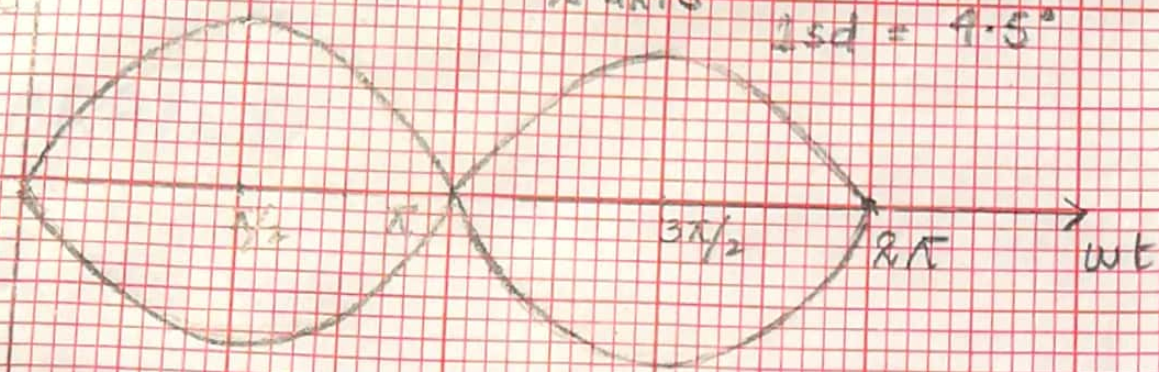


$V_o \uparrow$

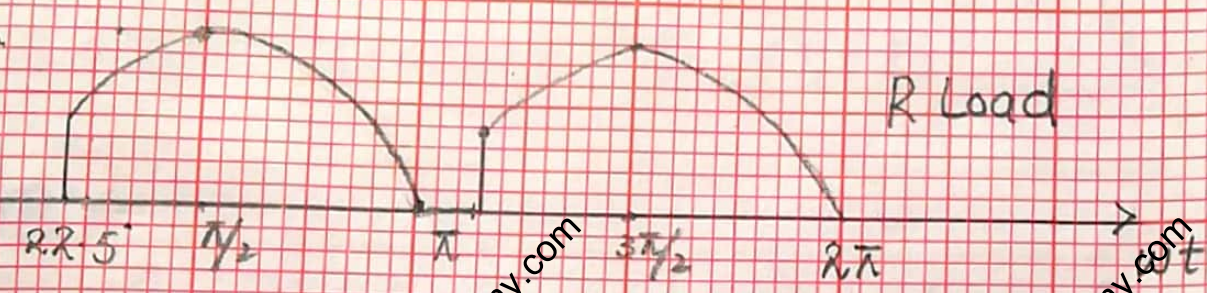


V_o

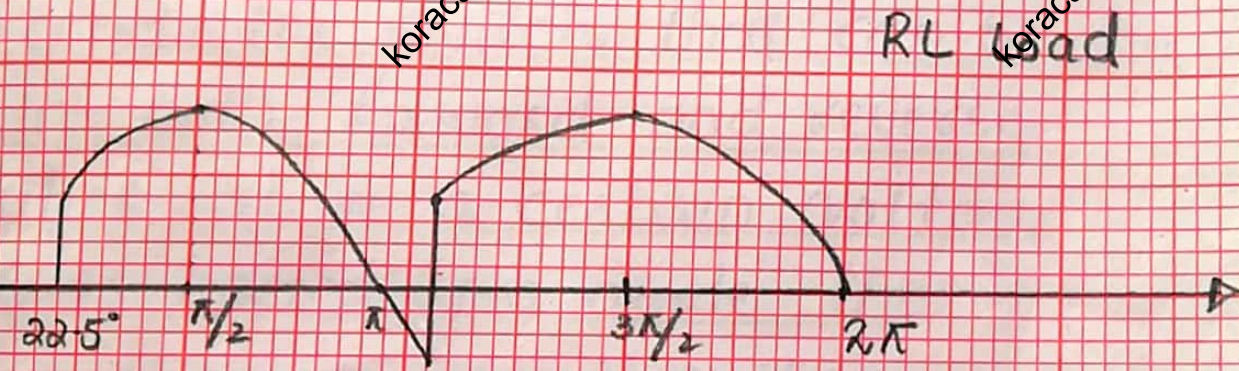

$I_o \uparrow$

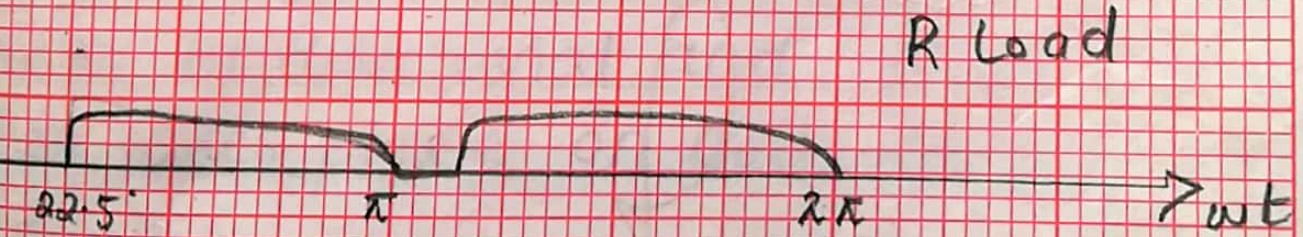

I_o

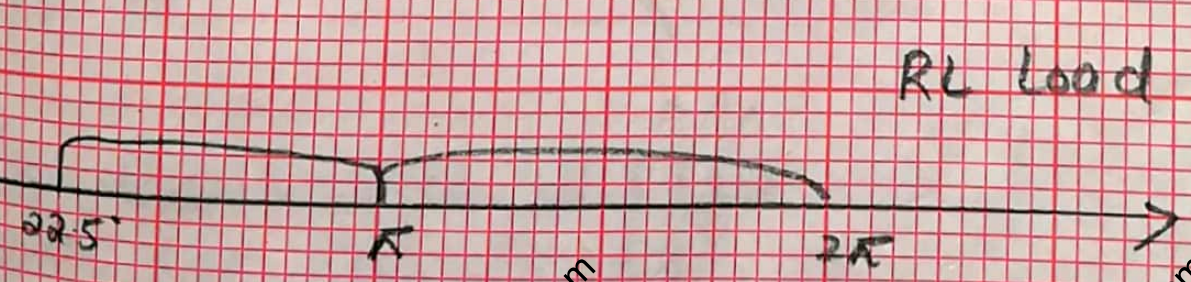

EXPERIMENT NO 9 5074

To study characteristic of "DIAC"

APPARATUS:

Power electronic control unit PE 481

Connecting cables

Oscilloscope


Basic trigger circuit PE 481D

98/100


THEORY:

A DIAC is a bi-directional semiconductor switch that can be turned ON in both forward and reverse polarities above a certain voltage. The DIAC is basically a diode that conducts after a "break-over" voltage. Its behaviour is bi-directional and thus its function takes place on both halves of an AC cycle.

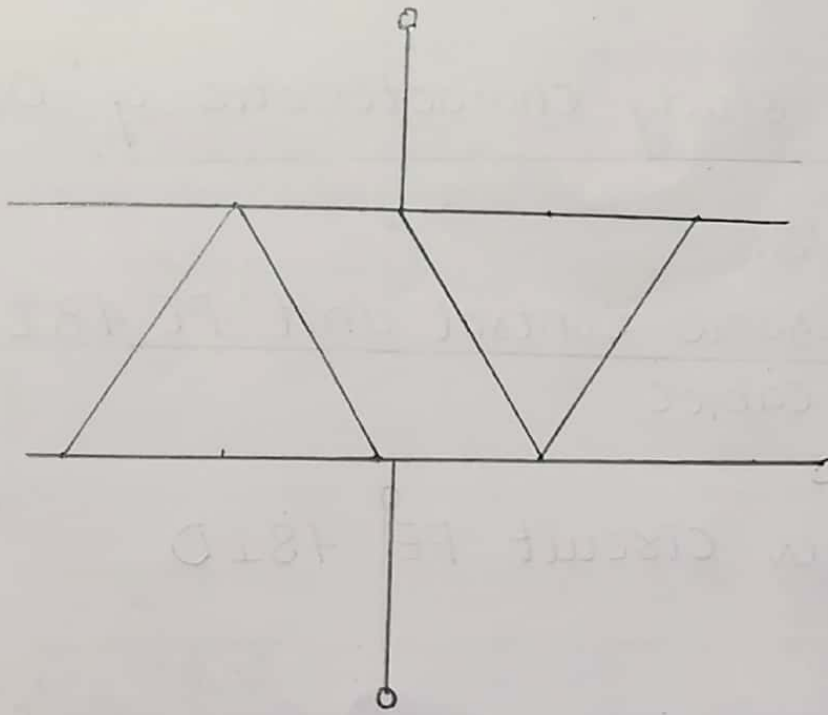The break-over voltage of "DIAC" depends on the specification for the particular component type. When the DIAC break over voltage occurs, the resistance of the component decreases.



DIAC SYMBOL

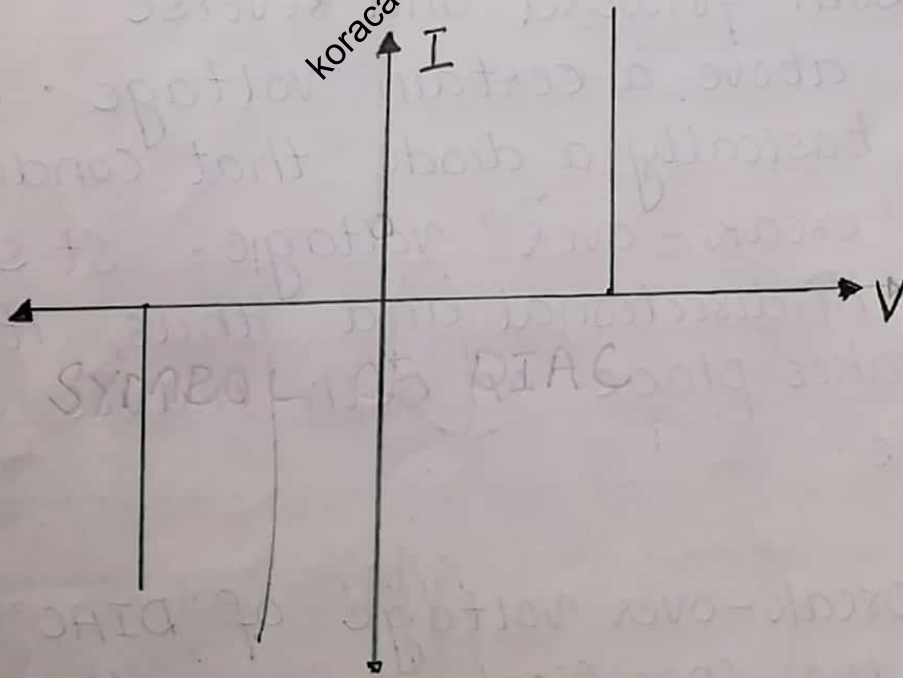

VI CHARACTERISTIC
OF DIAC

Unlike simple diodes DIAC conduct in both forward and reverse directions if a voltage higher than the break-over voltage is applied whereas the simple diode starts conduction in only forward direction.

PROCEDURE:

I connected the DIAC with oscilloscope to analyze the current & voltage across the DIAC. From 0 I started increasing the input voltage.

When voltage become greater than break-over voltage, the current started flowing through the device.

CONCLUSION:

I concluded from this experiment that DIAC is a special type of switch that is used to make the current flow in both forward and backward directions when the break-over voltage is reached.

5074

EXPERIMENT NO 10:

"To study the switching characteristic of a triac"

95/100

APPARATUS:


- 1) Power Electronic control unit PE 4810.
- 2) AC thyristor circuit PE 4810
- 3) Power Electronic LCR load unit PE-481.

THEORY:



The triac can be turned on by either by +ve current or -ve current pulse applied at its gate terminals. However in practice triac's with -ve gate pulse are usually used.

The triac conducts in both directions. In order to conduct gate pulse must be provided when Anode 1 is +ve SCR conducts because of forward biasing same case with SCR₂ if anode 2 is +ve. Hence it would conduct if sufficient gate pulse is provided.

SYMBOL :

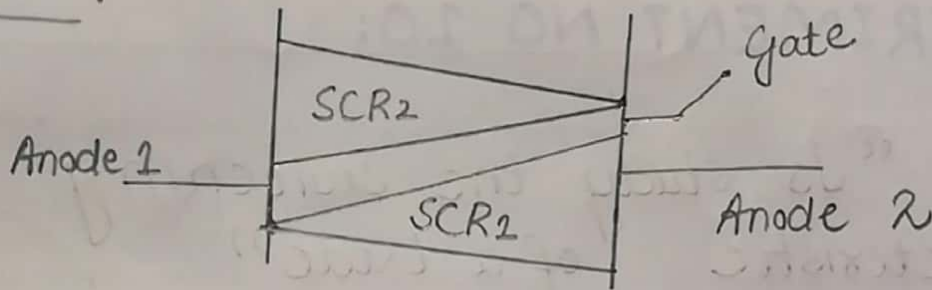

Equivalent circuit:-

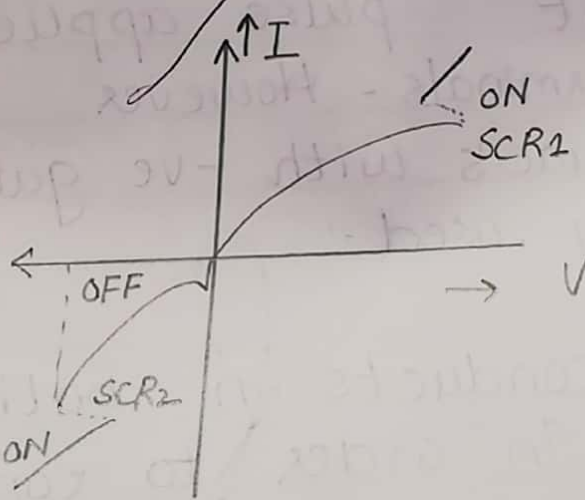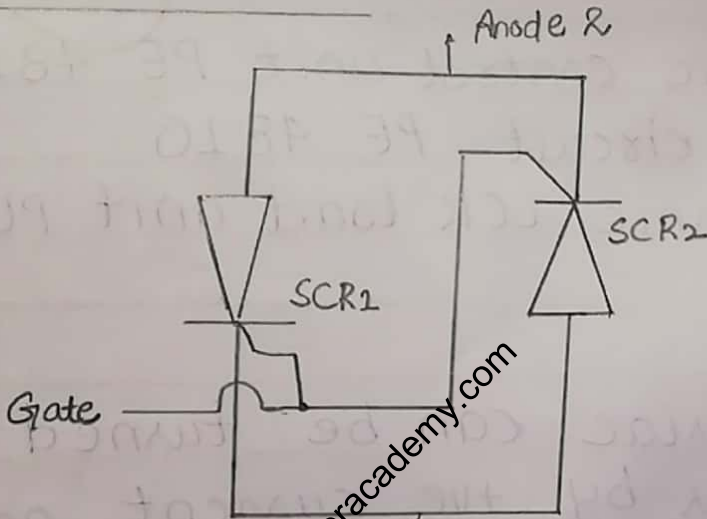

OBSERVATION

$\alpha = 89.6^\circ$	$V_{rms} \text{ actual} = 22V$	$V_{rms} \text{ (cal)} = 21.22V$
$\alpha = 125.5^\circ$	$V_{rms} \text{ actual} = 13V$	$V_{rms} \text{ cal} = 11.55V$

It is a five layered device having PNPN. It allows the current in either direction.

CONCLUSION:

In this experiment we studied about TRIAC, its voltage waveform and found out RMS voltage for different values of α .

EXPERIMENT NO 11 :-

To study voltage regulation using triac in phase control mode

APPARATUS:

Power Electronics Control unit PE 481

Oscilloscope

Connecting cables

Power electronics LCR load units PE 482

Basic trigger circuit PE 481D


THEORY:

Triac is a bi-directional semi-conductor device that conducts current in both forward and backward directions when triggered. It is a three terminal device

Gate pulse (the firing angle) is applied at the gate terminal of a triac to make it trigger. In AC thyristor circuits PE 481C module,

we already have a triac circuit, to which AC input 50V signal is applied and we use this triac in our circuit.

Circuit Diagram:-

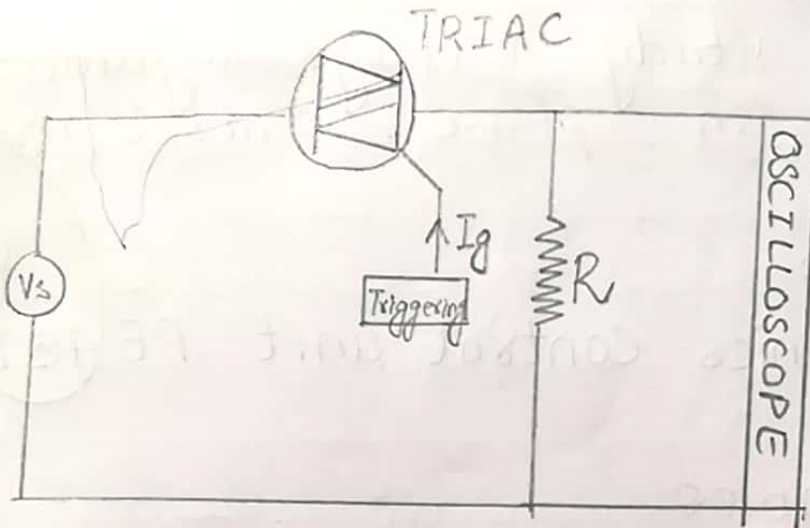

OBSERVATIONS:-

$$20 \text{ div} = 2\pi$$


$$\pi = 10 \text{ div}$$

$$1 \text{ div} = 18^\circ$$

$$\alpha + 7 = 10 \text{ div} = \pi$$

$$\alpha = 3 \text{ div}$$

$$\alpha = 54^\circ$$

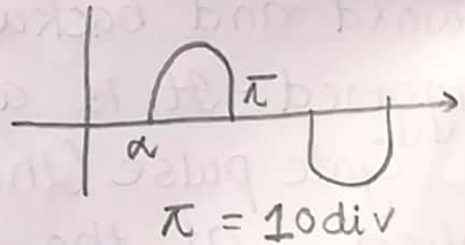

Now:

$$V_{rms} = \sqrt{2 \left(\frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \, d\omega t \right)}$$

$$= V_m \sqrt{\frac{1}{2\pi} (1 - \cos 2\omega t \, d\omega t)}$$

$$V_{rms} = 39.15 \text{ volts.}$$

PROCEDURE:

I made the circuit practically according to the ckt diagram.

I applied the firing angle from the basic trigger circuit


I connected the output of load with oscilloscope to analysis the output voltage across the load.

I took different values of firing angle α and calculated the rms value of voltage







Changing triggering angle change the voltage waveform.

CONCLUSION:

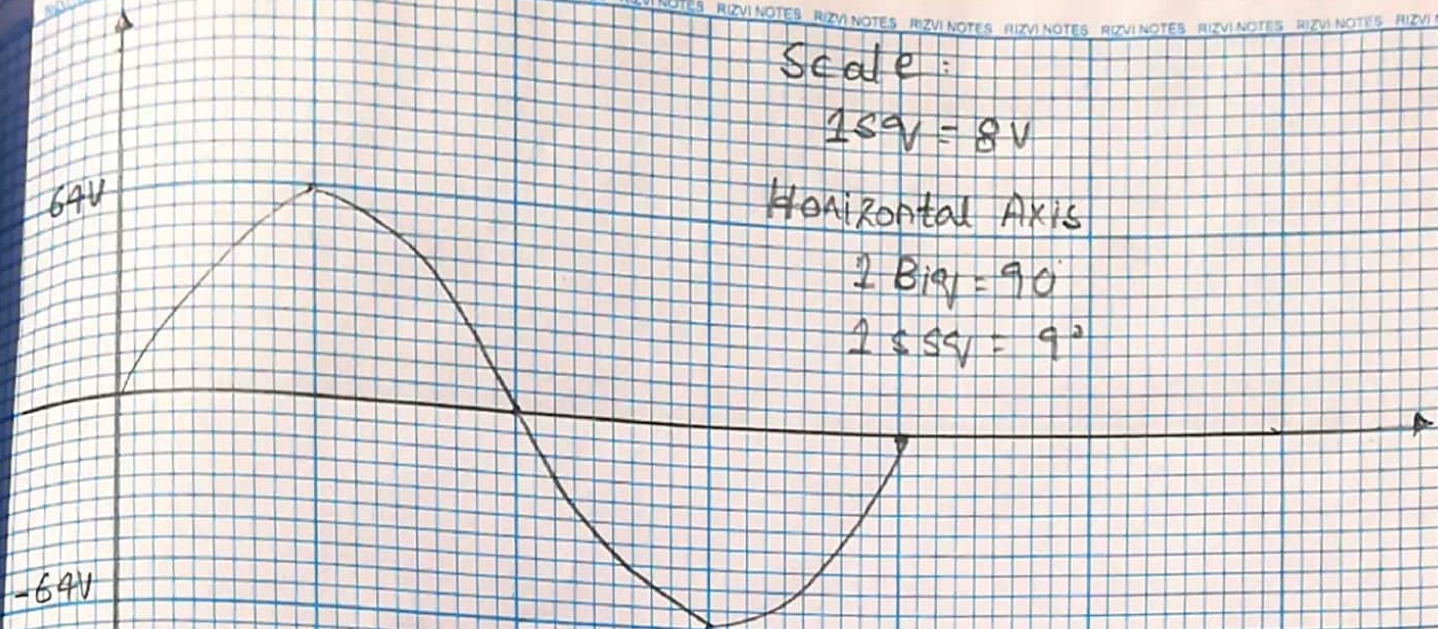From this experiment I concluded that triac does not conduct at all voltages. It starts conduction at a certain level of gate voltage.



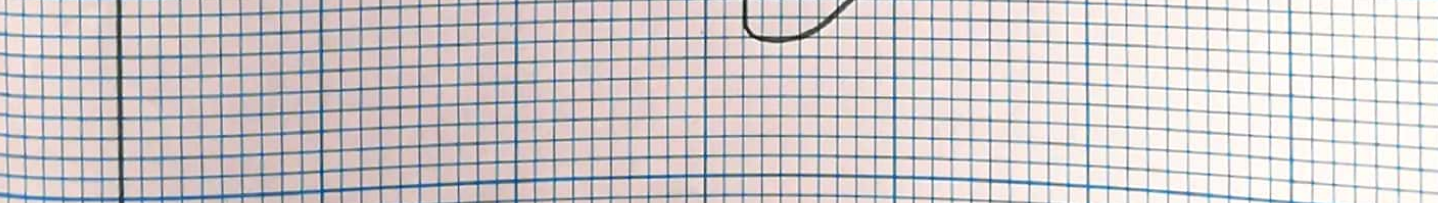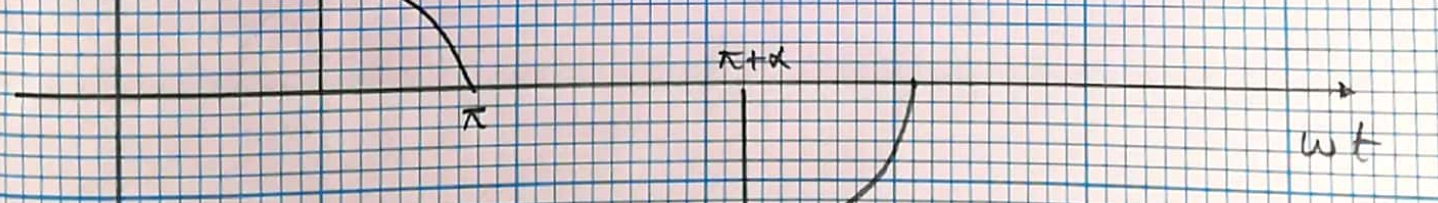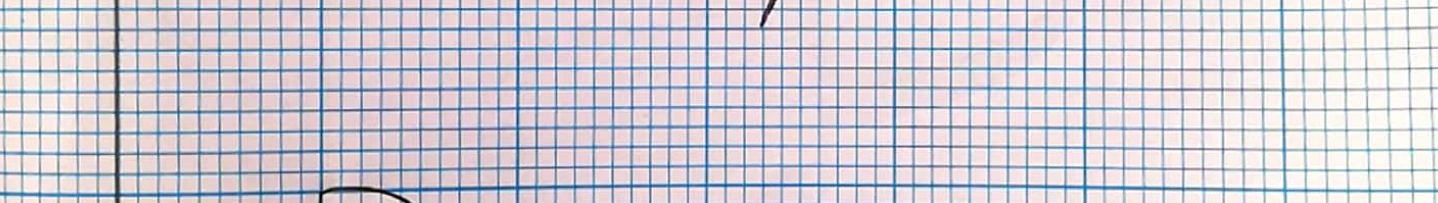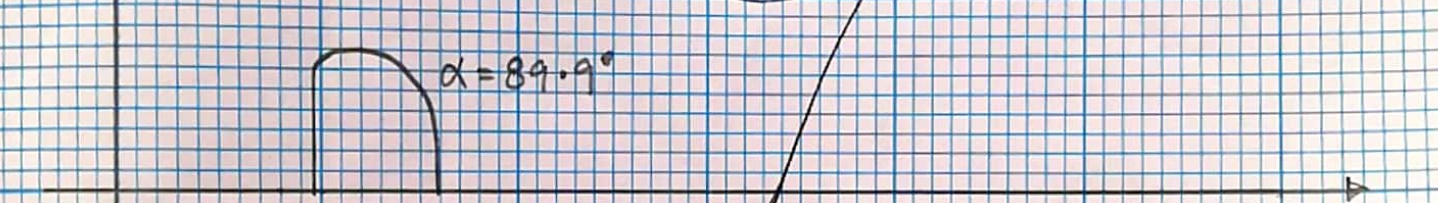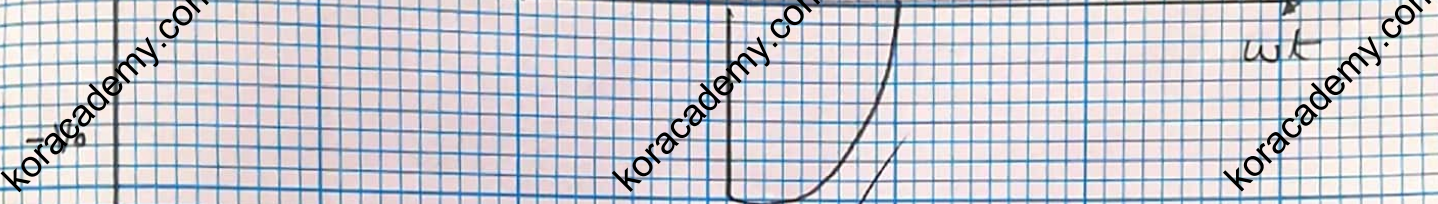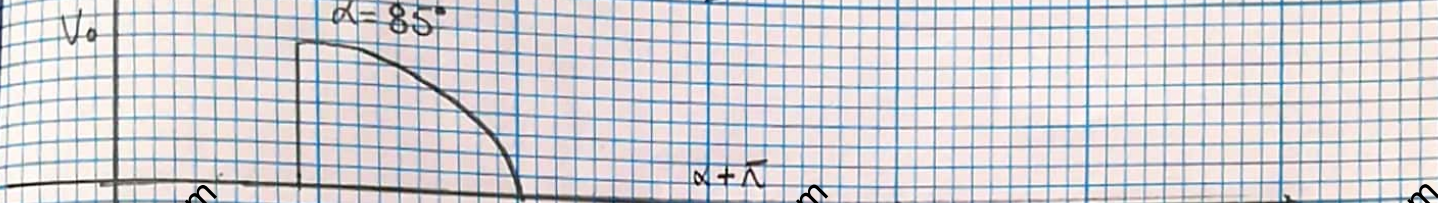Scale :
1 sqv = 8V
Horizontal Axis
2 Bigv = 90°
2 sqv = 9°






Scale:

Horizontal Axis

1 big sq = 90°

1 small sq = 9°

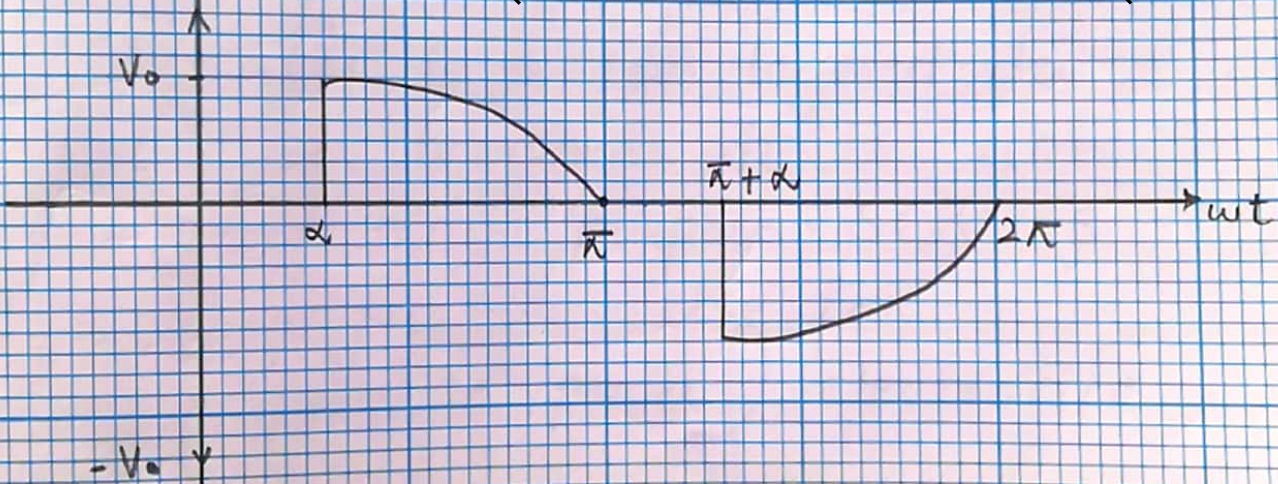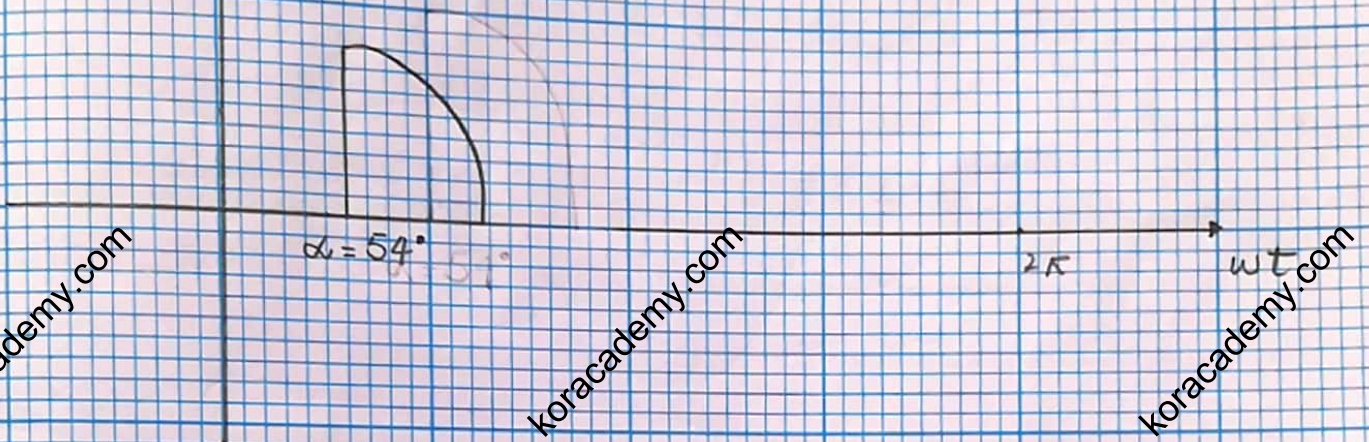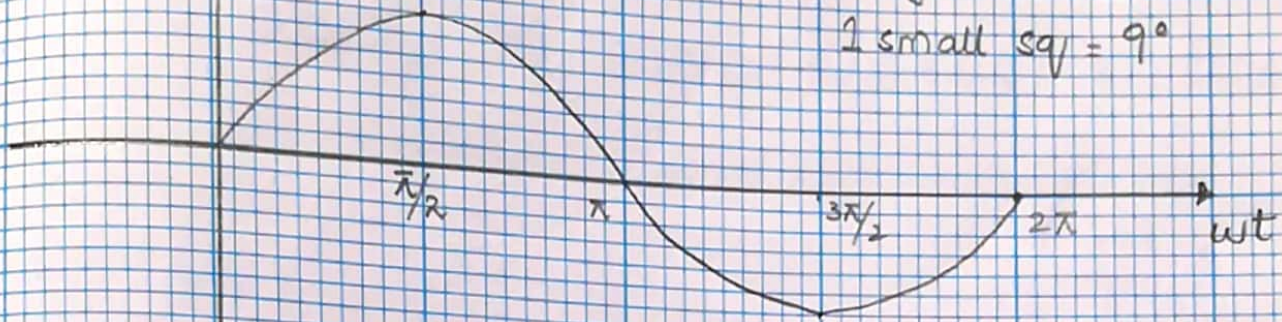

EXPERIMENT NO 12: 5074

TITLE:

To study dynamic characteristics of SCR

APPARATUS:

9/6/18



Power Electronic control unit PE-482
Power electronic LCR load unit PE-482
Single thyristor circuit PE 482-A
Oscilloscope (CSO-1030) etc

THEORY:

Thyristor is a four layered device with two power terminals. It is use for the switching purpose. SCR is a type of thyristor use for switching purpose in power electronic devices.

For SCR to begin to conduct, it must have a gate current applied while it has positive anode to cathode voltage. When gate pulse is given the SCR gets triggered and starts conduction. The minimum gate current that must

SYMBOL

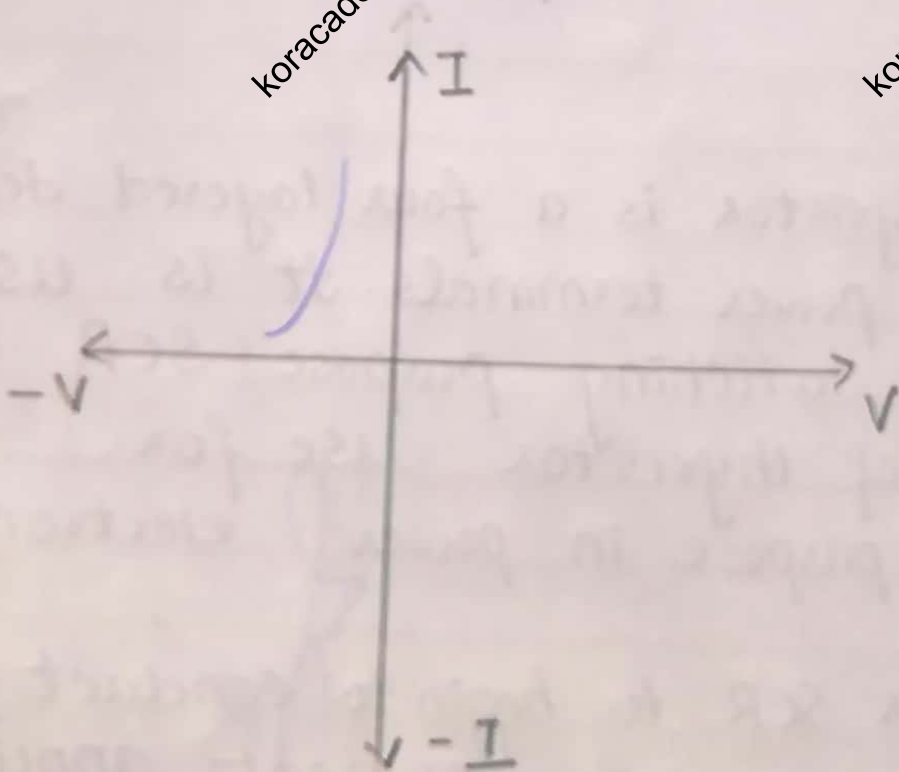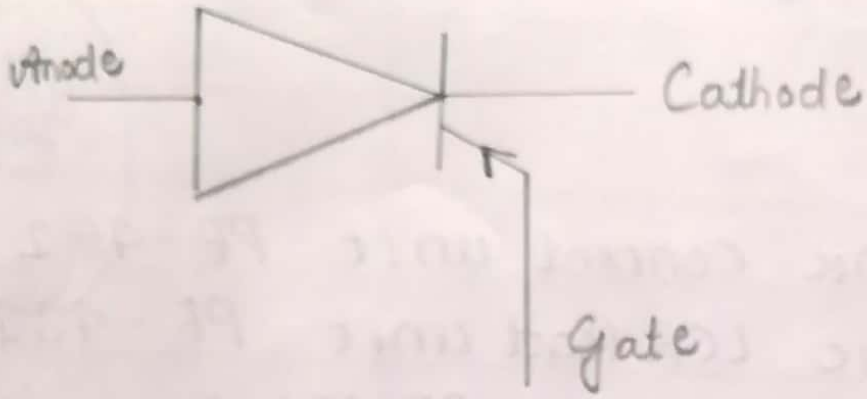

be to SCR to make the current flow through the device is called latching current. The minimum current that must be maintained through the device is called holding current.

PROCEDURE:

Change oscilloscope mode to x-y mode so we can analyze both voltage & current through SCR simultaneously on oscilloscope.

x-axis is for voltage.

y-axis is for current through the device.

Connect SCR with oscilloscope.

Analyze the output V-I characteristics from oscilloscope.

CONCLUSION:

In this lab I observed the dynamic characteristics of SCR. We can obtain the V-I curve using oscilloscope and we can control the output by changing the firing angle.

EXPERIMENT NO 13

To study voltage regulation using inverse parallel thyristor


APPARATUS:

Power electronics control unit PE 481
 Power electronics LCR load unit PE-481
 uni-junction transistor trigger circuits PE 481E
 Thyristor circuits PE 481C
 Oscilloscope

28/10/23

THEORY:

A thyristor is a solid state semi-conductor device with four layer of P and N type material. It acts exclusively as a bi-stable switch conducting when the gate receives a current trigger. An SCR is a type of thyristor that in which turn off of the device is in our control. SCR starts conduction when anode of the SCR is positive with respect to cathode and when a gate pulse is given to the gate terminal to make it trigger.

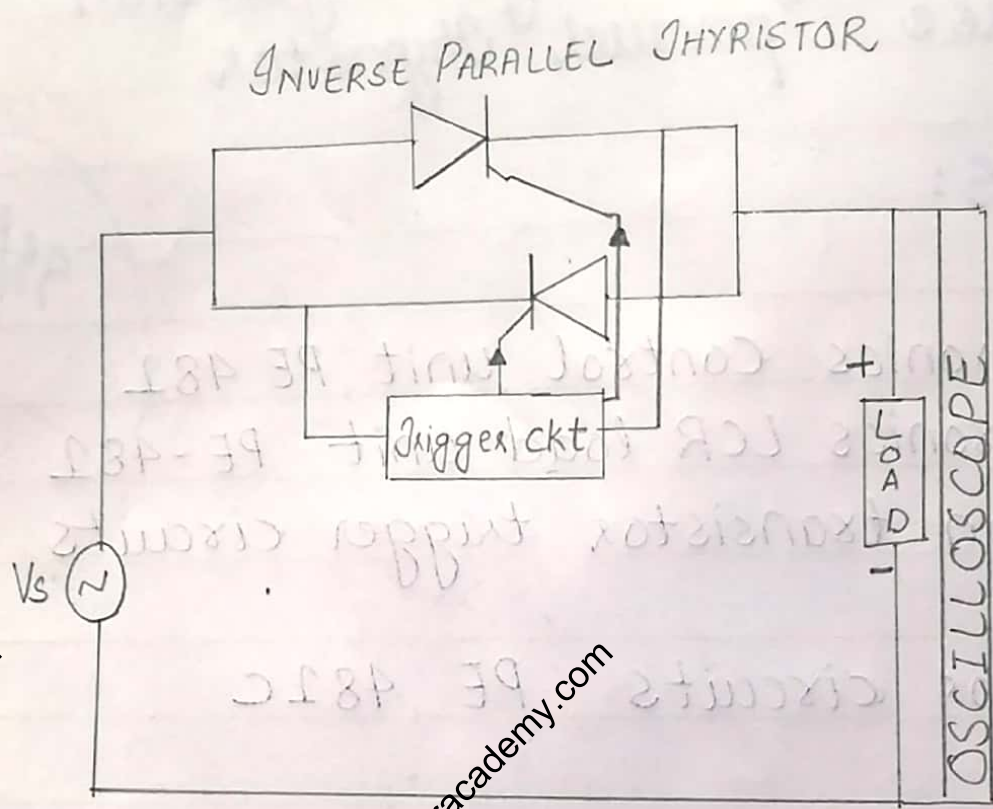

CIRCUIT DIAGRAM

When two SCRs are connected in Anti-parallel manner it is called inverse parallel thyristor.

PROCEDURE:

I made the circuit practically according to the circuit diagram using the mentioned apparatuses.

Input signal is applied

fixing angle is given to the SCR.

For positive half cycle one thyristor is forward biased and it starts conduction when it receives gate pulse while 2nd SCR is reverse biased.

For -ve half cycle we still have O/P voltage because 2nd SCR becomes forward biased and it conducts when it receives gate pulse while 1st SCR is reverse biased.

I analyzed the output voltage across the load using oscilloscope

For different values of fixing angle I analyzed the circuits and plotted the graphs.

OBSERVATION AND CALCULATION:

Horizontally:

$$20 \text{ div} = 360^\circ$$

$$1 \text{ div} = \frac{360}{20} = 18^\circ$$

$$\alpha_1 = 2 \text{ div} = 2 \times 18^\circ = 36^\circ$$

$$\alpha_2 = 3 \text{ div} = 3 \times 18^\circ = 54^\circ$$

$$\alpha_3 = 6 \text{ div} = 6 \times 18^\circ = 108^\circ$$

Vertically: -


$$V_m = 10 \text{ div}$$

$$V_m = 10 \times 10 = 100 \text{ V}$$

α	$V_{o \text{ rms}}$ (actual)	$V_{o \text{ rms}}$ (calculated)	% Error
36°	43.19V	41.21V	4.8%
54°	40.62V	40.05	1.39%
108°	28.28V	26.18	8.02%

CONCLUSION:

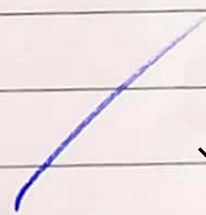In lab I observed that inverse parallel thyristor circuit we have output voltage for both +ve and -ve cycles of input voltage and can be controlled by fixing angle (α).



Scale:-

$$\phi = 108^\circ$$


Scale

x-axis

1 small div = 38°

y-axis

1 small div = 20V

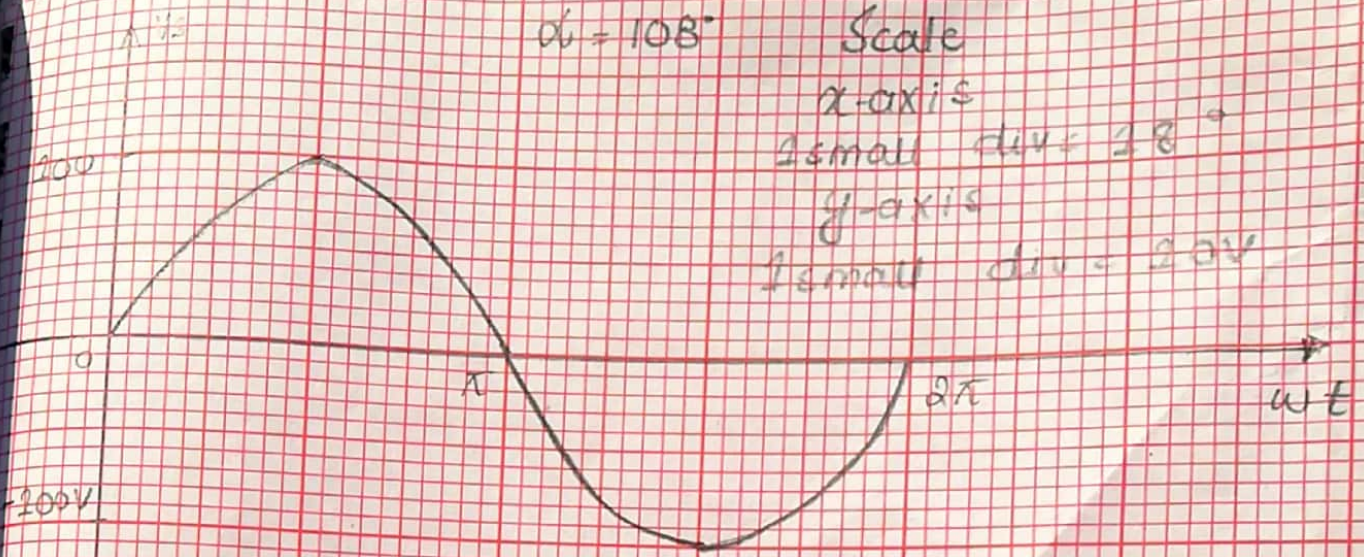

α

$$\alpha = 108^\circ$$

$V_o(V)$

100V


$$\alpha = 108^\circ$$

$$\pi + 108^\circ$$

2π

100V

wt

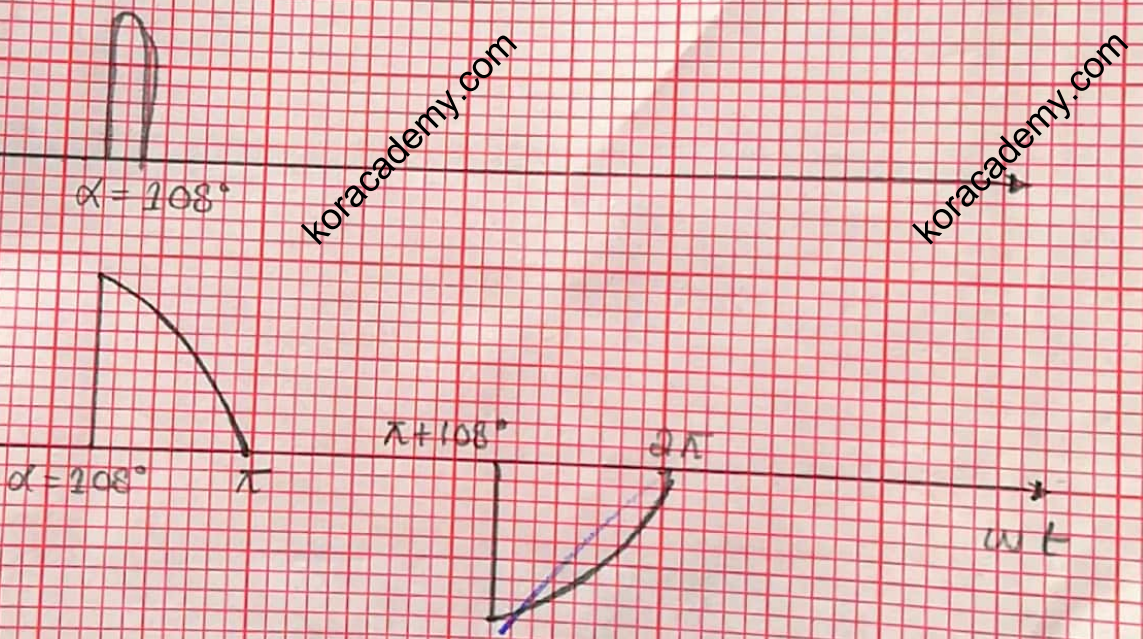


1/3/2017

Scale:-

X-axis

1 small div = 25°

1 small div = 10V

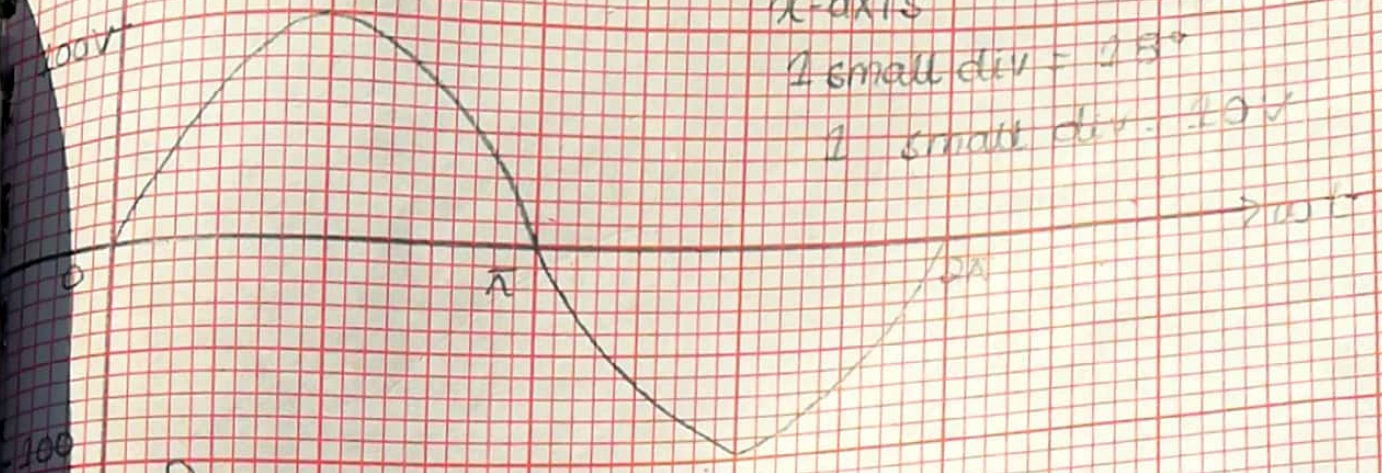

$\alpha = 54^\circ$

koracademy.com

koracademy.com

koracademy.com



$\alpha = 54^\circ$

koracademy.com

koracademy.com

koracademy.com