

NOTES

Subject _____

Sr. No:

Date

Topic

ELECTRICAL MEASUREMENT AND INSTRUMENTATION

Sir Anjid khattak.

Sir FAYOON,

Books:

Accuracy, Precision, Sensitivity,
resolution, significant figures

Error with types

Statistical analysis \rightarrow mean, standard

deviation, property of error

system of units, Galvanometer.

Ammeter, multirange ammeter.

egs \rightarrow

DC voltmeter, voltmeter \rightarrow

Series type ohmmeter \rightarrow

shunt \rightarrow \rightarrow eg

calibrator.

Rectifier type instruments.

26/9/19


Electronics deal with motion of electrons.

Electrical Electronics




Remote

Vacuum tube \Leftrightarrow diode

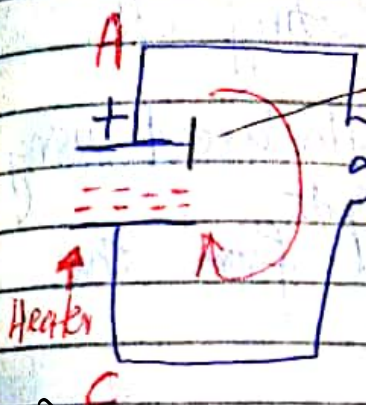

control (grid)

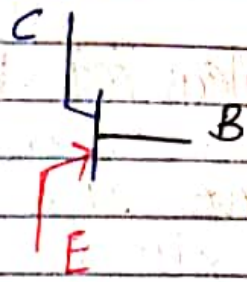

Thermionic emission \Leftrightarrow transistors

Measurement

Man uses his imaginative skills.
 ↳ to identify a physical phenomena
 ↳ developed and utilized a means to understand this.

To measure means to determine the magnitude ~~and~~ or extent or degree of the condition of system in terms of some standard.

All measuring systems based on laws of nature.

Meter: Instrument used to indicate or record measured value.

Measurand Variable under measurement.


Metrology and accurate Science of dealing with precise measurements.

Instrument or magnitude A device for determining the value of a variable.

↳ used for sensing, detecting, measuring, recording, controlling, communicating etc.

Measured value is a value calculated using a measurement system / instrument.

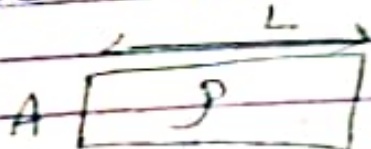True value is value calculated from the rated values.




$$R = \frac{PL}{A}$$

Accuracy is the degree of closeness of measured value with true value.

Precision is the degree of closeness of measured values with each other.


eg bird eye target

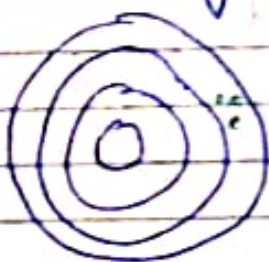

less accurate
more precise



Accurate
and precise

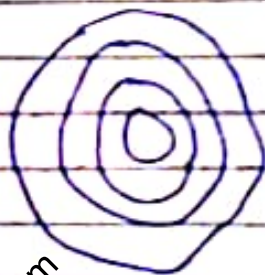

Sensitivity of a device is defined as the ratio of change in output signal (response) to the change in input variable. $S = \frac{\Delta \text{output}}{\Delta \text{input}}$

Resolution is the smallest change in input that can be detected by device.
 ↳ depends on the no. of significant figures.

Significant Figures.

- (i) Any non zero digit is significant.
- (ii) Any zero b/w two non zeros is significant.
- (iii) Any zero before non zero is not significant.
- (iv) Any zero after non zero are not significant if the given number has no decimal part.
- (v) Any zero after non zero is significant if it has decimal.

Number	# of sig F
17	2
132.556	6
101	3
0.5	1
0.00305	3
5000	1
1000	4
2000	2
370.	3
0.003205300	7

$5000 = 5 \times 10^3$
 $370. = 3.70 \times 10^2$
 $5000 = 5.00 \times 10^3$

One trillion, 2 billion, Nine thousand

1 billion = 1000 millions

1 trillion = 1000 billions

Addition And Subtraction.

(i) Math first, sig figures last.

Arithmetic operations like less and more are done on results to less significant

cid if both nos have

$$\begin{array}{r} 156.0 \\ + 0.702 \\ \hline 156.702 \end{array}$$

$$\begin{array}{r} 0.854 \\ - 0.0594 \\ \hline 0.7946 \end{array} \rightarrow 0.795$$

(ii) if both numbers or any one does not have a decimal point. depend on the position of ~~highest~~ highest

$$\begin{array}{r} 4.51 \\ + 3 \\ \hline 7.51 \end{array}$$

$$\begin{array}{r} 12000 \\ - 3500 \\ \hline 87500 \end{array}$$

(Answer in thousands)

$$\begin{array}{r} 500.0 \\ - 90 \\ \hline 410.0 \end{array}$$

$$\begin{array}{r} 500 \\ - 90 \\ \hline 410 \end{array}$$

Multiplication And DIVISION

Answer has lowest no. of decimal

$$\begin{array}{r} 815.991 \\ \times 329.6 \\ \hline 264870.670 \end{array}$$

Lecture 2

02/Oct/19

Error: Difference b/w true and measured value


Accuracy and Precision

↳ degree of closeness of true value of quantity under observation.

Precision → degree of agreement within a group of measurements or instruments.

(i) is composed of two ch
(ii) conformity
(iii) No. of sig fig.

sig fig ↑

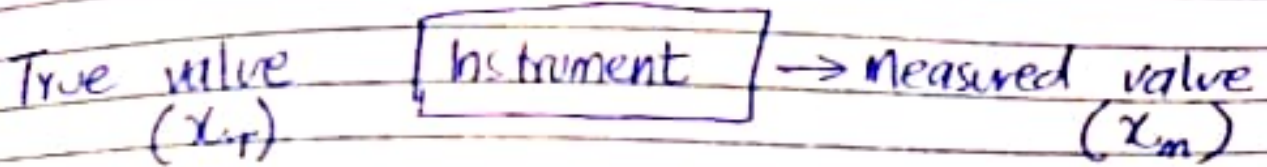

$$\text{Error} = x_m - x_T$$

Reducing error by statistical analysis:

→ more than one reading required.

(i) Arithmetic Mean.

Readings → $x_1, x_2, x_3, \dots, x_n$

$$\bar{x} = \frac{x_1 + x_2 + x_3 + \dots + x_n}{n}$$

→ most value.

2) Deviation from the mean

$$d_1 = x_1 - \bar{x} \quad d_2 = x_2 - \bar{x} \quad d_n = x_n - \bar{x}$$

Example Readings 2, 4, 3, 3, 2

$$\bar{x} = \frac{2 + 4 + 3 + 3 + 2}{5} = 2.8$$

$$d_1 = -0.8 \quad d_2 = 1.2 \quad d_3 = 0.2 \quad d_4 = 0.2 \quad d_5 = -0.8$$

3) Average deviation

$$D = \frac{|d_1| + |d_2| + \dots + |d_n|}{n}$$

4) Standard Deviation

RMS deviation

$$\delta = \sqrt{\frac{d_1^2 + d_2^2 + d_3^2 + \dots + d_n^2}{n}}$$

↳ called as population standard deviation

$$\delta = \sqrt{\frac{d_1^2 + d_2^2 + \dots + d_n^2}{n-1}}$$

↳ Sample standard deviation


Parameter	Statistic
Each and every individual	Small sample out of the total
Mean is parameter	Mean is statistic
$\bar{x} = \frac{\sum_{i=1}^n x_i}{n}$	$\bar{x} = \frac{\sum_{i=1}^n x_i}{n}$

degree of freedom

Probability of Error.

Normal Distribution of Error;

Voltage Readings	99.7	99.8	99.9	100.0	100.1	100.2	100.3
Number of Readings	1	4	12	19	10	3	1

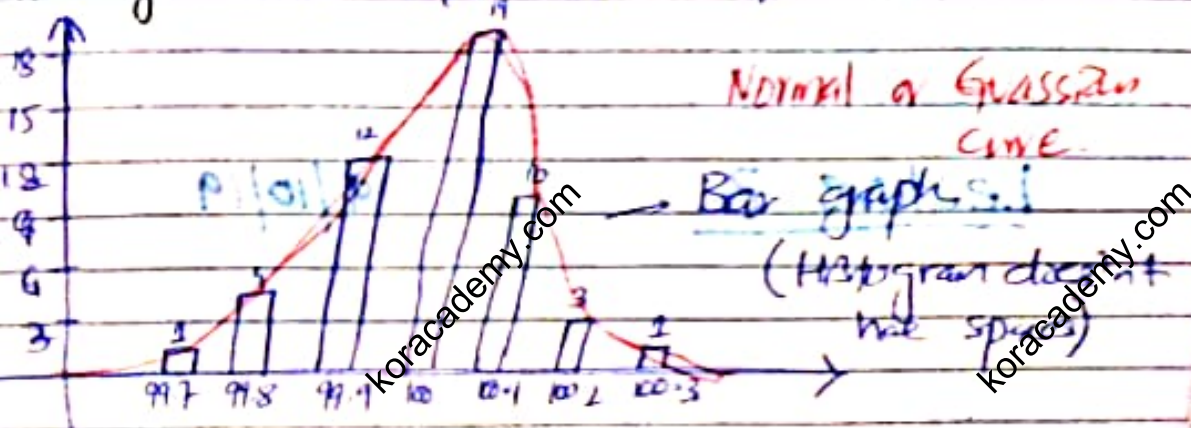


→ All observations include small disturbing effects called random errors.

→ Random error can be +ve or -ve


→ There is an equal probability of +ve and -ve

Small errors are more probable than large errors

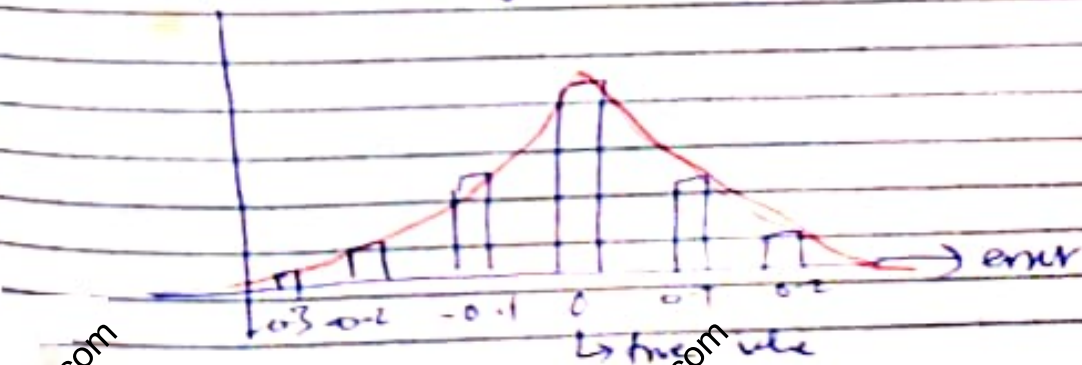→ There is an equal probability of + and - errors so that the probability of a given error will be symmetrical about 0 value



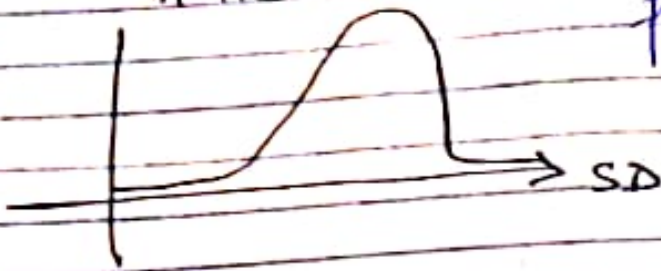In the standard deviation curve if you measure from $-x$ to x → you measure 100% of the area.



-2 to 2 |
 -2 to
 -3 to 3 → 44.
 -0.6745 to 0.6745 → 50%

Probable error = 0.6745 σ

Lecture 3

9/10/19

Chapter 2

1 meter is the length of light path travelled by light in vacuum in time interval of $\frac{1}{299,792,458}$ s. was defined in

Kilogram was defined in 1989. 1 kg is the mass of international prototype of kilogram (platinum iridium cylinder) kept at International Bureau of weights and measures at Paris.

1 second is the duration of 9,192,631,770 transitions of radiations corresponding to transition of hyperfine levels of ground state of Cs-133 atom. \rightarrow defined in 1967.

-273.15°C is that temperature at which all the molecular motion in water are ceased and this is equal to 0 Kelvin.

0.01°C is called as triple point. At this stage all three states of water exist.

One Kelvin is deflection of thermocouple temperature.

$$0.01^{\circ}\text{C} \rightarrow 273.10\text{K}$$

\uparrow

$$-273.15^{\circ}\text{C} \rightarrow 0\text{K}$$

\uparrow

One mole is the amount of substance as many elementary particles as there are in 0.012 kg of carbon.

Lecture 4

16/oct/19


Suspension Galvanometer.

moving coil instruments.

Permanent magnet moving coil (PMMC)
↳ Dorsional movement

Electrical magnet moving coil (EMMC)

Galvanometer principle

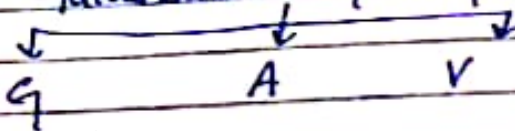

- ① Deflection torque
- ② Opposing torque (spring)

$\theta \rightarrow$ angle b/w Area and \vec{B} .
 $\phi \rightarrow$ deflection of galvanometer.

① Indicating type instruments.
Gives you display.

② Recording type instruments
Display + Recording

③ Integrating type instruments
Display + Recording + Cumulative addition

④ Null type instrument
eg wheatstone bridge

$$\vec{F} = \vec{I} L \times \vec{B}$$

1. Deflecting Torque

$$T_d \propto I, \quad T_{sp} \propto N$$

$$T_d \propto NI \varphi$$

$$T_d = BAN I$$

$$B = \frac{\varphi}{A}$$

$$\rightarrow T_d \propto I$$

deflecting torque is only dependent on current.
In order to control / stop pointer at some point we need controlling torque (T_c).

2- Controlling torque

We use spiral spring

$$T = K\theta$$


When $T_d = T_c \rightarrow$ pointer stops.

$$BAN I = K\theta \Rightarrow \theta = \frac{BAN}{K} I$$

$$\theta = c I \Rightarrow \theta \propto I$$

Due to inertia, initially it doesn't stop.

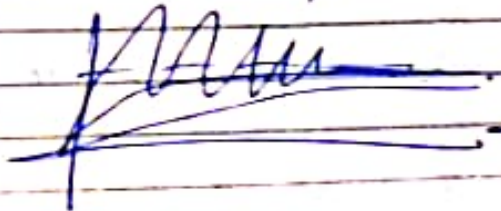oscillations \rightarrow underdamped
ideally \rightarrow critically damped
 \rightarrow we need third torque



3- Damping torque

(a) Mechanical damping: we just special bearings; but we have losses in it as we introduce friction.

(b) Electromagnetic damping: eddy current damping.

- aluminium disc - vibration changes magnetic flux - produces eddy current - direction opposite to its cause (Lenz's law)

cc) Critical damping resistances.


Temperature also affects galvanometers

Lecture 5

22/10/19

DC voltmeter (G) 0 to I_{fsd} ↓
(V) 0 to V

G has very small resistance

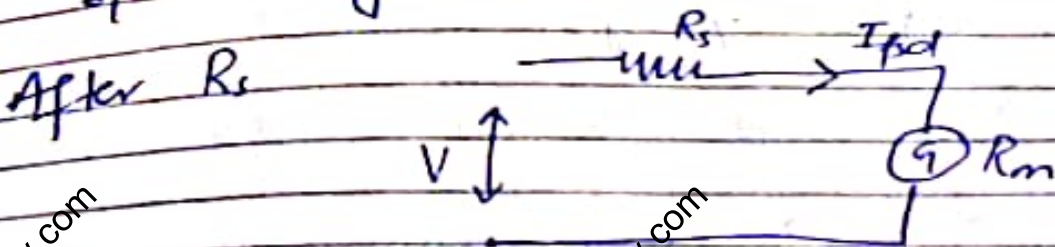


R_s is also known as multiplier.

KVL $\Rightarrow V = I_{fsd} (R_m + R_s)$


$$\frac{V}{I_{fsd}} = R_m + R_s$$

Multirange voltmeters have more than 1 series resistance.

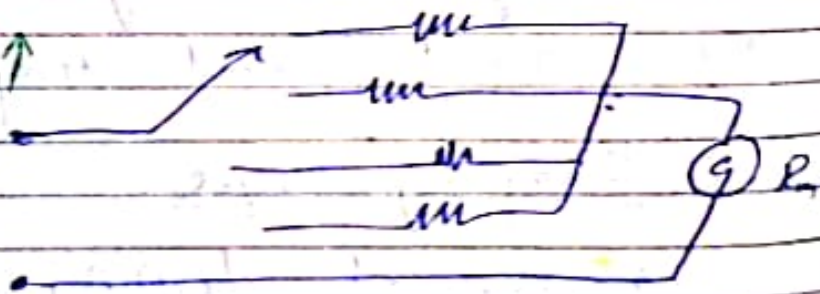$R_s \uparrow$ Range of voltmeter \uparrow



more practical \downarrow

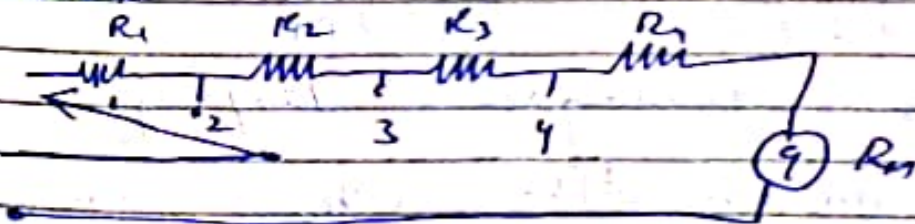

In first case we need all 4 resistors while in second case we need any 3 resistors
 → R_f should be of high quality

Ex 4.3

rating of the voltmeter

voltmeter sensitivity

$$S = \frac{R_f}{V_{fsd}}$$

$R_f \rightarrow$ total resistance of voltmeter (internal + series)

As $V_{fsd} = I_{fsd} (R_s + R_m)$
 $\Rightarrow V_{fsd} = I_{fsd} (R_f)$

$$S = \frac{R_f}{V_{fsd}} = \frac{1}{I_{fsd}}$$

It depends on full scale deflection of galvanometer.

$$S \times V = R_s + R_m$$

$$R_s = (S \times V) - R_m$$


\rightarrow in terms of series range of voltmeter

↓ Loading effect

Lecture 6

30/10/19

Shunt Type ohmmeter

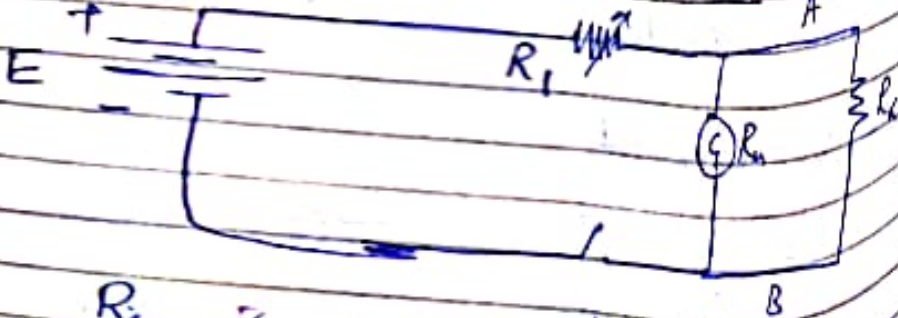

R_1 is current limiting resistor. Switch = open \rightarrow current will not flow from battery.

→ Switch increases battery life.

Case 1 $R_x = 0 \Rightarrow$ A and B = short
Switch closed \rightarrow no current through galvanometer
 \rightarrow no deflection \rightarrow that point marked as 0Ω .

Case 2 $R_x = \infty \Rightarrow$ A and B = open \Rightarrow all current will flow through galvanometer and deflection may be full scale or $1/2$ or 0 and fsd
So varying R_1 i.e. decreasing R_1 so that galvanometer give full scale deflection.
And then don't change R_1 and mark that point $\propto \Omega$.

Case 3 $R_x =$ some standard value

$$\text{let } R_x = 50 \Omega$$
$$R_x = 100 \Omega$$

When $R_x = \infty \rightarrow I_{fsd}$ was current through galvanometer in case 2.

$$\text{so } I_{fsd} = \frac{E}{R_1 + R_m} \rightarrow (1)$$

We need value of R_1 for which galvanometer gives full scale deflection.

$$I_{fsd} R_1 + I_{fsd} R_m = E$$

$$R_1 = \frac{E}{I_{fsd}} - R_m \rightarrow (2)$$

Now connecting some unknown resistor R_x
so now I_m current will flow through galvanometer

$$I = \frac{E}{R_1 + R_m \parallel R_x} \rightarrow (3)$$

Current divider rule $I_m = I \left(\frac{R_x}{R_m + R_x} \right)$

$$I_m = \frac{E}{R_1 + \frac{R_m R_x}{R_m + R_x}} \left(\frac{R_x}{R_m + R_x} \right)$$

$$\rightarrow I_m = \frac{E R_x}{R_1 R_m + R_1 R_x + R_m R_x} \rightarrow (4)$$

Divide (4) by (1)

$$\frac{I_m}{I_{fsd}} = \frac{E R_x}{R_1 R_m + R_1 R_x + R_m R_x} \times \frac{R_1 + R_m}{E}$$

$$\frac{I_m}{I_{fsd}} = \frac{R_x (R_1 + R_m)}{R_x (R_1 + R_m) + R_1 R_m}$$

$$\frac{I_m}{I_{fsd}} = \frac{R_x}{R_x + \frac{R_1 R_m}{R_1 + R_m}} \rightarrow \text{By dividing num and denom by } R_1 + R_m$$

$$\rightarrow \frac{I_m}{I_{fsd}} = \frac{R_x}{R_x + R_p} \rightarrow (5)$$

Using this eq we can calibrate end as resistance is non linear so scale will be non uniform.

- How to differ by a short type diameter
 → using mid scale point.

A and B → $R_x = R_h$ so G will give half scale deflection i.e. if

$$I_m = \frac{I_{fsd}}{2}$$

Using (5) we can find R_x


$$R_x = R_h$$

$$I_m = \frac{I_{fsd}}{2}$$

$$\textcircled{5} \Rightarrow \frac{0.5 I_{fsd}}{I_{fsd}} = \frac{R_h}{R_h + R_p} \Rightarrow 0.5 = \frac{R_h}{R_h + R_p}$$

$$\Rightarrow R_h = R_p = \frac{R_m R_l}{R_m + R_l} = \text{internal resistance.}$$

Ex 4-8

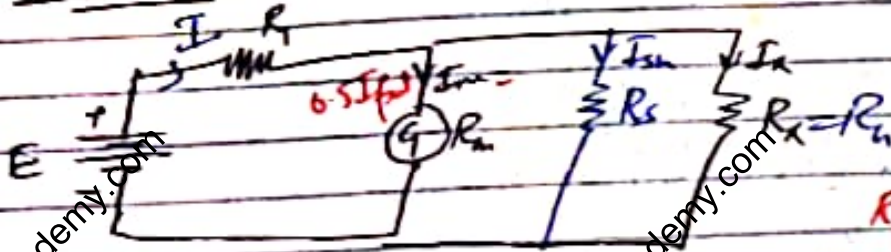

$$I_{fsd} = 10 \text{ mA}$$

$$R_m = 5 \Omega$$

$$E = 3 \text{ V}$$

In shunt type R_1 will always be relative greater than R_m .

Modify the circuit by connecting an appropriate resistance or shunt resistance across galvanometer such that new R_{sh} should be such that it will point of scale we have 0.5Ω .
ie $R_h = 0.5 \Omega$ after modification.


(i) $R_{sh} = ?$, (ii) $R_1 = ?$

(i) $R_x = R_h$ so meter will give half scale deflection so $I_m = \frac{I_{fsd}}{2} = 5 \text{ mA}$

$$E_m = I_m R_m = 5 \text{ mA} (5 \Omega) = 25 \text{ mV}$$

$$\text{Find } I_x \text{ ie } I_x = \frac{E_m}{R_h} = \frac{25 \text{ mV}}{0.5}$$

$$\Rightarrow I_x = 50 \text{ mA}$$

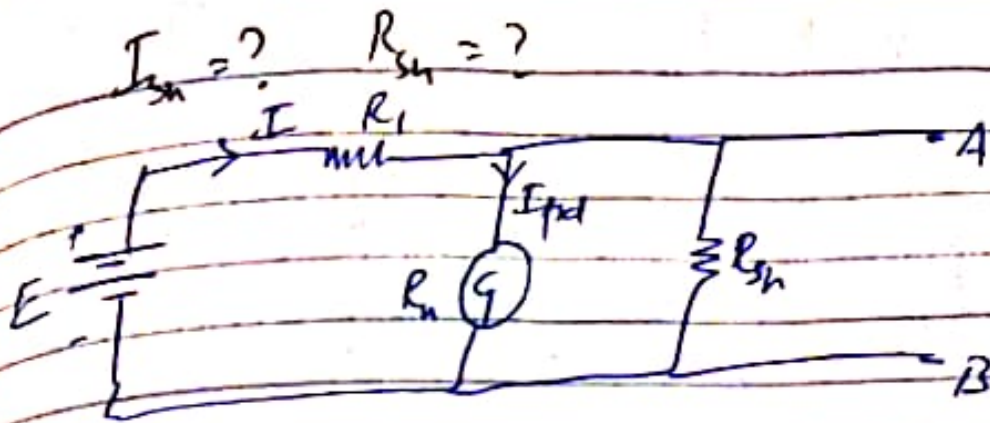

In both figures battery current is almost same because resistance of A and B is almost negligible.

In fig 2 current in meter became double as fig 1. also I_{sh} is doubled.

fig 1

$$I_{sh} = I_x - I_m$$

$$I_{sh} = 50 - 5 = 45 \text{ mA}$$

$$R_{sh} = \frac{E_m}{I_{sh}} = \frac{25 \text{ mV}}{45 \text{ mA}} \Rightarrow R_{sh} = \frac{5}{9} \Omega$$

(b) $I = I_m + I_{sh} + I_x = 5 + 45 + 50$
 $I = 100 \text{ mA}$

10V $E = E_1 + E_m$

$$E_1 = E - E_m = 3 - 25 \times 10^{-3}$$



$$E_1 = 2.975 \text{ V}$$

$$E_1 = I R_1$$

$$\Rightarrow R_1 = \frac{E_1}{I} = \frac{2.975}{100 \times 10^{-3}} = 29.75 \Omega$$

Multimeter or VOM:


4.21

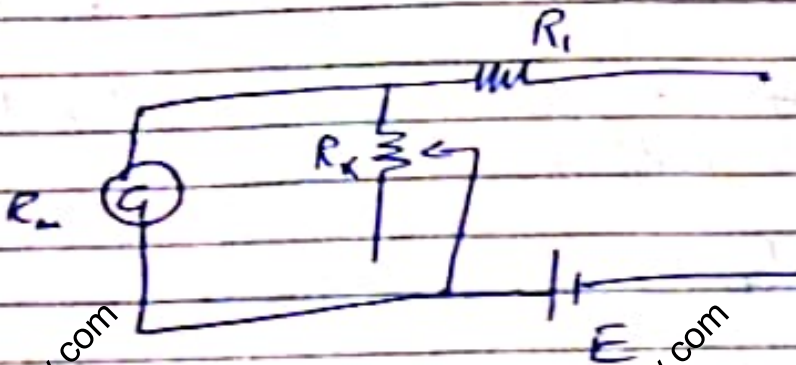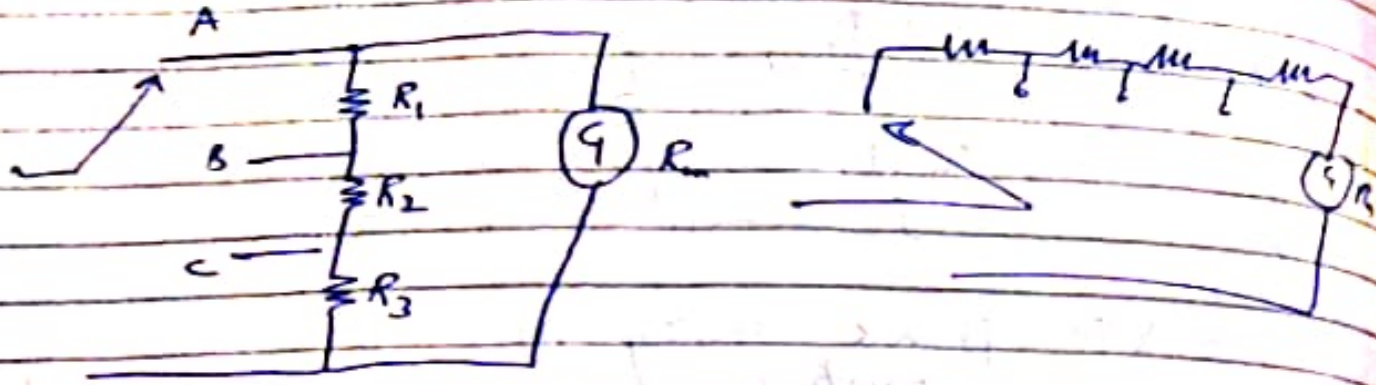

Calibration of DC instrument

One instrument that can be used for calibration is potentiometer.

Potentiometer is a null type device.

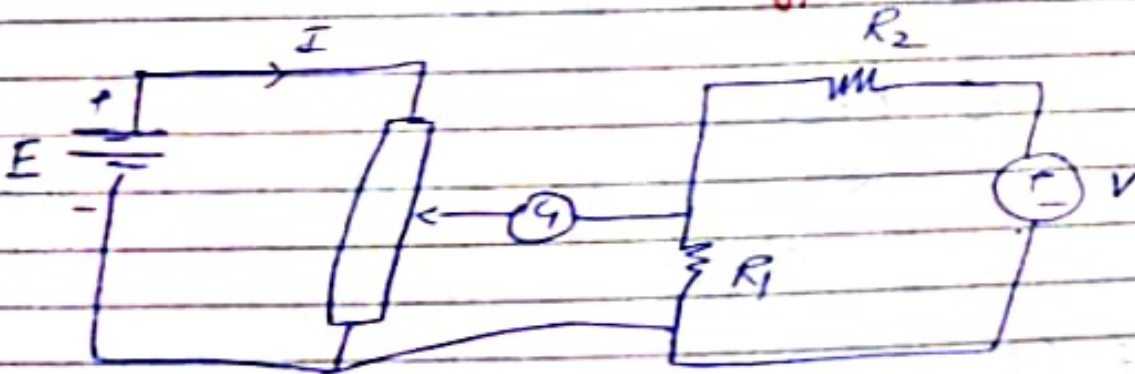

$$R_{total} = \frac{\rho L}{A}, \quad R_1 = \frac{\rho L_1}{A}$$

$$E = I R_{total}, \quad E_1 = I R_1$$


$$E = I \frac{\rho L}{A}, \quad E_1 = I \frac{\rho L_1}{A}$$

$$\frac{E_1}{E} = \frac{L_1}{L}$$

→

$$E_1 = \frac{L_1}{L} E$$

Calibration of DC Ammeter

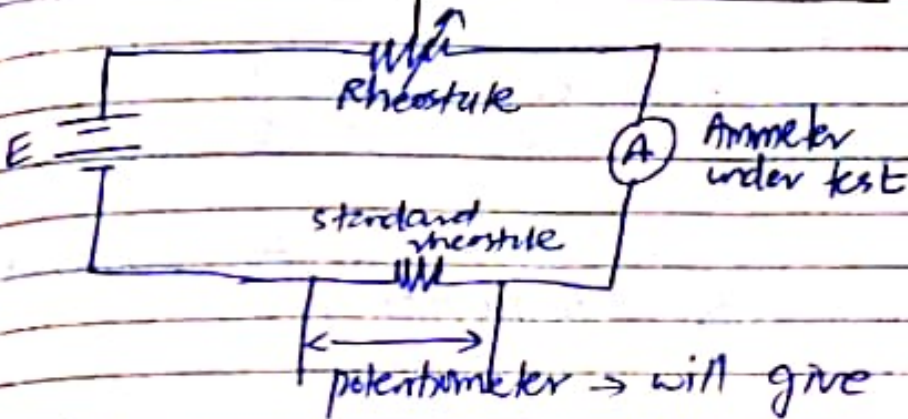


potentiometer → will give voltage.

$$I = V/R$$

— Find different current values for different rheostat values and make the scale.

Calibration of Voltmeter

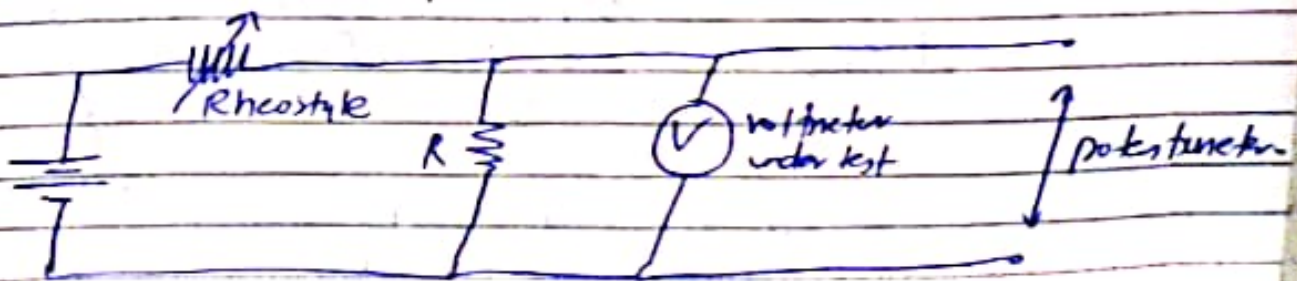

Alternating Current Indicating Instrument


$$T \propto I$$

Pointers also have some inertia.

AC A

$$f = 50 \text{ Hz}$$

$$T = 20 \text{ ms}$$

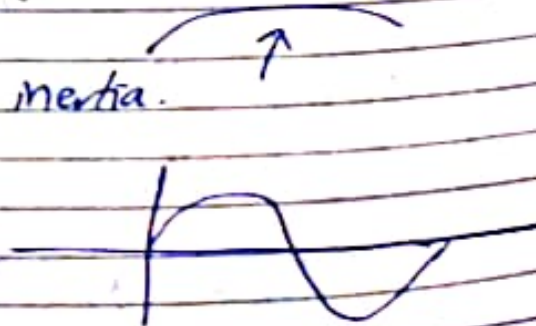

Electrodynamometer:


It can be used as AC voltmeter, AC ammeter.

We can also design power factor meter, power meter, frequency meter.

↳ It is also called transfer instrument
↳ calibration for DC is also valid for AC.

Disadvantage → can be used only for power line frequencies (low range frequencies).

Electrodynamometer Measurement:

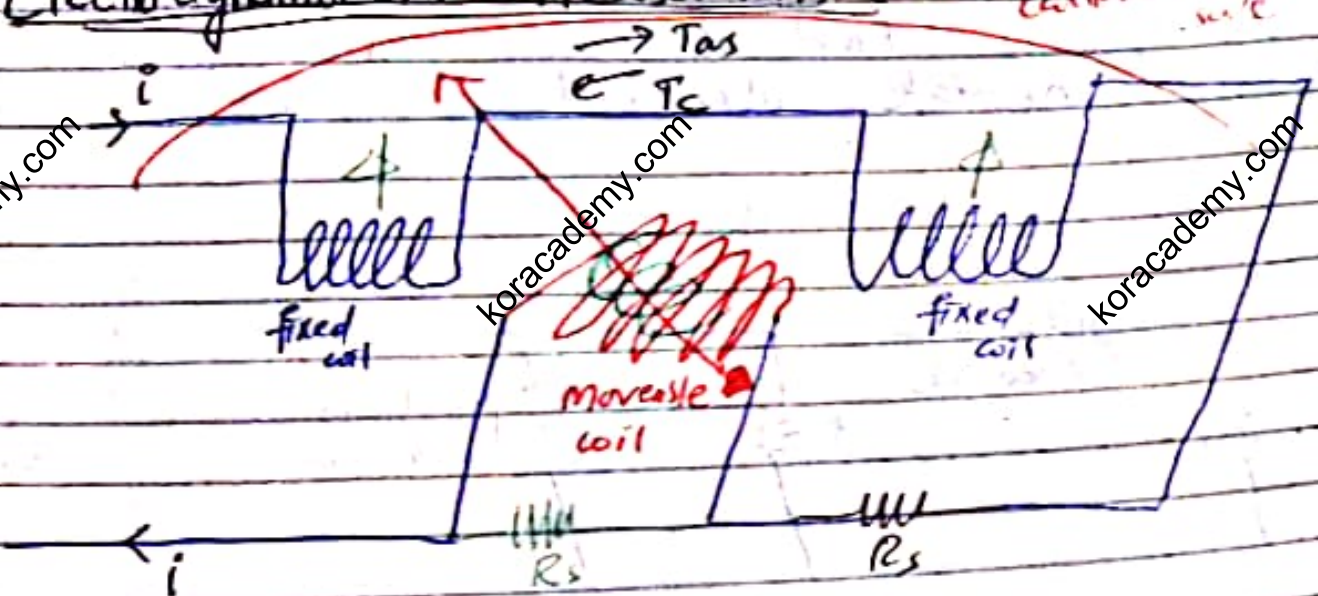

$$i \rightarrow \phi$$

$$T \propto \phi i N$$

$$T \propto \phi i$$

N is constant

$$\text{As } \phi \propto i \Rightarrow T \propto i^2$$

$$T_{inst} = K_1 i_{inst}^2$$

$$\text{instantaneous } \Rightarrow T_{inst} \propto i_{inst}^2 \quad \angle 0$$

$$T_{avg} = \text{avg} (T_{inst}) = \text{avg} (K_1 i_{inst}^2)$$

$$I_{avg} = \frac{1}{T} \int_0^T K_1 i_{inst}^2 dt$$

$$T_{ag} = k_1 \frac{1}{T} \int_0^T i_{ms} dt$$

$$I_{ms} = \sqrt{\frac{1}{T} \int_0^T i_{ms}^2 dt}$$

$$\rightarrow T_{ag} = k_1 I_{ms}$$

to make its top \rightarrow attach spring with pointer

$$T_c = k_2 \theta$$

Pointer will stop when $T_{ag} = T_c$

$$k_1 I_{ms}^2 = k_2 \theta$$

$$\rightarrow \theta = \frac{k_1}{k_2} I_{ms}^2$$

$$\rightarrow \theta = k I_{ms}^2$$

$$\rightarrow \theta \propto I_{ms}^2$$

\rightarrow deflects

Disadvantage?

- Scale is non linear as equation is non linear
- very low sensitivity.
- high power consumption

to measure up $\rightarrow R_s \rightarrow$ gears make coil conductor of coil should be more thicker.

To convert to voltmeter add R_s in series as shown

Lecture 7.

Form factor

Ex 4.9, 4.10

Thermoinstruments

Ex 1-1 117.02, 117.11, 117.09, 117.02

$$E_y = \frac{117.02 + 117.11 + 117.09 + 117.02}{4} = 117.06$$

1.2) $R_1 = 18.7 \Omega$ Range of error = Max - avg

$$117.11 - 117.06 = 0.05 \text{ V}$$

$$R_2 = 35.68 \Omega$$

$$23.06 \times 3 = 69.18 \text{ mV} < 50 \text{ mV} = 23.06$$

$$I = 3.18 \text{ A}$$

$$R = 35.68 \Omega$$

$$(3.18)(35.68) = 113.46$$

$$113.46$$

Ans 113

Ex 7-4

$$\text{Add } 826 \pm 5 + 628 \pm 3$$

$$\rightarrow 1354 \pm 8 \rightarrow \text{next int}$$

How to calculate %age error?

1.5 Subtract 628 ± 3 from 826 ± 5

1.6

1.7 Sensitivity = $1000 \Omega/V$ reads $100V$
on 150 scale
multiplic with $5mA$

$$I = \frac{V}{R} = \frac{100}{1000} = 0.1A = 100mA$$

Exercise 6:

30/10/19

Shunt type ohmmeter.

What value = Sensitivity \times full scale
 $= 1000 \times 150 = 150 \text{ k}\Omega$

$$\frac{R_1 R_V}{R_1 + R_V}$$

parallel

Voltmeter resistance = sensitivity \times full scale deflection.

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{20 \times 150}{170}$$

new value = 16.2

$$R_{eq} = \frac{40}{800 \text{ A}} = 50 \Omega$$

$$R_0 = 150 \times 1000 = 150 \text{ k}\Omega$$

$$R_2 = \frac{R_1 R_0}{R_1 + R_0}$$

$$\frac{100}{150} = \frac{150 + R_2}{150} \Rightarrow R_2 = 150 \times \frac{100}{150} - 150 = 100 - 150 = -50$$

$$R_2 = 120 - 120 = 0$$

denominator = reading = 100

$$R_2 = \frac{100 \times 150}{150 - 100} = \frac{15000}{50} = 300$$

emv = δ
 δ \rightarrow scale of δ

$$\delta = \frac{\sum d^2}{n-1}$$

0-150 voltmeter accuracy 1 percent full scale
 $V = 83V$ $100\% \times 150$ emv \rightarrow reading

likely emv = $150 \times 0.01 = 1.5V$

ist = $\frac{\delta}{FIT}$ $\frac{1.5}{83} \times 100\% = 1.81\%$

Three Things associated with a measuring device.

- ① Accuracy
- ② Precision
- ③ Sensitivity

\rightarrow closeness with the value

②

let i/p is $F = 10V$

i/p	instab	Readings again and again			
1	9	8	7	6	
2	9	9	2	3	
3	9	7	5	4	
4	7	7	7	7	\rightarrow precise
5	5	6	7	9	


Precise \rightarrow o/p is reproduced
 \rightarrow almost same o/p's

Precision is at the expense of accuracy.

ST

Accuracy is the precision of precision.

① Sensitivity -

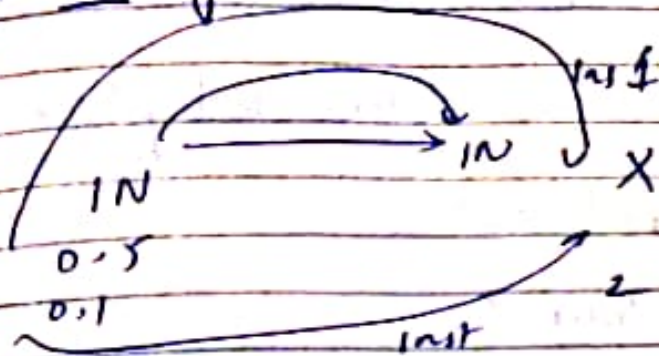

2 is more sensitive.

Responds to smaller changes in IP → more sensitive

Sensitive → to the scale for which it is designed

Resolution

Smallest change in IP that can be measured
 $\Delta I = 1 \text{ mm}$

DC Meter

will give you average value



$$\theta \propto I$$

$$\theta = KI$$

indicates the scale

of PMMC

measures DC not AC by scale is linear

AC IP → 0 OP

If $\theta \propto I^2$ → RMS measuring device.

→ An instrument is defined by the maximum current it can measure and its internal resistance.



AC meter measures both DC and AC


$\theta \propto I^2 \rightarrow$ RMS indicating device.

The scale is non linear.


eg moving iron instrument.

DC Ammeter Design

Initially the scale

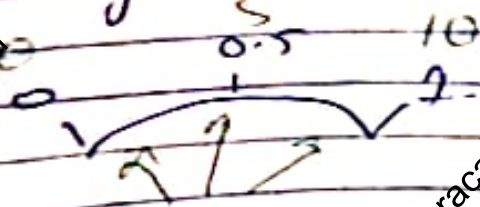

$R_s = ?$

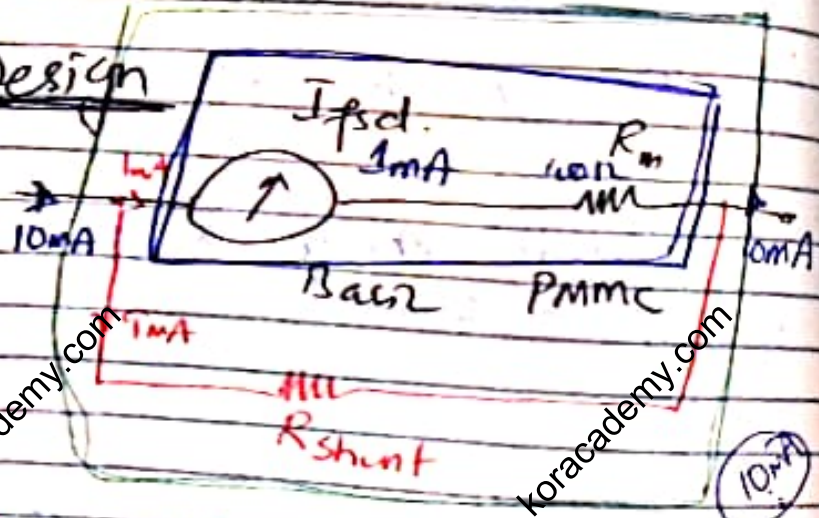

$$V_m = V_{sh}$$

$$I_m R_m = I_s R_s$$

$$\Rightarrow R_s = \frac{I_m R_m}{I_s}$$

$$1mA \times 100 = 9mA \times R_s$$

$$R_s = \frac{0.1}{9mA} = \frac{100}{9} = 11.11$$

multiplying factor / scale calibration factor = Required value / Actual value

In this case

$$\frac{10mA}{1mA} = 10$$

$$As \quad I_m R_m = I_s R_s$$



$$\frac{R_m}{R_s} = \frac{I_s}{I_m} = \frac{I - I_m}{I_m}$$

$$\frac{R_m}{R_s} = \frac{I}{I_m} - 1$$

$$\frac{R_m}{R_s} + 1 = \frac{I}{I_m} = \text{multiplying factor}$$

$$M = \frac{R_m}{R_s} + 1$$

DC Voltmeter design:

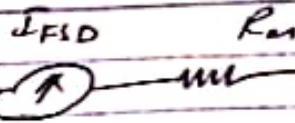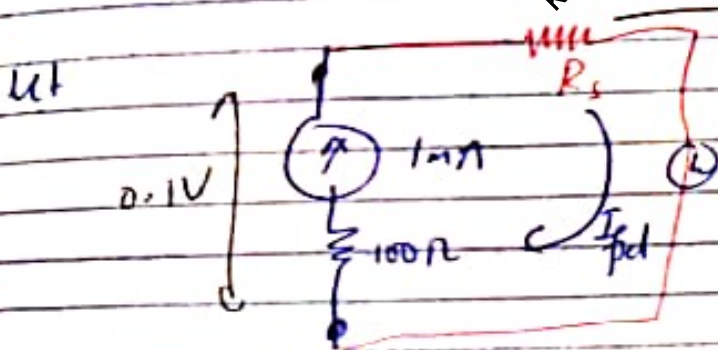

KVL

$$1 - 0.1 = I_{FSD} R_{se}$$

$$\frac{0.99}{1m} = R_{se}$$

$$\Rightarrow R_{se} = 0.99 \text{ k}\Omega$$


$$\frac{V_{FSD} - I_{FSD} R_m}{R_{se}} = I_{FSD}$$

$$V_{FSD} = R_{se} I_{FSD} + I_{FSD} R_m$$


$$V_{FSD} = [R_{se} + R_m] I_{FSD}$$

$$\text{Sensitivity} = \frac{1}{I_{FS}}$$

Loading Error:

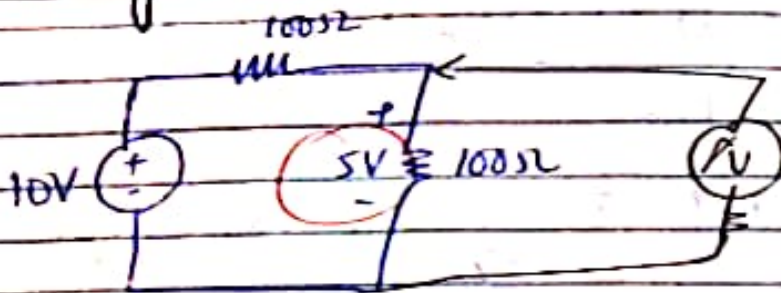


Limit of voltmeter of high S_V 100Ω

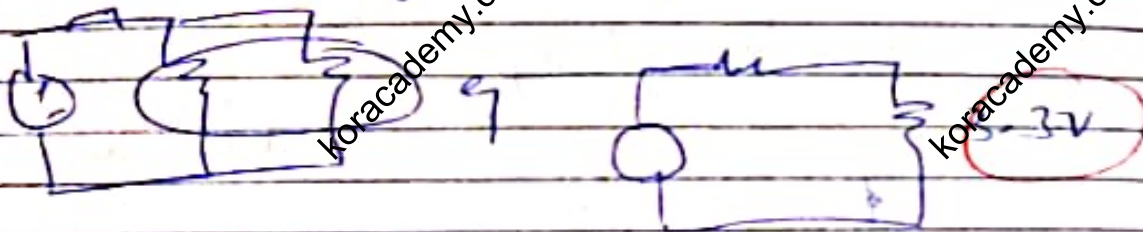

$S \rightarrow 3.3$
 \hookrightarrow loading error
 \hookrightarrow voltmeter resistance

$$L.E \downarrow \rightarrow R_V > 10 R_L$$
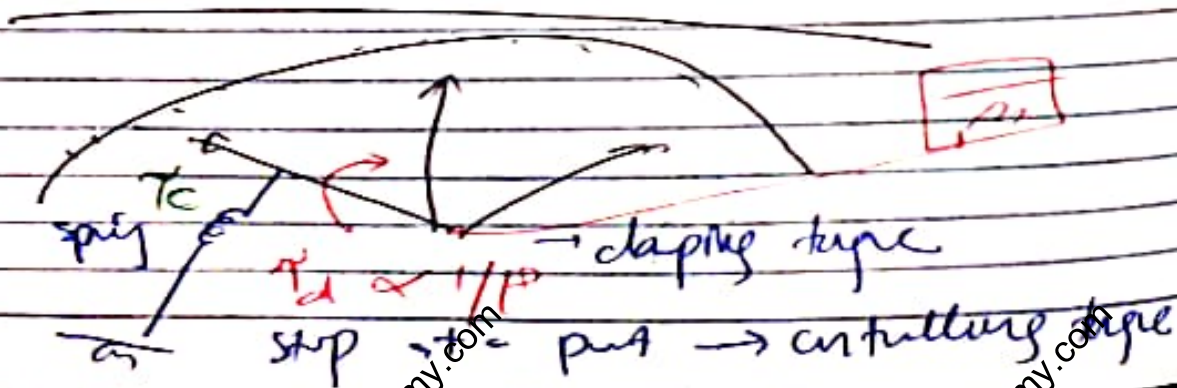
$$R_V \uparrow \rightarrow S \uparrow = \frac{S}{V}$$



$$= \gamma_c$$

gravity control is also there
 ↳ vertical motion which

damping torque?

vibration after $T_d = T_c$
 ↳ to stop piston → an damped
 ↳ equal damped
 ↳ eddy current damping → when there is high magnetic field

000, 000, 000, 000, 000

143, 010, 120, 009, 018

Addition 3 150.0 1
 0.702 3

$$\frac{4.51}{3} \times 100 \frac{T_n}{s}$$

$$= 7.51$$

$$\text{err} = 2m - 2f$$

$$\% \text{err} = \frac{2m - 2f}{2f} \times 100$$

$$n = 8$$


5, 3, 2

$$\frac{5+3+2}{3}$$

Probab err = 0.6745 σ

FINAL

Lecture 4

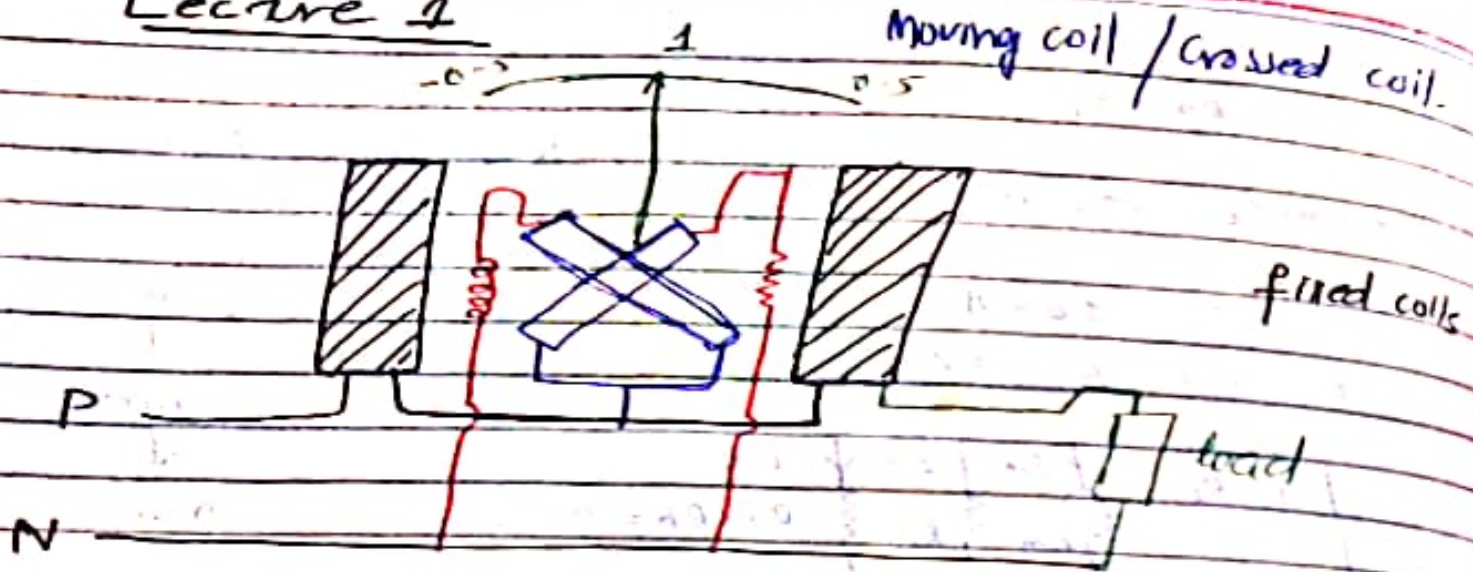


Watt hour reading meter

↳ unit of energy

kilowatt hour = Units.

Single Phase Induction Type Energy Meter

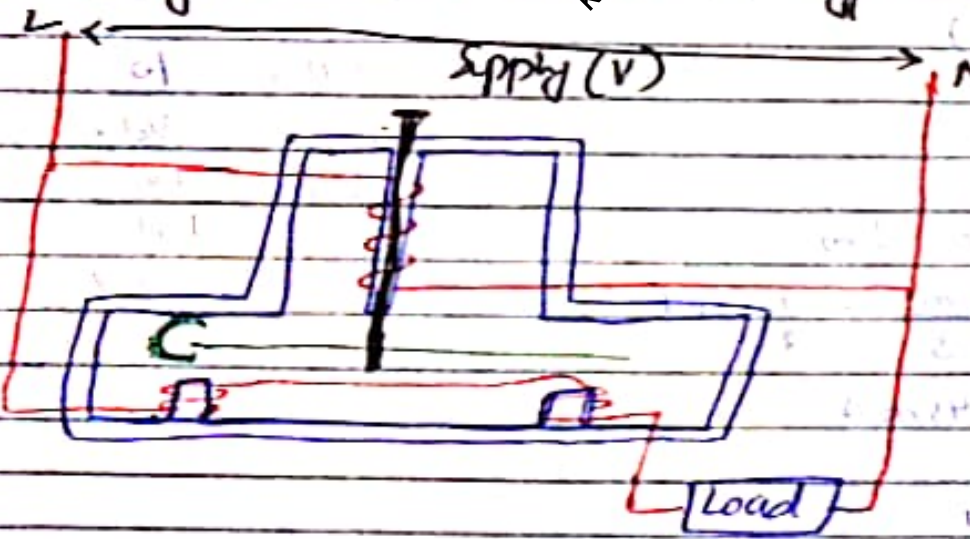

is an integrating type instrument
↳ (i) driving
(ii) braking
(iii) cumulative addition

- 4 main parts.
- i) Driving system
↳ voltage coil, current coil and the core.
↳ has to produce driving torque.

Eddy current

ii) Moving System

↳ Disk, shaft and bearings

iii) Braking System

Basically U shaped permanent magnet.

iv) Registering / Counting system
made from gears

Working.

Voltage coil \rightarrow highly inductive


I_2 lags V by 90°

Flux ϕ_2 produces. $\phi_2 \propto I_2$

Flux is always in phase with its current.

Induced emf E_{e2} lags ϕ_2 by 90°

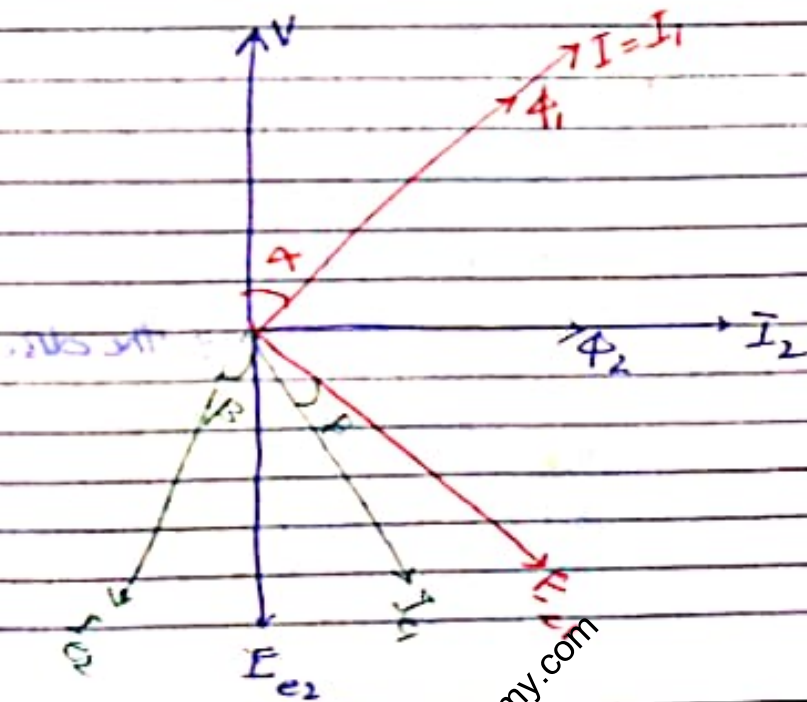I_{e2} lags $E_{e2} \rightarrow$ by angle? \rightarrow depends on μ and r of the disc.



I_1 and T_2 are opposite in direction

$$T_{\text{inst}} \propto VI \quad T_{\text{avg}} \propto P$$

$$T_{\text{inst}} \propto I_1 \phi_2$$

$$T_1 \propto I_1 \phi_2 \cos(\alpha + \beta)$$

$$T_2 \propto I_2 \phi_1 \cos(180^\circ - \alpha + \beta)$$

$$T_d = T_1 - T_2$$

$$T_d \propto I_1 \phi_2 \cos(\alpha + \beta) - I_2 \phi_1 \cos(180^\circ - \alpha + \beta)$$

$$T_d \propto IV \cos(\alpha + \beta) - VI \cos(180^\circ - \alpha + \beta)$$

$$T_d = K_1 VI [\cos(\alpha + \beta) - \cos(180^\circ - \alpha + \beta)]$$

↓

$$K_1 \cos(\alpha + \beta) = \cos \alpha \cos \beta - \sin \alpha \sin \beta$$

$$T_d = 2K_1 VI \cos \alpha \cdot \cos \beta$$

$$2K_1 \cos \beta = K_2$$

$$T_d = K_2 VI \cos \alpha$$

$$\boxed{T_d = K_2 P}$$

viva

Breaking torque.

$T_b \propto n$ speed of disc.

$$T_b = K_3 n$$

Point of action of these two torques are different.

$T_b = T_d \rightarrow$ disc will rotate with uniform speed.

$$K_3 n E = K_2 P E$$

$$K_3 N = K_2 E$$

$N \rightarrow$ no. of revolutions

$E \rightarrow$ energy

$$N = \frac{K_2}{K_3} E \Rightarrow N = K E$$

$$N \propto E$$

$$K = \frac{N}{E} = \left(\frac{\text{rev}}{\text{KW/Hour}} \right)$$

\rightarrow meter constant.


Lecture 2

04/12/19

Wheats tone Bridge

G has $S = 10 \text{mm}/4A$

Ex 5.1

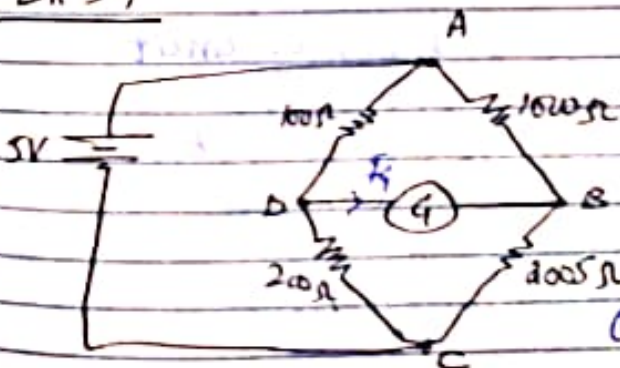


Internal resistor of G, $R_{in} = 100\Omega$

Deflection $D = ?$

Solving by thevenin eq circuit.

ⓐ Same as element.

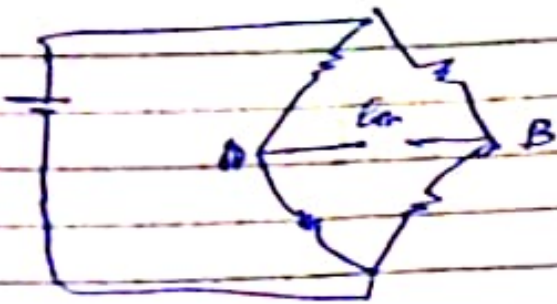


$$E_{Th} = E_B - E_D$$


$$E_{Th} = 5 \times \frac{2005}{1000 + 2005} - 5 \times \frac{2000}{1000 + 2000}$$

$$E_{Th} = 2.77 \text{ mV}$$

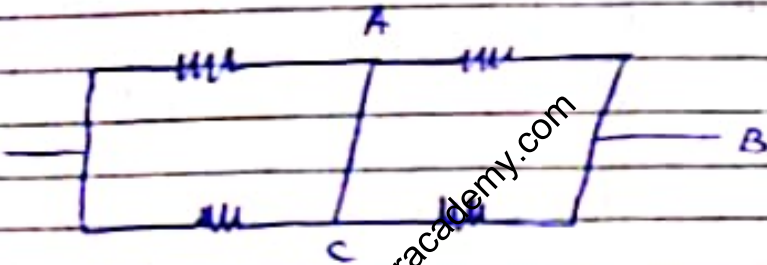② Find R_{Th} . open circuit resistance.
For R_{Th} make all sources zero first.




or can be redrawn as:

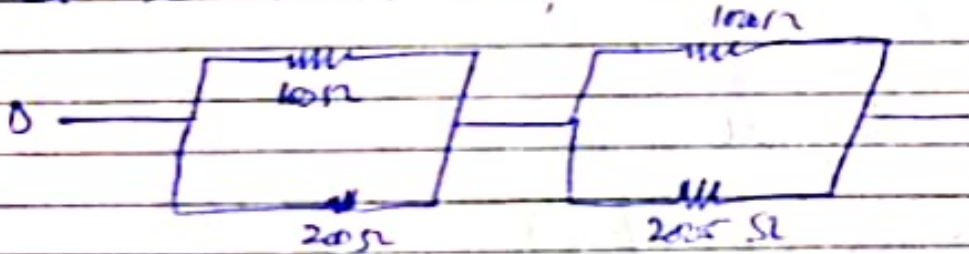

$$R_{Th} = 100 // 200 + 1000 // 2005$$

$$\Rightarrow R_{Th} = 734 \Omega$$

③ Design of circuit

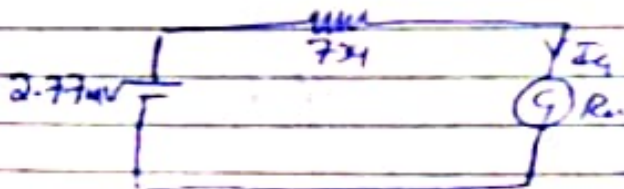

$$I_g = \frac{E_{Th}}{R_{Th} + R_L}$$


$$I_g = 3.32 \mu A$$

$$= \frac{2.77 \times 10^{-3}}{734 + 1000}$$

$$D = I_g \lambda_s = 332 \text{ } \mu\text{m}$$

$$\Rightarrow D = 332 \text{ mm}$$

Effects of connecting leads

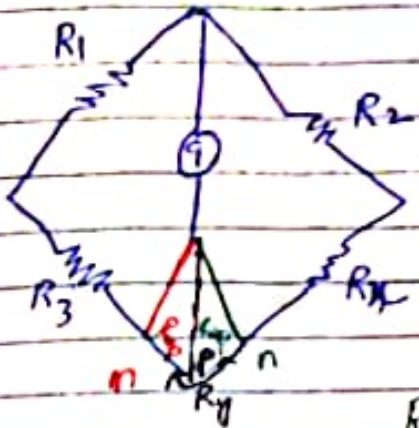

$$R_1 (R_3 + R_y) = R_2 R_3$$

$$R_1 R_x = R_2 (R_3 + R_y)$$

If connected to point P.

$$R_1 (R_3 + R_{np}) = R_2 (R_3 + R_{np})$$

$$R_1 R_x + R_1 R_{np} = R_2 R_3 + R_2 R_{np}$$


$$R_1 R_x = R_2 R_3 + R_2 R_{np} - R_1 R_{np} \rightarrow \text{ⓐ}$$

$$\frac{R_{np}}{R_{ap}} = \frac{R_1}{R_2}$$

$$R_2 R_{np} = R_1 R_{ap}$$

$$R_1 R_x = R_2 R_3$$

Kelvin Bridge

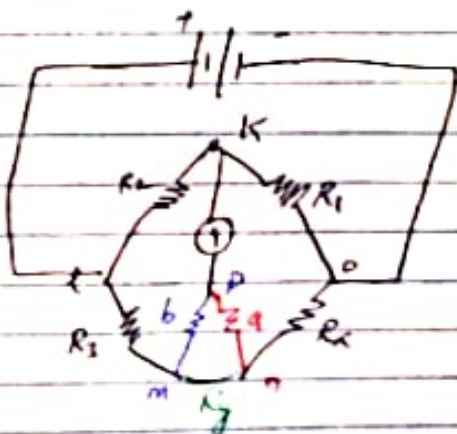

$$\frac{a}{b} = \frac{R_1}{R_2} \rightarrow \text{ⓐ}$$


Balanced

$$E_x = -E_p$$

$$E_x - E_k = E_l - E_p$$

$$E_x = E_p \rightarrow \text{ⓑ}$$

$$E_k = E_x \frac{R_2}{R_1 + R_2}$$

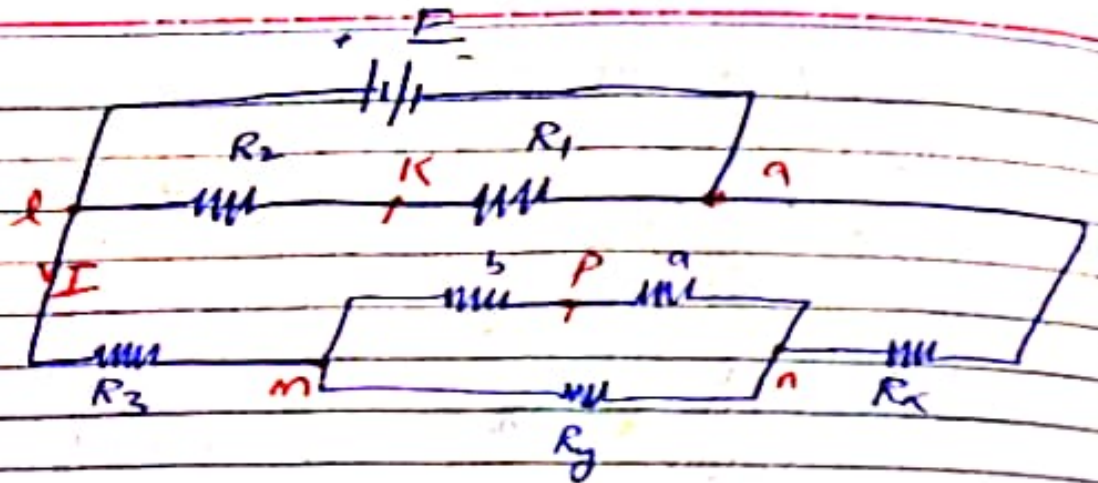

$$E = I \times (R_2 + (a+b) \parallel R_y + R_7) \rightarrow (4)$$

$$E_{\text{ext}} = \frac{R_2}{R_1 + R_2} \times I \times \left(R_2 + \frac{(a+b)R_y}{a+b+R_y} + R_7 \right) \rightarrow (5)$$

E_{ep}

$$E_{\text{ep}} = IR_3 + E_{\text{mp}} \rightarrow (6)$$

$$E_{\text{mp}} = E_{\text{mn}} \times \frac{b}{a+b} \rightarrow (7)$$

$$E_{\text{mn}} = I \times \left((a+b) \parallel R_y \right) \rightarrow (8)$$

$$E_{\text{mp}} = I \times \frac{(a+b)R_y}{a+b+R_y} \times \frac{b}{a+b}$$

$$E_{\text{mp}} = I \times \frac{bR_y}{a+b+R_y} \rightarrow (9)$$

$$(9) \text{ in } (6) \quad E_{\text{ep}} = I \left(R_3 + \frac{bR_y}{a+b+R_y} \right) \rightarrow (10)$$

⑤ and ⑥ in ②

$$\Rightarrow \frac{R_2}{R_1 + R_2} \times I \times \left(R_3 + \frac{(a+b)R_y}{a+b+R_y} + R_x \right) =$$

$$I \left(R_3 + \frac{bR_y}{a+b+R_y} \right)$$

$$\Rightarrow R_3 + \frac{aR_y}{a+b+R_y} + \frac{bR_y}{a+b+R_y} + R_x = \left(\frac{R_1 + R_2}{R_2} \right) \left(R_3 + \frac{bR_y}{a+b+R_y} \right)$$

$$\Rightarrow R_3 + \frac{aR_y}{a+b+R_y} + \frac{bR_y}{a+b+R_y} + R_x = \frac{R_1 R_3}{R_2} + \frac{R_1 bR_y}{R_2 (a+b+R_y)} + R_3 + \frac{bR_y}{a+b+R_y}$$

$$\Rightarrow R_x = \frac{R_1 R_3}{R_2} + \frac{bR_y}{a+b+R_y} - \frac{a b R_y}{b(a+b+R_y)}$$

$$R_x = \frac{R_1 R_3}{R_2} + \frac{bR_y}{a+b+R_y} \left(\frac{R_1}{R_2} - \frac{a}{b} \right)$$

$$\Rightarrow \boxed{R_x = \frac{R_1 R_3}{R_2}}$$

Lecture 3

11/12/19

AC Bridge applications

" SMC \rightarrow AC


\rightarrow Power line frequency 50 - 60 Hz
 \rightarrow RF = radio frequency

- 2) Detector
- Buzz
 - Headphone
 - Amplifier
 - Electrogn

4) Balanced principle for balanced condition

Impedances	z_1	z_2
	z_3	z_4

Guarded Wheatstone Bridge

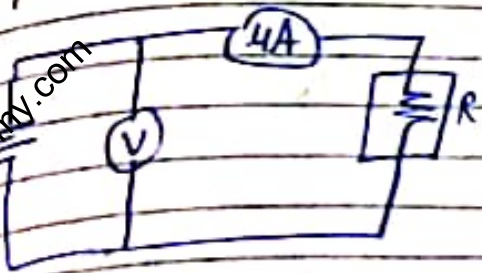

$\mathcal{E} = 2V$

$R = \frac{\mathcal{E}}{I}$



$z_1 + z_2$



$\frac{z_1 z_2}{z_1 + z_2}$



$\frac{y_1 y_2}{y_1 + y_2}$



$y_1 + y_2$

$z = R + jX$

R → resistance X → reactance

$X_L = j\omega L$

$X_C = \frac{-j}{\omega C}$

$y = G + jB$

$G = \text{conductance} = 1/R$

$B = \text{susceptance}$

$= \frac{1}{Z}$

$$\text{---} B = +j\omega C$$

$$\text{---} B = -j/\omega L$$

Lecture 4

18/12/19

Schering Bridge

Wein Bridge

Wagner ground connection

bridge \rightarrow true coming
by step

Problem Sol

$$f = 1 \text{ KHz}$$

$$AB: C_1 = 0.24 \mu\text{F} \quad BC: R_2 = 500 \Omega$$


CD: unknown

$$DA: R_3 = 300 \Omega \parallel C_3 = 0.14 \mu\text{F}$$

CD: R and C or L

connected in series.

Balanced bridge.

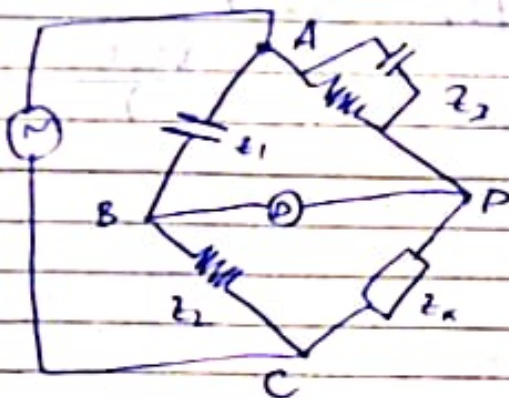

Balanced so $z_1 z_x = z_2 z_3$

$$z_x = \frac{z_2 z_3}{z_1} = \frac{z_2}{z_1} z_3$$

$$Z_1 = \frac{-j}{2\pi f C_1} = \frac{-j}{2\pi (1000)(0.2 \times 10^{-6})} = -j 795.8 \Omega$$

$$Z_2 = R_2 = 500 \Omega$$

$$Y_3 = \frac{1}{R_3} + j2\pi f C_3 = \frac{1}{360} + j2\pi (1000)(0.1 \times 10^{-6})$$

$$Y_3 = (3.33 \times 10^{-3} + j 628.32 \times 10^{-6}) \text{ S}$$

$$\Rightarrow Z_x = \frac{500}{(-j 795.8)(3.33 \times 10^{-3} + j 628.32 \times 10^{-6})}$$

$$\Rightarrow Z_x = (34.4 + j 182.2) \Omega$$

+j → inductive
-j → capacitive


$$Z_x = R_x + j\omega L_x$$

$$R_x = 34.4 \Omega$$

$$2\pi f L_x = 182.2$$

$$L_x = \frac{182.2}{2\pi (1000)} = 29 \text{ mH}$$

If in parallel;

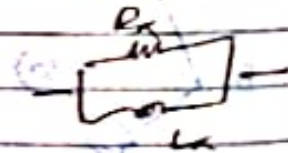

$$Y_x = \frac{1}{Z_x}$$

$$Y_x = G_x - jB_x$$

$$Y_x = \frac{1}{R_x} - \frac{j}{2\pi f L_x}$$

Lecture 5

CT, PT

Lecture 6

24/12/19

Oscilloscope.

Lab 12

To learn the construction and working of

D.S.O.

Lecture 7

01/01/20

Transducer

Lecture 8

08/01/20

Digital Multimeter.

We will measure

- (i) AC voltage (ii) DC voltage (iii) AC current
(iv) DC current (v) Resistance.


Principle? we will convert unknown quantity (except DC voltage) into an equivalent DC voltage \rightarrow then we will measure that DC voltage \rightarrow And then we will calibrate to find the unknown quantities.

V_m AC voltage $V \dots$ DC voltage

A_m AC current $A \dots$ DC current

Ω Resistance.

Block diagram

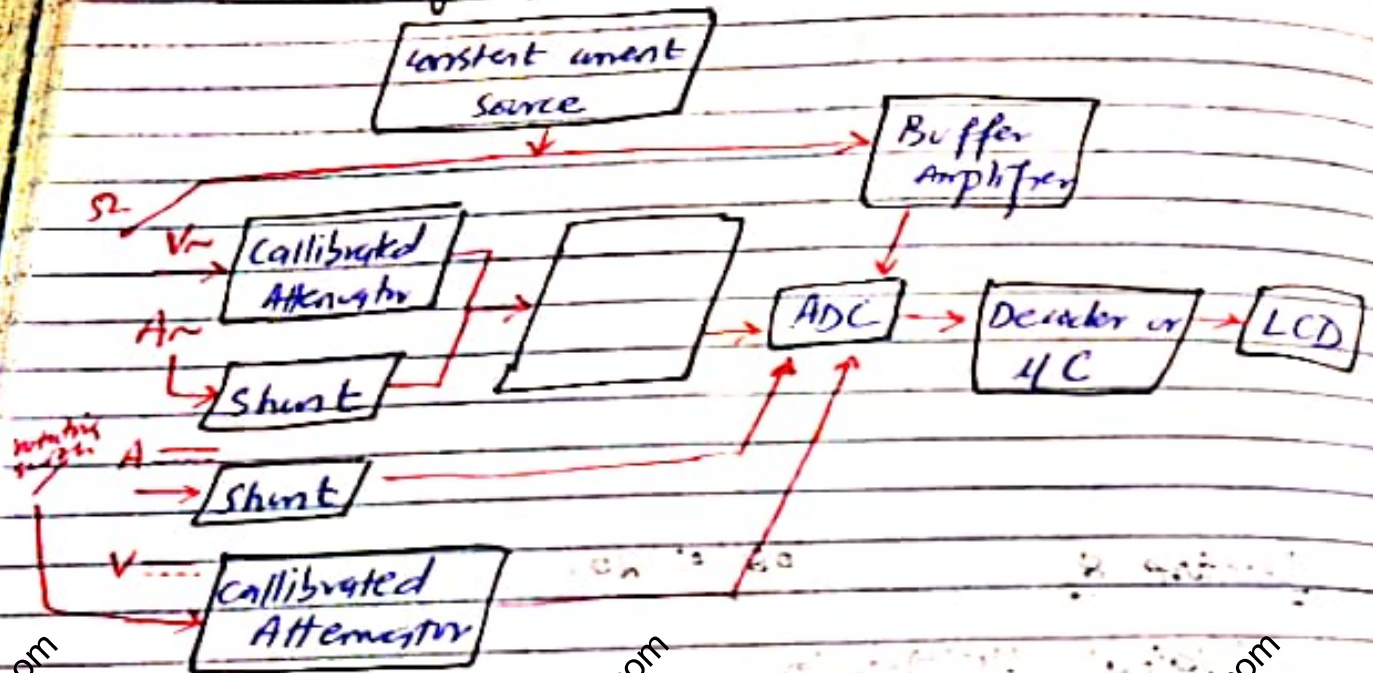


DC voltage measurement

i/p may be very high so we use callibrated attenuator (series resistance) so we connect very high resistance in series to galvanometer ($k\Omega, m\Omega$)

let i/p voltage is 5V.

+ attenuator 100 times = 5mV

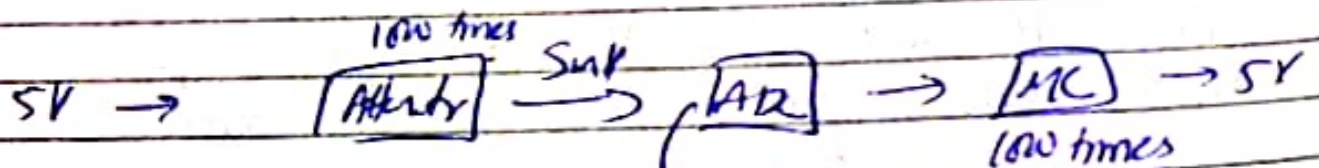


let

1mV	100100
2mV	01011
1	
5mV	01010


~~AC voltage~~ if in nano Volts then capacitor is used.

AC voltage Measurement

rotating switch V_m

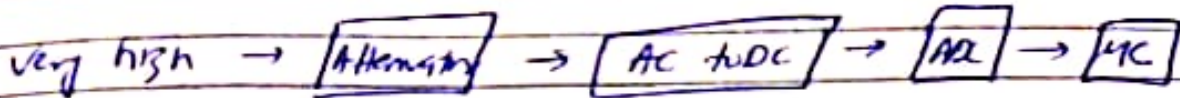

DC current

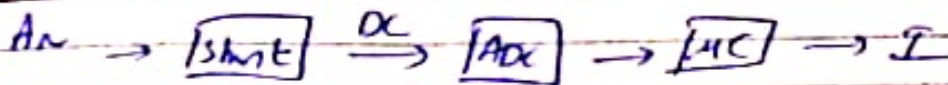


we use R in parallel to galvanometer to convert to ammeter.

$$I_{sh} \approx I$$

$$V_{sh} = I_{sh} R_{sh}$$


$$V_{sh} \propto I_{sh}$$

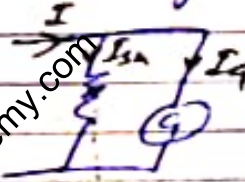

R_{sh} is very low so V_{sh} is low so no need of attenuator.

$$I = \frac{V_{sh}}{R_{sh}}$$

AC current

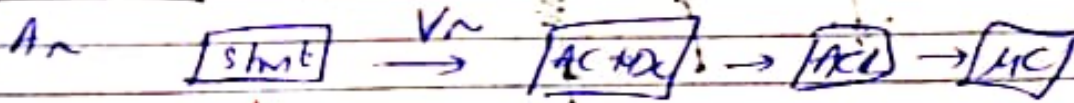


\downarrow
we may use current to voltage convert.

Resistance measurement


→ Ω

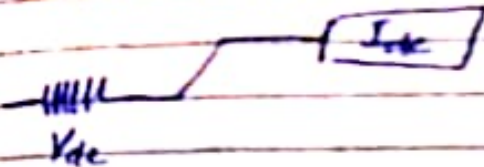constant constant same with provide DC const




→ If voltage of the source is independent of the load then it is voltage source.

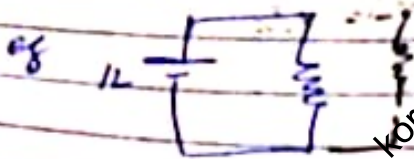→ If the current applied by the source is not changing with change in load, then it is current source.




V same

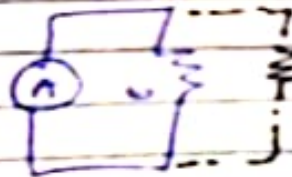

I same

Current source

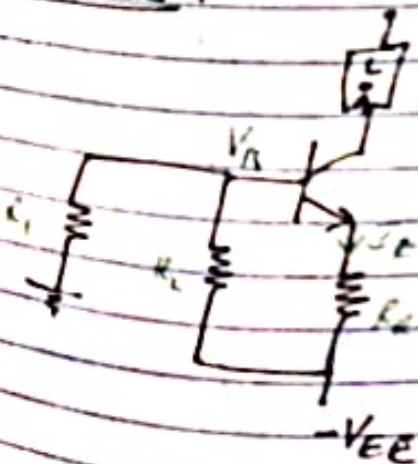

Suppose same output impedance of BJT is much larger than R_1 and R_2 .

choose R_1, R_2 such that source current is greater.

$$V_B = \frac{R_1}{R_1 + R_2} (-V_{EE})$$

$$V_{BE} = V_B - V_E = 0.7$$

$$V_E = V_B - 0.7$$


$$I_E = \frac{V_E + V_{EE}}{R_E} \approx I \quad (\text{constant})$$

other quantities are constant

Buffer Amplifier.

of amp is a three part circuit

(i) i/p (ii) o/p (iii) power

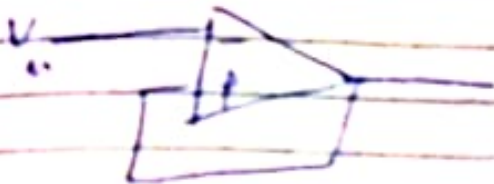

In -ve feedback

$$V^+ = V^-$$

If we connect V_{in} to ground then $V_{in} = 0$, V^- is virtual ground.

$$V^+ = V_{in}$$

$$V^+ = V_{out}$$

$$V_{in} = V_{out}$$

$$A_f = 1$$

• Impedance matching

i/p impedance almost ∞ .


o/p about 0.

• Isolation.

Isolate one part of circuit from another part


$$I_{in} = I_{out} R$$

Fibre Optic Measurement

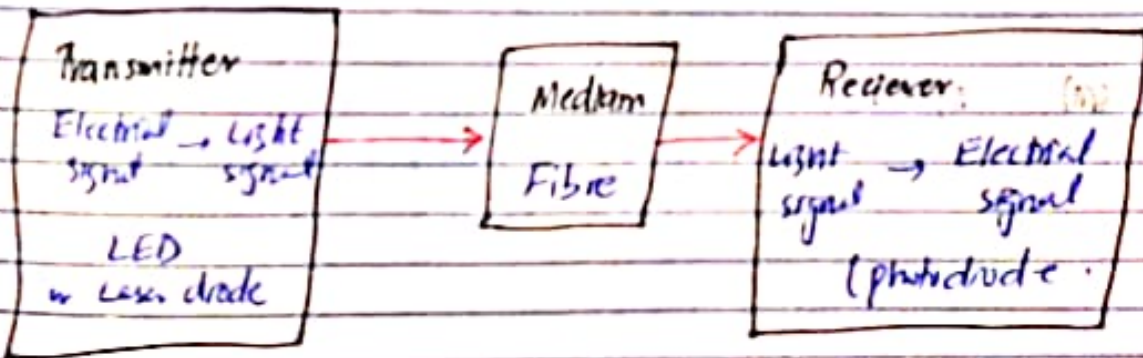

Fibre optics work on the principle of total internal reflection

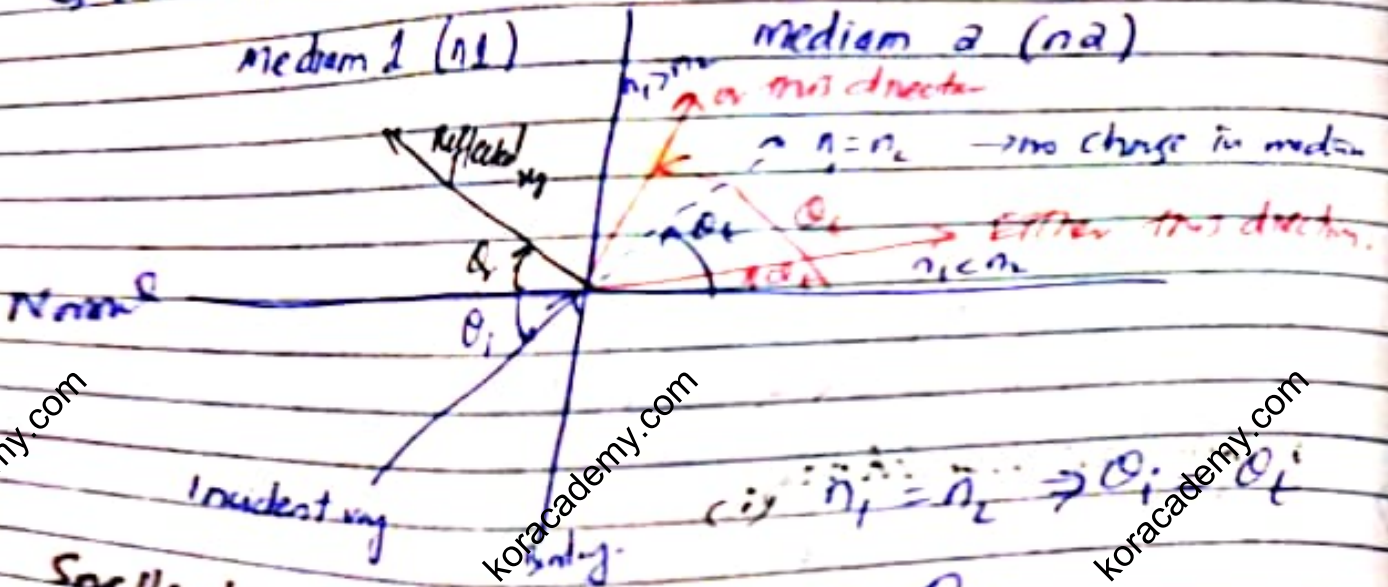$n \rightarrow$ refractive index.
 $n = 1$ for air
 For all other mediums is greater than 1.



Snells law of reflection: $\theta_i = \theta_r$

Snells law of refraction: $n_1 \sin \theta_i = n_2 \sin \theta_t$

(i)

$$n_1 > n_2$$

$$\sin \theta_i < \sin \theta_t$$

$$\theta_i < \theta_t$$

Ray bends away from the normal

$$\theta_i \uparrow \rightarrow \theta_t \uparrow$$

$$\text{when } \theta_t = 90^\circ$$

$$\text{then } \theta_i = \theta_c$$

(ii)

$$n_1 < n_2$$

$$\sin \theta_i > \sin \theta_t$$

$$\theta_i > \theta_t$$

Ray bends towards the normal

$$\text{if } \theta_i > \theta_c$$

the ray is reflected


total internal reflection

Fibre can be made of glass or plastic (polymer).

for long range communication \rightarrow glass
 short range \rightarrow plastic
 medium range \rightarrow both

Inner cylinder core $\rightarrow n_1$
 outer cylinder cladding $\rightarrow n_2$


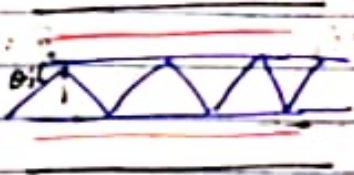
for protection \rightarrow an outer layer of coating \rightarrow Jacket



Answer to voltage with should have to filter the response.

(i) $V_{out} = K I_i$

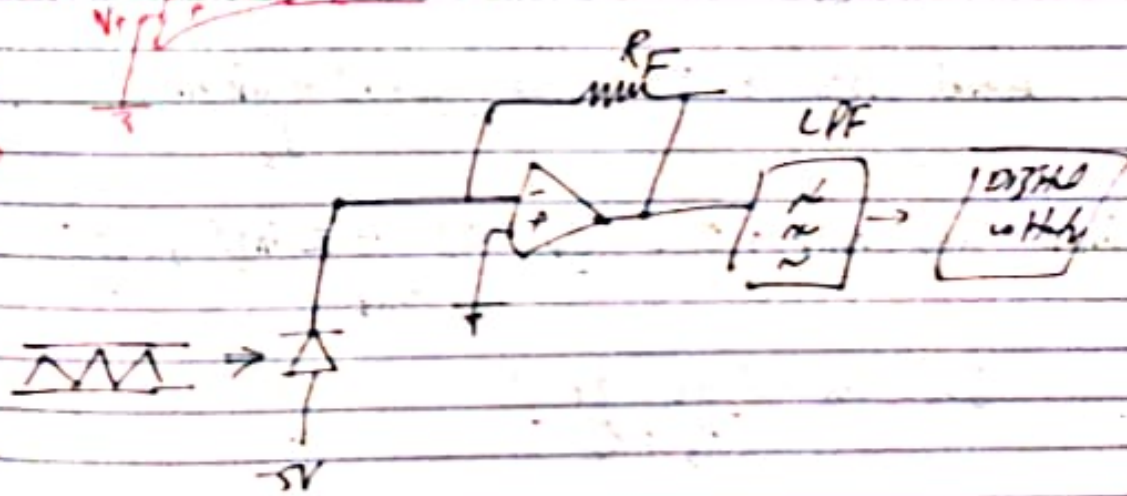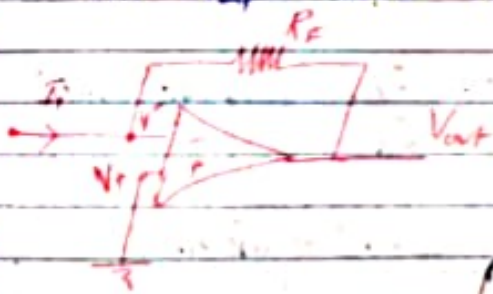(ii) V_{out} should be independent of the load.



Transformer impedance amplifier

Feedback



$$V^- = V^+ \Rightarrow I_f = I_i$$

$$0 - V_{out} = I_f R_f$$

$$\text{if } K = -R_f$$

$$V_{out} = -I_f R_f$$

$$\Rightarrow V_{out} = K I_i$$

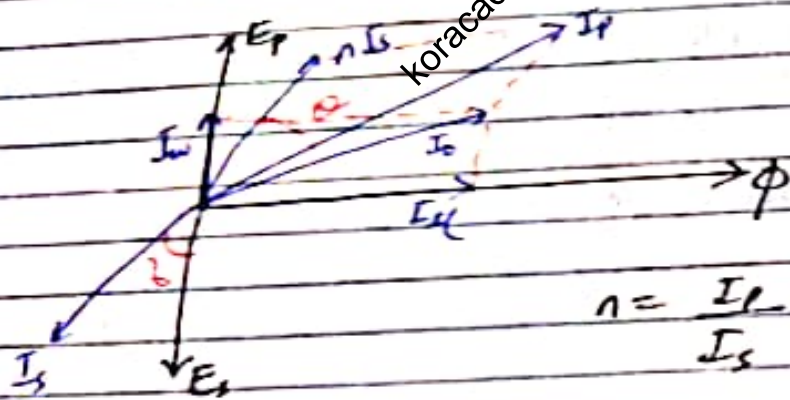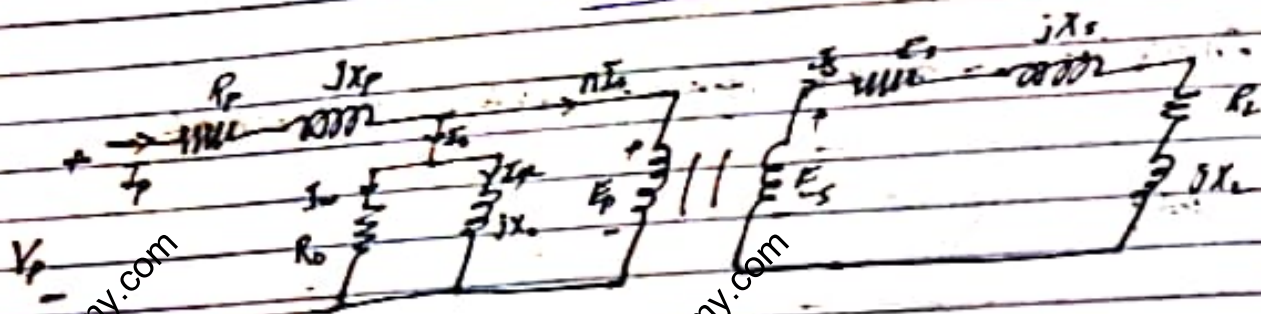

$$n = \frac{I_p}{I_s} = \text{current ratio}$$


$$\text{Actual ratio} \Rightarrow R = n + \frac{I_w \cos \phi + I_x \sin \phi}{I_s}$$

$$\text{Phase angle error} \Rightarrow \theta = \frac{I_w \cos \phi - I_x \sin \phi}{n I_s} \times \frac{180^\circ}{\pi}$$

$$\phi = \tan^{-1} \left(\frac{X_s + X_l}{R_s + R_l} \right)$$

Example: A mag. core type CT has a ratio of 200/10
 $n = 200$, when getting at a rated primary current
 with a secondary burden of 2Ω the ratio value of
 a SL: $\phi = 0^\circ$ $R_L = 2 \Omega$ $I_0 = 2 A$ $Pf = 0.3$

$I_S = 10 A$ Ratio error = ?

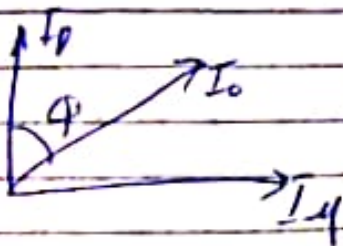

$$I_2 \cos \phi = I_0$$

$$= 2 \times 0.3$$

$$I_2 = 0.6 A$$

$$R = n + \frac{I_2}{I_S}$$

$$= 200 + \frac{0.6}{10}$$

$$\Rightarrow R = 200.06$$

$$\% \text{ R.E.} = \left| \frac{n - R}{R} \times 100 \right| = 0.03\%$$

Phase angle

$$\theta = \frac{I_2}{n I_S} \times \frac{180^\circ}{n}$$

$$\phi = \cos^{-1}(0.3) = \dots$$

$$I_0 \sin \phi = I_{21}$$

$$\theta = 0.055966^\circ$$

Actual phase angle

$$180^\circ - \theta$$

Expt. of an auto transformer. ($n_p = n_1 = 1$) $\therefore n_s = 400$

Impedance of secondary circuit: $2 + j1.5 = Z_s$ with 4 A flowing in the secondary. Magnetizing MMF is 80 A-T. at the primary loss is 1 Watt. Determine the voltage error and phase angle error.


$N_1 = 1 \rightarrow$ bar magnet $N_2 = 400$
 $Z_s = 2 + j1.5 \Omega$ $I_s = 4A$ $MMF = 80 A \cdot T$
 1 W loss = 1 W

Ratio error = ? $\phi = ?$

$$a = \frac{N_2}{N_1} = \frac{400}{1} = 400$$

$$|Z_s| = \sqrt{(1.5)^2 + (2)^2} = 2.5$$

$$\cos \phi = \frac{2}{2.5} = 0.8$$

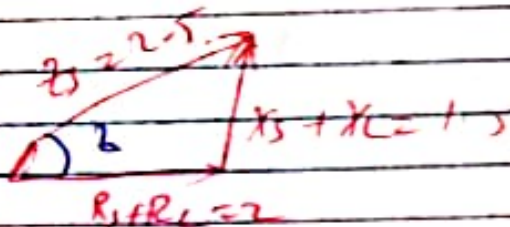

$$\sin \phi = \frac{1.5}{2.5} = 0.6$$

$$MMF = F_m N_1 \Rightarrow I_{m1} = \frac{MMF}{N_1} = 80 A$$

$I_w = ?$

$$I_{w \text{ loss}} = I_w^2 R_w = I_w I_w R_w = I_w E_p$$

$$1 = I_w E_p \Rightarrow I_w = \frac{1}{E_p}$$

$E_p = ?$

First E_s

$$E_s = I_s Z_s$$

$$= (4)(2.5) = 10V$$

$$N_w E_p = \frac{E_s}{n} = \frac{10}{90} = \frac{1}{9} \text{ W}$$

$$N_w I_w = \frac{1}{E_p} \Rightarrow I_w = 40 \text{ A}$$

$$R = n + \frac{I_w \cos \phi + I_u \sin \phi}{I_s}$$

$$= \frac{400 + (40 \times 0.8) + (80 \times 0.6)}{4}$$

$$\Rightarrow R = 420$$

$$\% \text{ Extra emf} = \left| \frac{n - R}{R} \times 100 \right| = 4.76\%$$

$$\theta = \frac{I_u \cos \phi - I_w \sin \phi}{I_s} \times \frac{180^\circ}{\pi}$$

$$\Rightarrow \theta = 1.43^\circ$$

EMI GATE ACADEMY

Wheatstone Bridge

Bridge network

DC bridge

- DC supply ($\omega = 0$)
- Only resistive components
- Phasors are not involved as V and I are in phase

AC bridge

- AC supply ($\omega \neq 0$)
- R, L, C
- Phasors are involved.

Why bridge is used?


For measurement of R, L, C , power factor, quality factor, etc.

Major application of bridge is the calibration of ammeter or voltmeter.

Wheatstone bridge is the basic DC bridge.
Invented by Charles Wheatstone in 1833.

It is a series parallel combination of 4 resistors which gives zero difference voltage at balanced condition.

Assume a simple network;

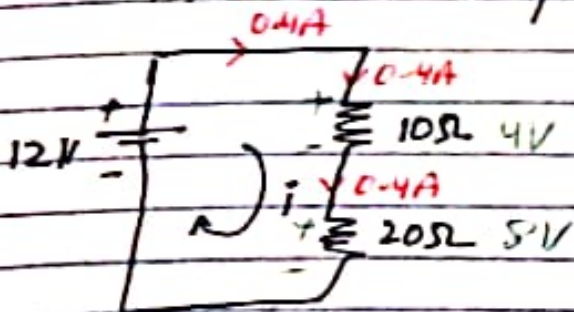


$$\begin{aligned} \text{KVL} \quad -12 + i10 + i20 &= 0 \\ 30i &= 12 \\ \Rightarrow i &= \frac{12}{30} = 0.4 \text{ A} \end{aligned}$$

Voltage drop;

$$10 \times 0.4 = 4 \text{ V}$$

$$20 \times 0.4 = 8 \text{ V}$$

Connect another same arm in parallel.

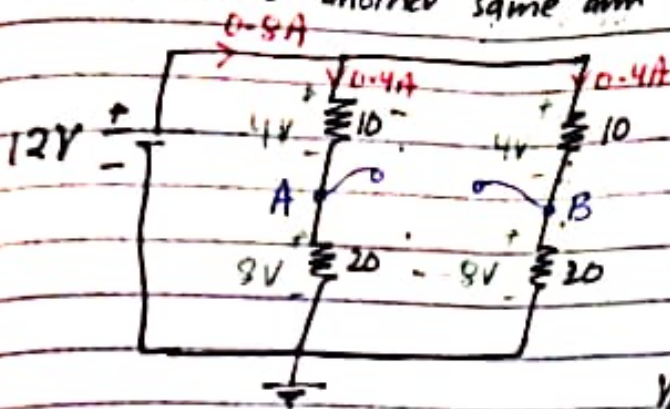

$$10 + 20 \parallel 10 + 20$$

Bk equivalent resistance is half i.e. $30/2$.
Current drawn is double i.e. 0.8

$$V_A = 8V \quad V_B = 8V$$


$$V_{AB} = V_A - V_B = 8 - 8 = 0V$$

Balanced condition.

Bridge?

4 arms and 4 nodes.

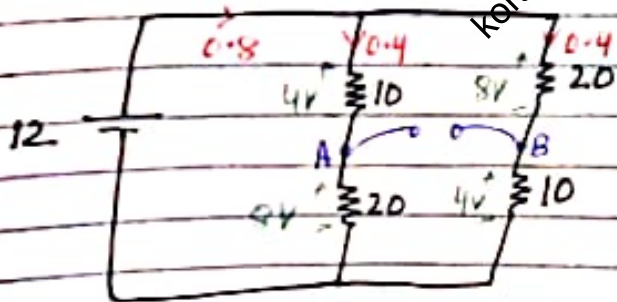Source and detector are always connected in two opposite nodes in a bridge network.



$$V_A = 8V$$

$$V_B = 4V$$

$$V_{AB} = V_A - V_B = 4V$$

Bridge unbalanced

Balancing is judged by voltages.

How is voltage modified in terms of current?

Difference voltage is the open circuit voltage of terminals A and B.

Install an instrument to detect balanced condition. Thevenin voltage

Basic electrical quantities: Voltage, current


Basic instruments: Voltmeter, Ammeter, Galvanometer.

voltage
measurment

current
measurment

galvanometer.
current
detection


Voltage source and Voltmeter

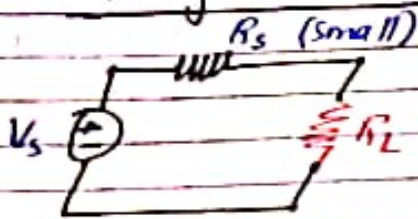

Practical voltage source



Ideal

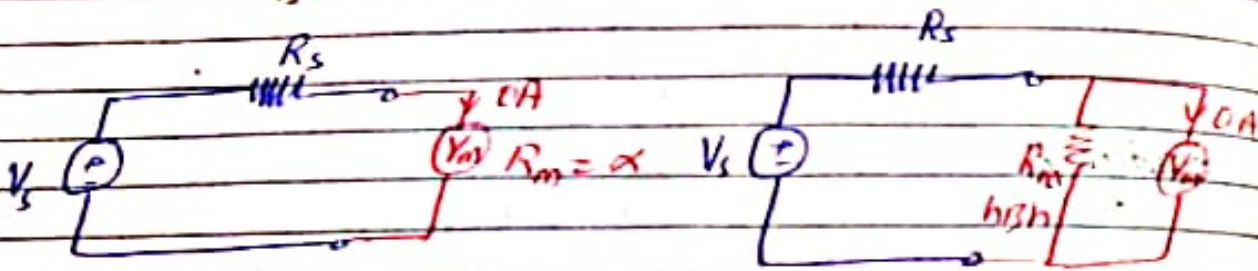

Ideal voltmeter.

$$\begin{aligned} \rightarrow (i) \quad -V_s + 0 \times R_s + V_m &= 0 \\ \Rightarrow V_m &= V_s \end{aligned}$$

(ii) Practical voltmeter

Therem / open circuit voltage as $I = 0$

(ii) Voltage divider rule

$$V_m = V_s \times \frac{R_m}{R_m + R_s} = V_s \times \frac{\text{High}}{\text{High} + \text{low}}$$

$$\Rightarrow V_m \approx V_s \times \frac{\text{high}}{\text{high}}$$

$$\Rightarrow V_m \approx V_s$$

Approximately Therem voltage.


Voltage source \Rightarrow internal impedance in series \Rightarrow very small ideally $R_s = 0$

voltmeter \Rightarrow internal impedance in parallel \Rightarrow very high. ideally infinite \Rightarrow current $= 0$


$$R_m = \infty$$

\Rightarrow open circuit voltage

Ammeter

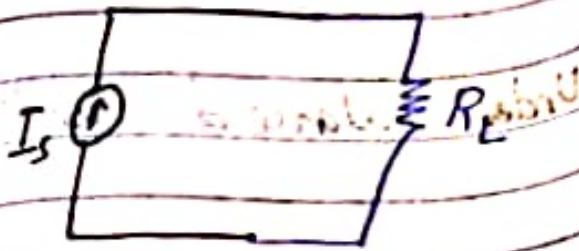

Ideal

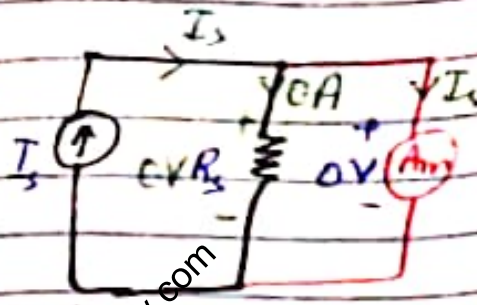

(i) Ideal ammeter



$$I_A = I_s \times \frac{R_s}{R_s + R_{am}} = I_s \times \frac{\text{high}}{\text{low} + \text{high}}$$

$$\Rightarrow \boxed{I_A \approx I_s}$$

$$I_A = I_s \times \frac{\text{high}}{\text{high}}$$

$$(ii) \boxed{I_A = I_s}$$

Ideal ammeter always measures the circuit current i.e. Norton current.

Current source Ammeter \rightarrow internal impedance in parallel \rightarrow very high ideally infinite.

Current Ammeter \rightarrow internal impedance in series \rightarrow very low ideally $R_s = 0 \rightarrow$ voltage = 0 \rightarrow so short circuit current.

So we can connect: either voltmeter, ammeter or galvanometer b/w points A and B.

Under balanced condition;



$$V = 0 \text{ Volt}$$




$$I = 0 \text{ Amp} \rightarrow \text{measured}$$



$$I = 0 \text{ Amp} \rightarrow \text{detected}$$

We can calculate the exact balanced point with the help of Thevenin equivalent circuit.


Thevenin Equivalent of Bridge Network

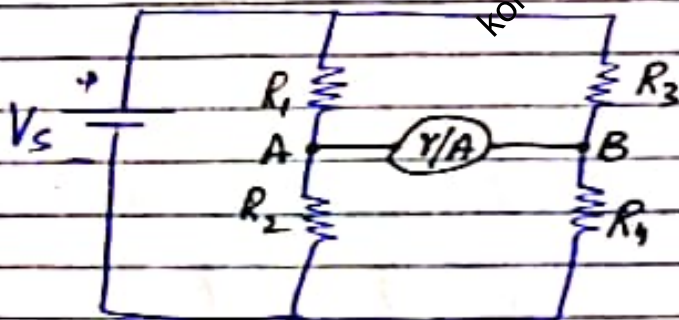

We calculate the Thevenin equivalent circuit across the terminals AB.

Calculation of Thevenin voltage.

Open circuit A and B.

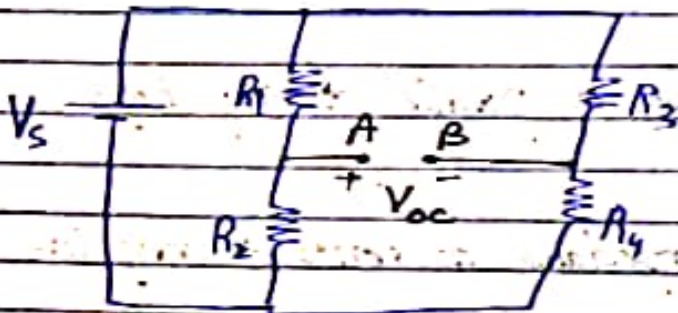

$$V_{oc} = V_A - V_B = V_{TH}$$


$$V_{TH} = \frac{V_s \times R_2}{R_1 + R_2} - \frac{V_s \times R_4}{R_3 + R_4}$$

$$V_{TH} = V_s \left[\frac{R_2}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \right]$$


$$V_{Th} = V_s \left[\frac{R_2 R_3 + R_2 R_4 - R_4 R_1 - R_2 R_4}{(R_1 + R_2)(R_3 + R_4)} \right]$$

$$V_m = V_s \left[\frac{R_2 R_3 - R_4 R_1}{(R_1 + R_2)(R_3 + R_4)} \right]$$

Calculation of Thevenin resistance

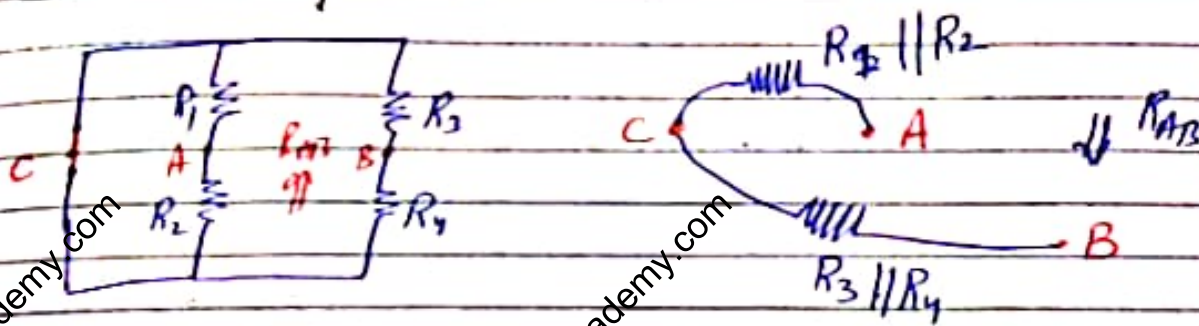

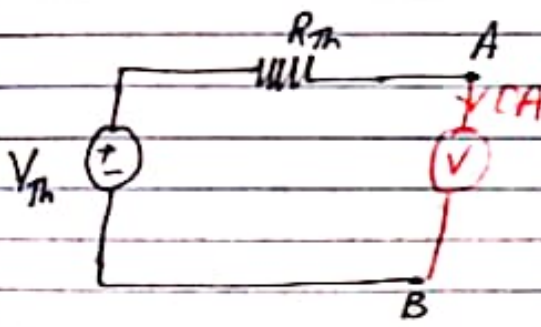
$$R_{AB} = R_{Th} = (R_1 \parallel R_2) + (R_3 \parallel R_4)$$



$$-V_{Th} + 0 \times R_{Th} + V = 0$$

$$V = V_{Th} = 0V$$

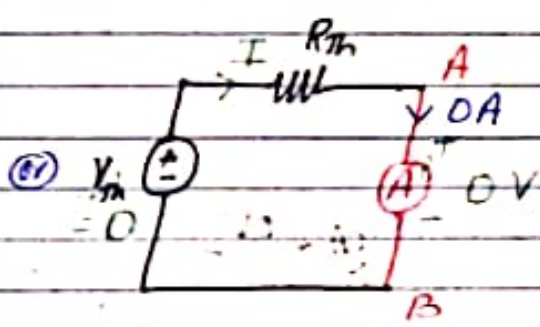

$$-0 + I R_{Th} + 0 = 0$$


$$\Rightarrow I = 0A$$

If balanced

Under balanced condition, the detector of bridge network is both open circuit and short circuit at the same time. (In case of resistive load)

$$V_{th} = 0 \Rightarrow R_2 R_3 - R_4 R_1 = 0$$
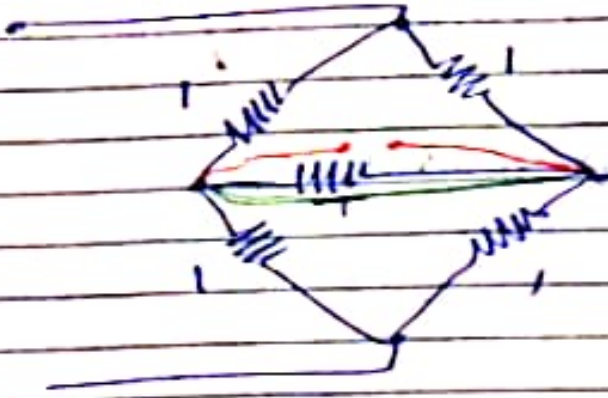
$$\Rightarrow \boxed{R_4 R_1 = R_2 R_3} \rightarrow \text{condition for balancing}$$



If open circuited

$$R_{th} =$$


$$\Rightarrow R_{th} = 1 \Omega$$

If short circuited

$$R_{th} = (1 \parallel 2) + (2 \parallel 1)$$

$$R_{th} = 0.5 + 0.5 = 1$$

The wheatstone bridge is as,

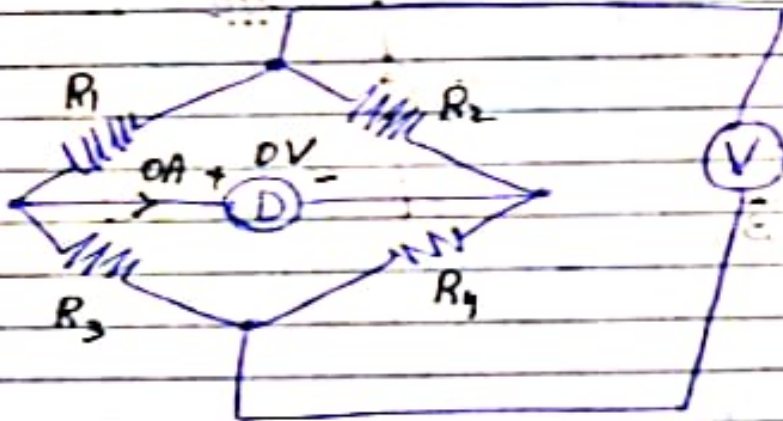


$$\boxed{R_2 R_3 = R_4 R_1}$$

Why are AC bridges used?

- i. For calculating R, L, C , power factor (p.f), dissipation factor (d.f) and loss tangent (LT) without using voltmeter and ammeter.
- ii. It is also used for providing phase shifting and providing feedback path to oscillators.

Basic Bridge network

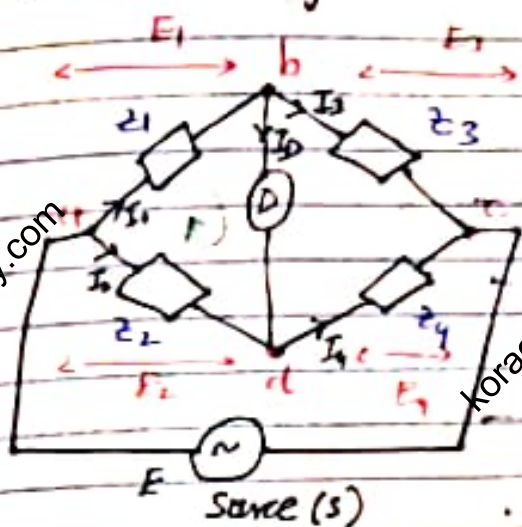

- 4 Nodes (a, b, c, d)
- 4 Arms (ab, ad, bc, cd)
- D: detector
- S: source

Source and Detector are connected in opposite nodes.

If source and detector are connected in the same node, the bridge will never come to balanced condition.

General criteria for bridge balance;

- (i) Detector current should be zero i.e. $I_D = 0$
- (ii) Potential difference b/w points b and d should be zero. i.e. $V_{bd} = 0$

Mathematical meaning of conditions;

$$I_1 = I_3, \quad I_2 = I_4$$

$$E_1 = E_3 \Rightarrow I_1 z_1 = I_3 z_3 \rightarrow \textcircled{A}$$

$$I_1 = I_3 = \frac{E}{z_1 + z_3}$$

$$I_2 = I_4 = \frac{E}{z_2 + z_4}$$

$$\textcircled{1} \Rightarrow \frac{E}{z_1 + z_3} \left(\frac{z_1}{z_1 + z_3} \right) = \frac{E}{z_2 + z_4} (z_2)$$

$$\Rightarrow \frac{z_1}{z_1 + z_3} = \frac{z_2}{z_2 + z_4}$$

$$\Rightarrow z_1(z_2 + z_4) = z_2(z_1 + z_3)$$

$$\Rightarrow z_1 z_2 + z_1 z_4 - z_1 z_2 - z_2 z_3 = 0$$

$$z_1 z_4 = z_2 z_3$$

similarly also for admittances;

$$Y_1 Y_4 = Y_2 Y_3$$

If impedances are given in complex form;

$$z_1 = |z_1| \angle \theta_1 \quad z_2 = |z_2| \angle \theta_2 \quad z_3 = |z_3| \angle \theta_3$$

$$z_4 = |z_4| \angle \theta_4$$

$$\Rightarrow |z_1| \angle \theta_1 \times |z_4| \angle \theta_4 = |z_2| \angle \theta_2 \times |z_3| \angle \theta_3$$

$$\Rightarrow |z_1| |z_4| \angle \theta_1 + \theta_4 = |z_2| |z_3| \angle \theta_2 + \theta_3$$

$$|z_1| |z_4| = |z_2| |z_3|$$


↳ magnitude criteria

$$\angle \theta_1 + \angle \theta_4 = \angle \theta_2 + \angle \theta_3$$

↳ phase criteria


ARM COMBINATIONS

1) Series R and L

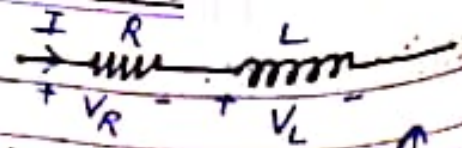

(i) Impedance angle (θ)

$$\tan \theta = \frac{\omega L}{R}$$

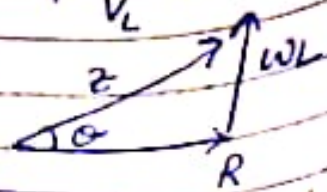

$$\Rightarrow \theta = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

(ii) Power Factor is $\cos \phi$

$$\cos \phi = \frac{R}{Z}$$

\Rightarrow this formula is valid only for series combination

(iii) Quality Factor (Q)


$$Q = \frac{V_L}{V_R} = \frac{\text{storing}}{\text{dissipating}} = \frac{I X_L}{I R} = \frac{X_L}{R}$$

$$Q = \frac{\omega L}{R}$$


(iv) Dissipation Factor is inverse of quality factor

$$\Rightarrow D = \frac{R}{\omega L}$$

2) Series R and C

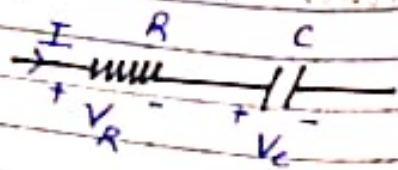

(i) Impedance angle

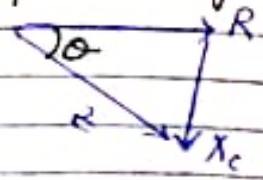

$$\tan \theta = \frac{1/\omega C}{R}$$

$$\theta = \tan^{-1} \left(\frac{1}{\omega C R} \right)$$

(ii) Power factor

$$\cos \phi = \frac{R}{Z}$$

ii. Quality Factor. $Q = \frac{V_C}{V_R} = \frac{I X_C}{I R} = \frac{X_C}{R}$


$\Rightarrow Q = \frac{1}{\omega C R}$

iv. Dissipation factor. $D = \frac{1}{Q} \Rightarrow D = \omega C R$

3 Parallel combination of R and L

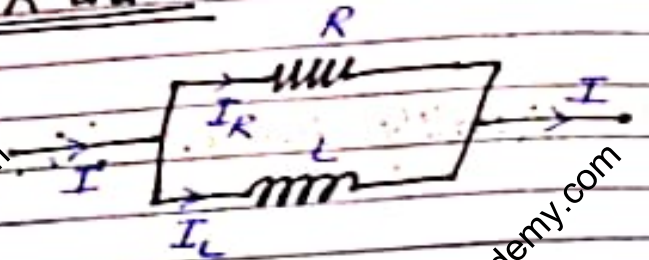(i) Impedance angle

$Z = R \parallel j\omega L$
 $Z = \frac{(R)(j\omega L)}{R + j\omega L}$



$\theta = 90^\circ - \tan^{-1}\left(\frac{\omega L}{R}\right)$

ii. Power Factor

As $I = I_R + I_L = \frac{V}{R} + \frac{V}{j\omega L} = V \left[\frac{1}{R} + \frac{1}{j\omega L} \right]$

$\frac{Y}{I} = \frac{1}{\left(\frac{1}{R} + \frac{1}{j\omega L}\right)}$ convert $Z \angle \phi$
 $\searrow \cos \phi$


(iii) Quality Factor

$Q = \frac{I_L}{I_R} = \frac{V/X_L}{V/R} = \frac{V R}{V X_L}$

$Q = \frac{R}{X_L} = \frac{R}{\omega L}$

(iii) Dissipation Factor, $D = \frac{1}{Q} = \frac{\omega L}{R}$

4 Parallel R and C

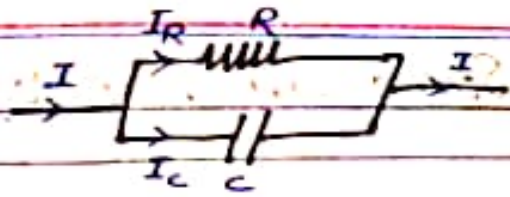

(i) Impedance Angle

$$Z = R \parallel \frac{1}{j\omega C} = \frac{(R) \left(\frac{1}{j\omega C} \right)}{R + \frac{1}{j\omega C}}$$

$$\angle Z = -90^\circ - \tan^{-1} \left(\frac{1}{\omega CR} \right)$$

(ii) Power Factor

$$I = I_R + I_C = \frac{V}{R} + \frac{V}{1/j\omega C} = V \left[\frac{1}{R} + j\omega C \right]$$

$$\frac{V}{I} = \left(\frac{1}{1/R + j\omega C} \right) \xrightarrow{\text{convert}} Z \angle \phi$$

(iii) Quality Factor

$$Q = \frac{I_C}{I_R} = \frac{V/1/j\omega C}{V/R} = \omega CR$$

(iv) Dissipation Factor

$$D = \frac{1}{Q} = \frac{1}{\omega CR}$$

Arm combination Q Factor

Series RL	$\Rightarrow Q = \omega L/R$
Parallel RL	$\Rightarrow Q = R/\omega L$
Series RC	$\Rightarrow Q = 1/\omega CR$
Parallel RC	$\Rightarrow Q = \omega CR$

$$Q_{\text{series}} = \frac{1}{Q_{\text{parallel}}}$$

Source And Detector


- For measurement at low frequency, power line may act as source of supply to bridge network.
- For measurement at high frequency, electronic oscillator may act as source of supply to bridge.
- Source and detector are always placed in opposite nodes.

Detector

Frequency

i. DC Galvanometer	0 Hz (DC)
ii. Vibration galvanometer	2 - 100 Hz
iii. Telephone and headphone galvanometer	100 - 2000 Hz
iv. Tunable amplifier galvanometer	$f > 2 \text{ kHz}$
v. CRO	In MHz.

Maxwell's Bridge

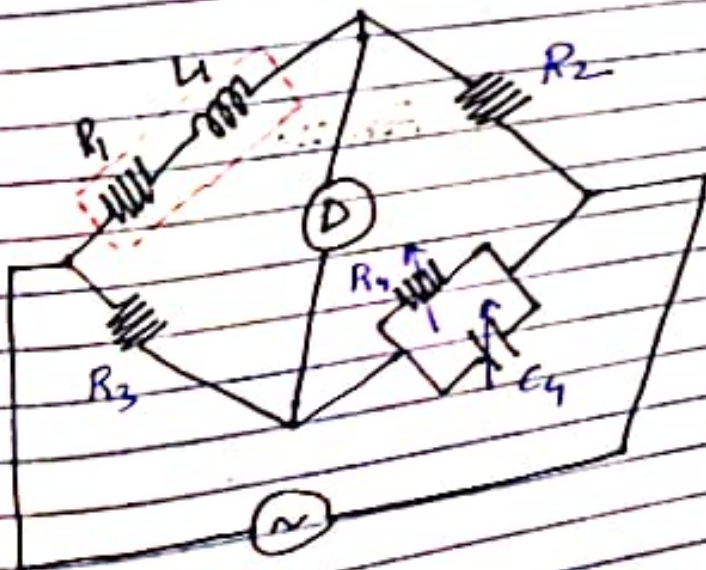

$R_1, L_1 \rightarrow$ unknown.

Rest all parameters are known.

$$Z_1 = R_1 + j\omega L_1$$

$$Z_2 = R_2$$

$$Z_3 = R_3$$

$$Z_4 = R_4 \parallel C_4$$

$$= \frac{R_4 \left(\frac{1}{j\omega C_4} \right)}{R_4 + \frac{1}{j\omega C_4}}$$

$$Z_4 = \frac{R_4}{j\omega C_4} = \frac{1 + j\omega R_3 C_4}{j\omega C_4}$$

$$Z_4 = \frac{R_4}{1 + j\omega R_3 C_4}$$

By opposite impedances; $Z_1 Z_4 = Z_2 Z_3$

$$\Rightarrow (R_1 + j\omega L_1) \left(\frac{R_4}{1 + j\omega R_3 C_4} \right) = R_2 R_3$$

$$\Rightarrow (R_1 + j\omega L_1) R_4 = R_2 R_3 (1 + j\omega R_3 C_4)$$

$$\Rightarrow R_1 R_4 + j\omega L_1 R_4 = R_2 R_3 + j\omega R_2 R_3 R_3 C_4$$

L.H.S = R.H.S \Rightarrow Real = Real
Imaginary = Imaginary

Real

$$R_1 R_4 = R_2 R_3 \Rightarrow R_1 = \frac{R_2 R_3}{R_4}$$

Imaginary

$$j\omega L_1 R_4 = j\omega R_2 R_3 R_3 C_4$$

$$L_1 = R_2 R_3 C_4 \quad L_1 \propto f(C_4)$$

$$R_1 = f(R_4)$$

Q factor of unknown arm

is $Q = \frac{\omega L_1}{R_1} \rightarrow$ put L_1 and R_1

$$Q = \frac{\omega R_2 R_3 C_4 R_4}{R_2 R_3} \Rightarrow Q = \omega C_4 R_4$$

$Q \propto C_4 \rightarrow$ disadvantage


medium range of Q factor \leftarrow

- $Q < 1 \rightarrow$ Anderson Bridge
- $1 < Q < 10 \rightarrow$ Maxwell's bridge
- $Q > 10 \rightarrow$ Hay's bridge

Key Points in Maxwell's Bridge

- \rightarrow Used for determination of medium range of Q factor.
- \rightarrow At balanced condition R_1, L_1 are independent of supply frequency.
- \rightarrow To achieve faster response, R_4 and C_4 should be variable.
- \rightarrow Maxwell's bridge should be used for measurement of R, L, Q factor and dissipation factor.

HAY'S BRIDGE

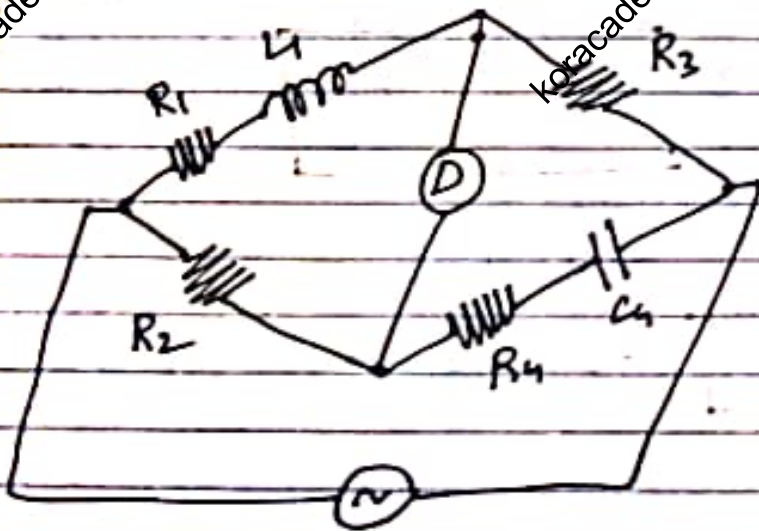

$$Z_1 = R_1 + j\omega L_1$$

$$Z_2 = R_2$$

$$Z_3 = R_3$$

$$Z_4 = R_4 + \frac{1}{j\omega C_4}$$

At balanced condition,

$$Z_1 Z_4 = Z_2 Z_3$$

$$(R_1 + j\omega L_1) \left(R_4 + \frac{1}{j\omega C_4} \right) = R_2 R_3$$

$$(R_1 + j\omega L_1) \left(\frac{j\omega C_4 R_4 + 1}{j\omega C_4} \right) = R_2 R_3$$

$$\Rightarrow (R_1 + j\omega L_1) (j\omega C_4 R_4 + 1) = R_2 R_3 j\omega C_4$$

$$\Rightarrow j\omega C_4 R_4 R_1 + R_1 + j\omega L_1 - \omega^2 L_1 C_4 R_4 = j\omega R_2 R_3 C_4$$

$$\Rightarrow \boxed{j\omega C_4 R_4 R_1 + R_1 + j\omega L_1 = \omega^2 L_1 C_4 R_4 + j\omega C_4 R_2 R_3}$$

Real = Real Imaginary = Imaginary

$$R_1 + j\omega (L_1 + C_4 R_4 R_1) = \omega^2 L_1 C_4 R_4 + j\omega C_4 R_2 R_3$$

Real $\boxed{R_1 = \omega^2 L_1 C_4 R_4}$

$$j\omega (L_1 + C_4 R_4 R_1) = j\omega C_4 R_2 R_3$$

$$L_1 = C_4 R_2 R_3 - C_4 R_4 R_1$$

$$L_1 = C_4 (R_2 R_3 - R_4 R_1)$$

Problem: one unknown is a function of another
i.e. R_1 of L_1

Putting values $L_1 + C_4 R_4 (\omega^2 L_1 C_4 R_4) = C_4 R_2 R_3$

$$L_1 + \omega^2 L_1 C_4^2 R_4^2 = C_4 R_2 R_3$$

$$L_1 (1 + \omega^2 C_4^2 R_4^2) = C_4 R_2 R_3$$

$$\boxed{L_1 = \frac{C_4 R_2 R_3}{1 + \omega^2 C_4^2 R_4^2}}$$

put this in R_1

$$R_1 = \omega^2 C_4 R_4 \times \frac{C_4 R_2 R_3}{1 + \omega^2 C_4^2 R_4^2}$$

$$R_1 = \frac{\omega^2 R_2 R_3 R_4 C_4^2}{1 + \omega^2 C_4^2 R_4^2}$$

Now $Q = \frac{1}{\omega^2 C_4^2 R_4^2}$

If Q is high

$$1 + \omega^2 C_4^2 R_4^2 = 1 + \left(\frac{1}{Q}\right)^2 \approx 1$$

$$\Rightarrow L_1 \approx C_4 R_2 R_3$$

$$R_1 \approx \omega^2 R_2 R_3 R_4 C_4^2$$

For unknown arm, $Q = \frac{\omega R_1}{R_1} \rightarrow$ put exact values

$$Q = \omega \frac{C_4 R_2 R_3}{1 + \omega^2 C_4^2 R_4^2} \times \frac{1 + \omega^2 C_4^2 R_4^2}{\omega^2 R_2 R_3 R_4 C_4^2}$$

$$Q = \frac{1}{\omega R_4 C_4} \Rightarrow Q \propto \frac{1}{C}$$


disadvantage? R_1 is a function of frequency

From equations of R_1 and L_1 , R_1 and C_4 are variable

Boundness? Vary R_4 first and then C_4 .

\hookrightarrow slow response.

SCHERING BRIDGE

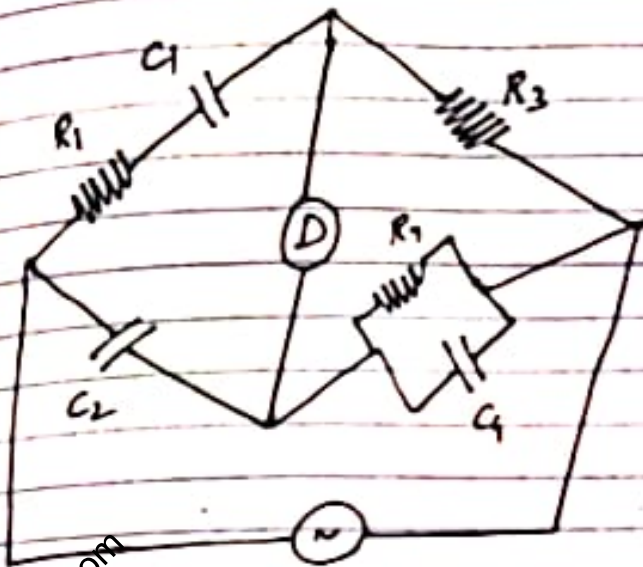

$$Z_1 = R_1 + \frac{1}{j\omega C_1}$$

$$Z_2 = \frac{1}{j\omega C_2}$$

$$Z_3 = R_3$$

$$Z_4 = R_4 \parallel \frac{1}{j\omega C_4}$$

$$Z_4 = \frac{R_4}{1 + j\omega R_4 C_4}$$

Balanced condition;

$$Z_1 Z_4 = Z_2 Z_3$$

$$\Rightarrow \left(R_1 + \frac{1}{j\omega C_1} \right) \left(\frac{R_4}{1 + j\omega R_4 C_4} \right) = R_3 \left(\frac{1}{j\omega C_2} \right)$$

$$\Rightarrow \left(R_1 + \frac{1}{j\omega C_1} \right) R_4 = \frac{R_3}{j\omega C_2} (1 + j\omega R_4 C_4)$$

$$\Rightarrow R_1 R_4 + \frac{R_4}{j\omega C_1} = \frac{R_3}{j\omega C_2} + \frac{j\omega R_4 R_3 C_4}{j\omega C_2}$$

Comparing real $R_1 R_4 = \frac{R_3 R_4 C_4}{C_2}$

$$R_1 = \frac{R_3 C_4}{C_2}$$

Imaginary

$$\frac{R_4}{j\omega C_1} = \frac{R_3}{j\omega C_2} \Rightarrow \frac{R_4}{C_1} = \frac{R_3}{C_2}$$

$$C_1 = \frac{R_4 C_2}{R_3}$$

Quality Factor

$$Q_1 = \frac{1}{\omega C_1 R_1}$$

Dissipation factor, $D_1 = \omega C_1 R_1$

$$D_1 = \omega \left(\frac{R_4 C_2}{R_3} \right) \left(\frac{R_3 C_1}{Q_1} \right)$$

$$\Rightarrow D_1 = \omega R_4 C_4$$

$$\omega C_1 R_1 = \omega R_4 C_4$$

DeSAUTY'S BRIDGE

DeSauty's bridge

Unmodified

modified

→ Used for perfect capacitor.

$$C \neq 0, R = \infty$$


Imperfect C.

$$R \neq 0, C \neq 0$$

Unmodified DeSauty's Bridge

lossless C.

C_1 is unknown.

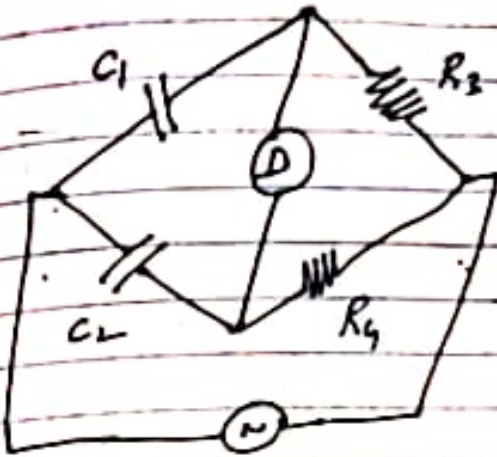

$$Z_1 = \frac{1}{j\omega C_1}$$

$$Z_2 = \frac{1}{j\omega C_2}$$

$$Z_3 = R_3$$

$$Z_4 = R_4$$

Opposite impedances $Z_1 Z_4 = Z_2 Z_3$


$$\left(\frac{1}{j\omega C_1}\right) R_4 = \left(\frac{1}{j\omega C_2}\right) R_3$$

$$\Rightarrow \frac{R_4}{j\omega C_1} = \frac{R_3}{j\omega C_2} \Rightarrow \boxed{C_1 = \frac{R_4 C_2}{R_3}}$$

only real or only imaginary term?
B/c only one variable here i.e. C_1 .

Modified DeSauty's Bridge

Y_1, Y_2 , losses.

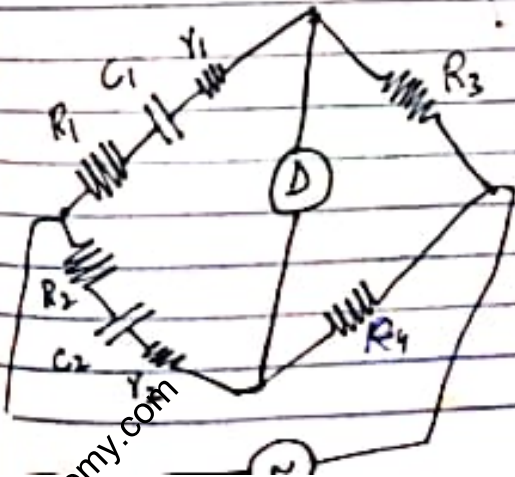

$$Z_1 = R_1 + Y_1 + \frac{1}{j\omega C_1}$$

$$Z_2 = R_2 + Y_2 + \frac{1}{j\omega C_2}$$

$$Z_3 = R_3, \quad Z_4 = R_4$$

Opposite impedances $Z_1 Z_4 = Z_2 Z_3$

$$\Rightarrow \left(R_1 + X_1 + \frac{1}{j\omega C_1} \right) R_4 = \left(R_2 + X_2 + \frac{1}{j\omega C_2} \right) R_3$$

$$\Rightarrow \boxed{R_1 R_4 + X_1 R_4 + \frac{R_4}{j\omega C_1} = R_2 R_3 + X_2 R_3 + \frac{R_3}{j\omega C_2}}$$

Comparing real.

$$(R_1 + X_1) R_4 = (R_2 + X_2) R_3$$

$$\Rightarrow R_1 + X_1 = \frac{(R_2 + X_2) R_3}{R_4}$$

$$\Rightarrow \boxed{R_1 = \frac{(R_2 + X_2) R_3}{R_4} - X_1}$$

Comparing imaginary;

$$\frac{R_4}{j\omega C_1} = \frac{R_3}{j\omega C_2} \Rightarrow \frac{R_4}{C_1} = \frac{R_3}{C_2}$$

$$\Rightarrow \boxed{C_1 = \frac{R_4 C_2}{R_3}}$$

Quality Factor, $Q_1 = \frac{1}{\omega C_1 R_1}$

Dissipation factor, $D_1 = \omega C_1 R_1$

put values of C_1 and R_1

$$D_1 = \frac{WR_4 C_2}{R_3} \left[\frac{(R_2 + Y_2) R_3 - Y_1 R_4}{R_4} \right]$$

$$D_1 = \frac{WC_2}{R_3} \left[(R_2 + Y_2) R_3 - Y_1 R_4 \right]$$

$$D_1 = \frac{WC_2}{R_3} \left[R_2 + Y_2 \right] R_3 - Y_1 R_4$$

$$D_1 = WC_2 R_2 + WC_2 Y_2 - WC_2 Y_1 R_4$$

$$D_1 = D_2 + WC_2 Y_2 - WC_2 Y_1 R_4$$

Dissipation factor of the capacitor depends on D of another, so we can't measure D₁ and hence can't measure Q₁.
So this bridge is only used for calculation of imperfect capacitance.

Kelvin's Bridge for unknown resistance.


Very low resistances can't be measured by Wheatstone bridge because of lead resistance.

Lead resistance!

S + resistance

R + resistance

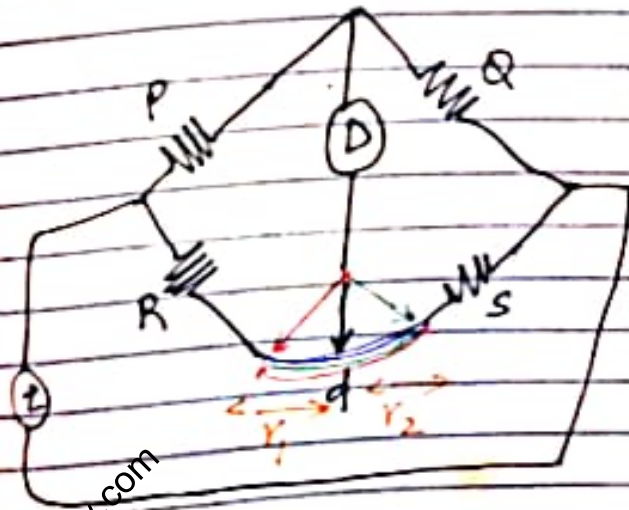Connect at d to nullify lead resistances.



$$\frac{R}{R_2} = \frac{P}{Q}$$

opposite impedances; $P(S+Y_2) = Q(R+Y_1)$

$$\Rightarrow R+Y_1 = \frac{P}{Q}(S+Y_2) \rightarrow \text{①}$$

$$\text{As } \frac{Y_1}{Y_2} = \frac{P}{Q}$$

$$\Rightarrow \frac{Y_1}{Y_1+Y_2} = \frac{P}{P+Q}$$

$$\text{and } \frac{Y_2}{Y_1+Y_2} = \frac{Q}{P+Q}$$

$$\text{let } Y_1+Y_2 = Y$$

$$\text{①} \Rightarrow R + \left(\frac{P}{P+Q} Y \right) = \frac{P}{Q} \left(S + \frac{Q}{P+Q} Y \right)$$


$$\Rightarrow R + \frac{PY}{P+Q} = \frac{PS}{Q} + \frac{PY}{P+Q}$$

$$\Rightarrow R + \frac{PY}{P+Q} = \frac{PS}{Q} + \frac{PY}{P+Q}$$

$$\boxed{R = \frac{PS}{Q}}$$

WEIN BRIDGE

$$Z_1 Z_4 = Z_2 Z_3$$

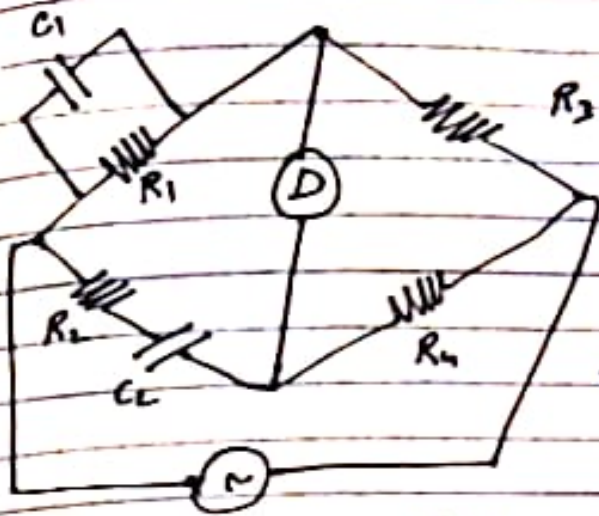

$$\rightarrow (R_1 \parallel C_1) R_4 = R_3 \left(R_2 + \frac{1}{j\omega C_2} \right)$$

$$\Rightarrow \left(\frac{R_1}{1 + j\omega C_1 R_1} \right) R_4 = R_3 R_2 + \frac{R_3}{j\omega C_2}$$

$$\Rightarrow \frac{R_1 R_4}{1 + j\omega C_1 R_1} = \frac{R_3 R_2 j\omega C_2 + R_3}{j\omega C_2}$$

$$\Rightarrow R_1 R_4 (j\omega C_2) = (R_3 R_2 j\omega C_2 + R_3) (1 + j\omega C_1 R_1)$$

$$\Rightarrow R_1 R_4 (j\omega C_2) = R_3 + j\omega C_1 R_3^2 + R_3 R_2 j\omega C_2 + R_3 (-1)\omega^2 C_1 C_2 R_2 R_1$$

Equate real part to zero.

$$R_3 + (-1)\omega^2 R_2 R_3 C_2 R_1 C_1 = 0$$

$$R_3 = \omega^2 R_2 R_3 C_2 R_1 C_1$$

$$\Rightarrow \omega = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

CRO

Basic voltmeter

↳ electronic voltmeter

↳ responsible quantity is voltage:

CRO is a voltage sensitive element.

↳ we have a display

↳ Electronic image plotter

Test circuit checks the unknown signal.

Probe and cable working as transmitting media

↳ will take signal into vertical amplifier.

its o/p now goes in two ^{ways} parts

↳ horizontal plate.

CRT → electron gun → we can control its intensity and focus.

We generally measure different parameters in y-t mode.

We generate a signal in horizontal time based circuit (whose time period is in our control) and take it into vertical plates through horizontal amplifier.

In x-y mode we provide external signal and it is used when we have to measure phase difference b/w two signals or frequency.

y-t mode is Amplitude Time mode.


x-y mode has x and y two different signals.

The basic principle of CRO is thermionic emission


koracademy.com

koracademy.com

koracademy.com

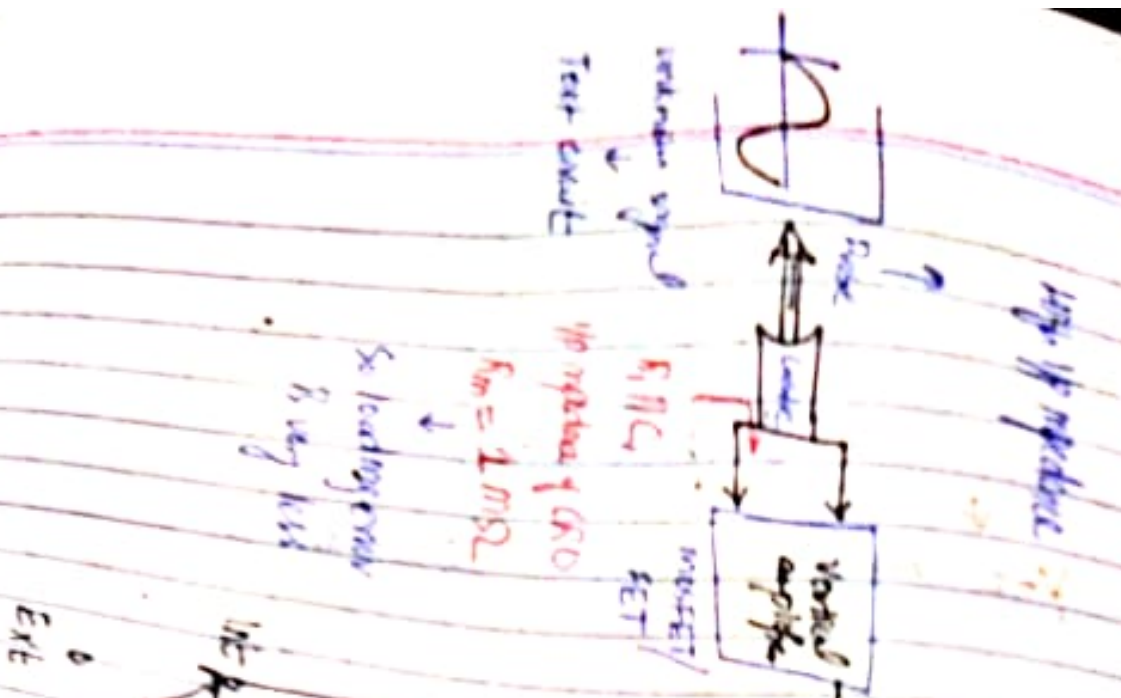

high impedance

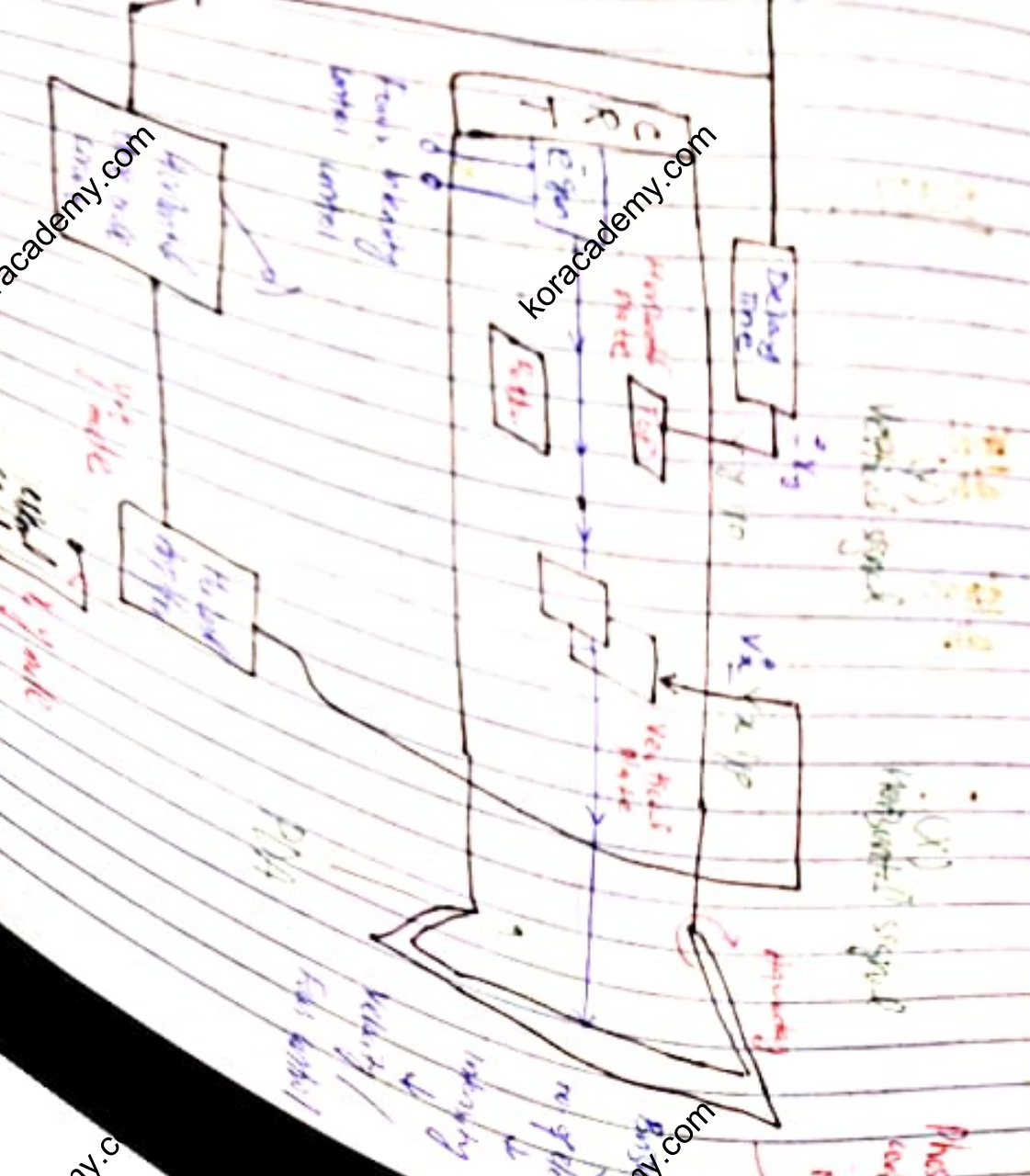

Focus: binary
lower control

EXT

koracademy.com

koracademy.com

koracademy.com

koracademy.com

koracademy.com

koracademy.com

PDA \rightarrow Post deflection acceleration.


If electron speed is low, it spreads it to get a sharp image on the screen.

Modes of CRO

- Y-t mode**
 - \rightarrow RMS
 - \rightarrow Peak
 - \rightarrow Average value
- x-y mode**
 - \rightarrow Phase
 - \rightarrow Frequency

SCREEN

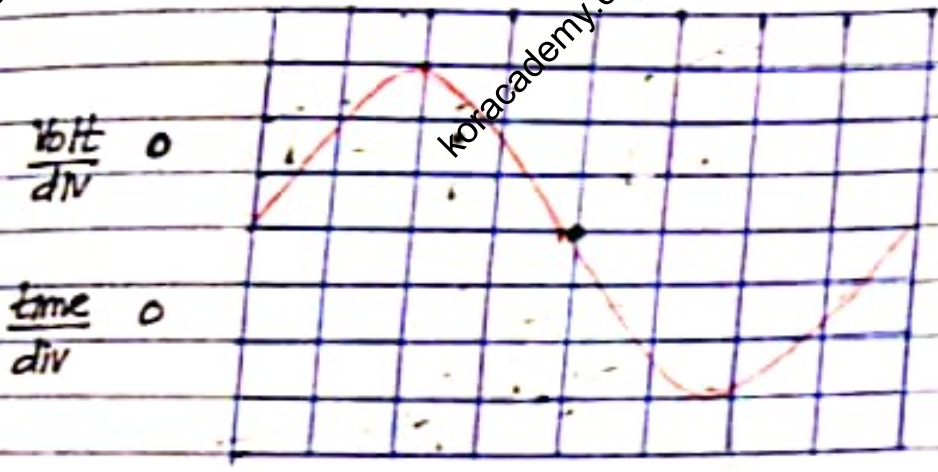y setting = volt/div \rightarrow voltage
x setting = time/div \rightarrow time




• origin this is an 8x8 screen.
 \hookrightarrow total rows & columns.

Two knobs, volt/div and time/div.

eg if volt/div is 2V, it means that each division is of 2V.

Consider the case.
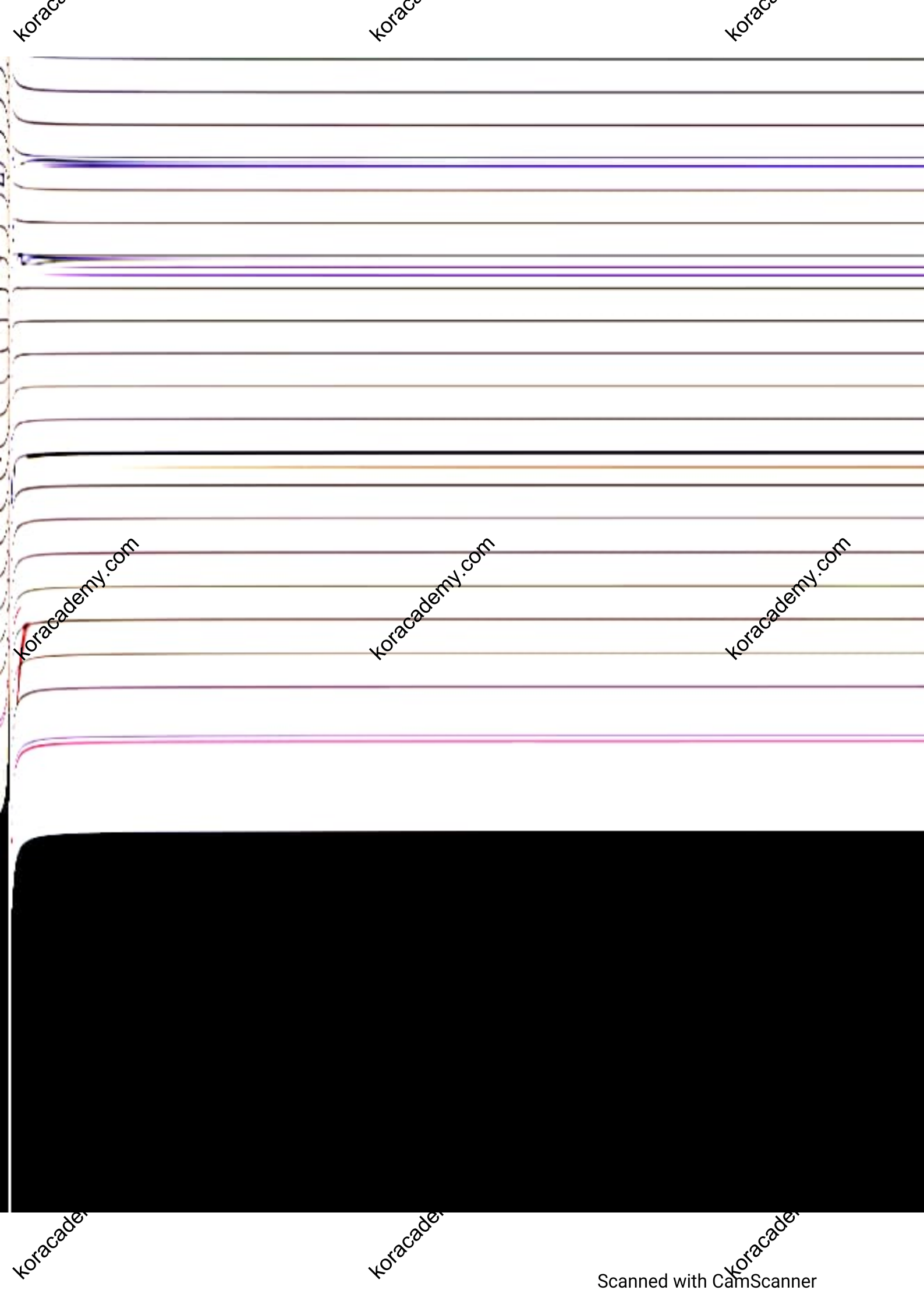
$$\text{Peak value} = 3 \text{ div} \times 2 \frac{\text{volt}}{\text{div}} = 6 \text{ volts}$$



koraca

koraca

koraca

koracademy.com

koracademy.com

koracademy.com

koracade


koracade

koracade


$$y-t \text{ plot} = S \times V_y$$

t	V _x	V _y	
t ₀	-2	0	→ 0 × 2 = 0
t ₁	-1	+2	→ 2 × 2 = 4 div
t ₂	0	0	→ 0 × 2 = 0
t ₃	-1	-2	→ -2 × 2 = -4 div
t ₄	+2	0	→ 0 × 2 = 0

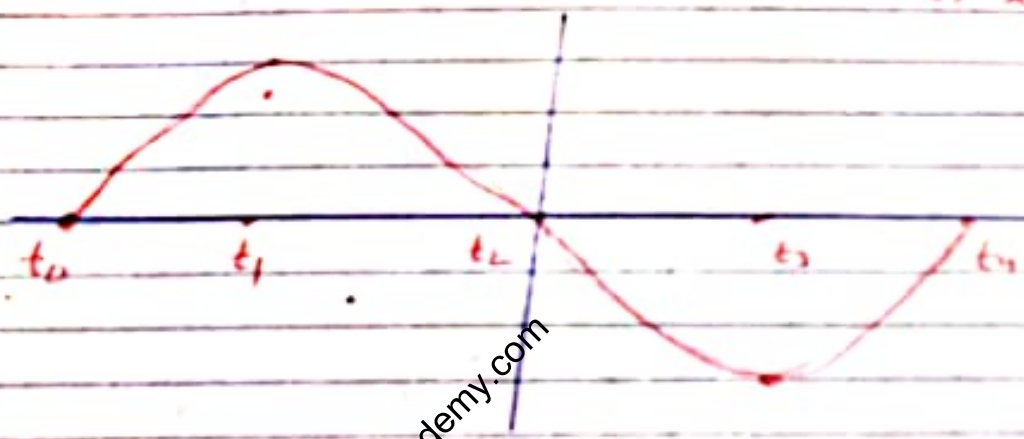→ we can also find the exact values as sensitivity is known




Conclusions from y-t mode

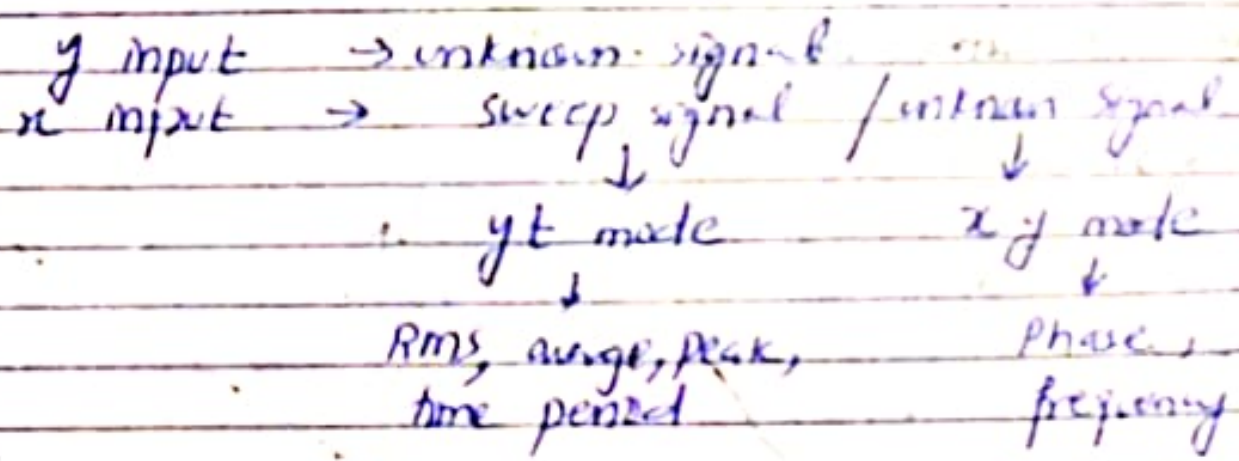


CRO will display the signal definitely but what portion will it display is important.

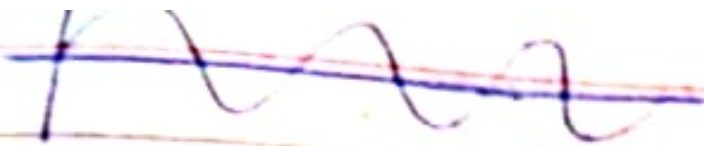
↳ At least one complete cycle should be displayed.



$f_{\text{signal}} = 1 \text{ kHz}$

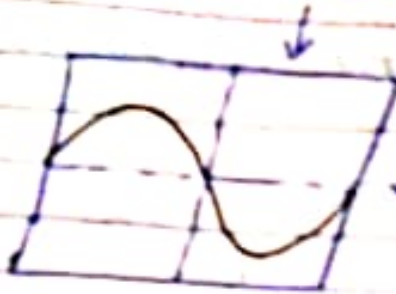

$f_{\text{sweep}} = 2 \text{ kHz}$

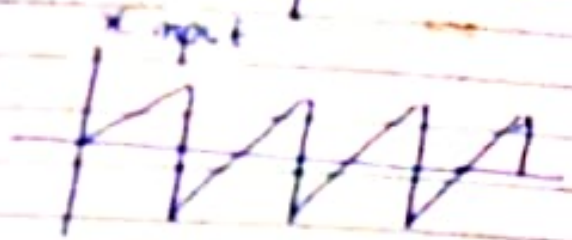

If n is the no. of cycles to be displayed;

$$n = \frac{f_{\text{signal}}}{f_{\text{sweep}}}$$

Ex: Here $n = \frac{1 \text{ kHz}}{1 \text{ kHz}} = 1$

Similarly we can calculate using time period;

$$n = \frac{1}{T_{\text{sig}}} \div \frac{1}{T_{\text{sweep}}} = \frac{1}{T_{\text{sig}}} \times T_{\text{sweep}}$$

$$\Rightarrow n = \frac{T_{\text{sweep}}}{T_{\text{signal}}}$$


To display more cycles than 1,

$$n > 1 \quad \frac{f_{\text{signal}}}{f_{\text{sweep}}} > 1 \Rightarrow f_{\text{signal}} > f_{\text{sweep}}$$


$$\text{or similarly} \quad \frac{T_{\text{sweep}}}{T_{\text{signal}}} > 1 \Rightarrow T_{\text{sweep}} > T_{\text{signal}}$$

C F_{signal} γ_s F_{sweep}

1 Unsynchronized and untriggered

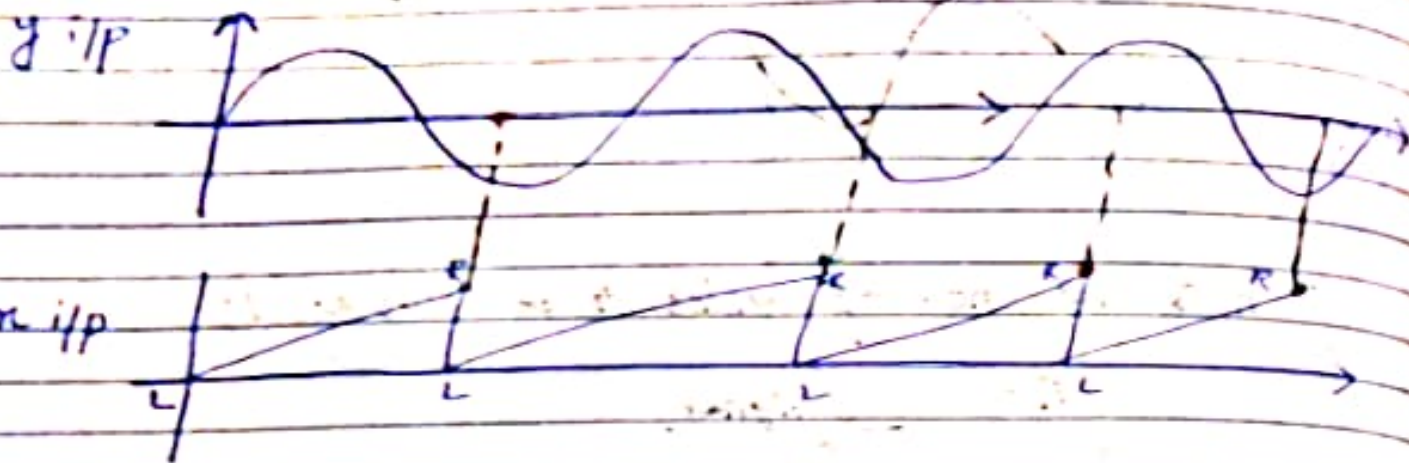


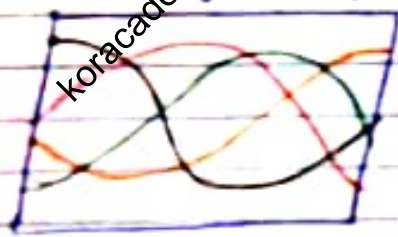
Oscilloscope displays the portion of y i/p for which the x i/p is increasing from left to right.



So we have a jumped up.

2 Trigger Setting Are made

Slope = +ve Voltage level = 0 volts

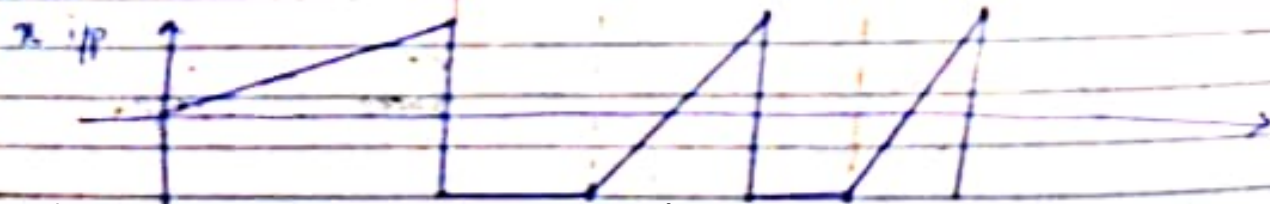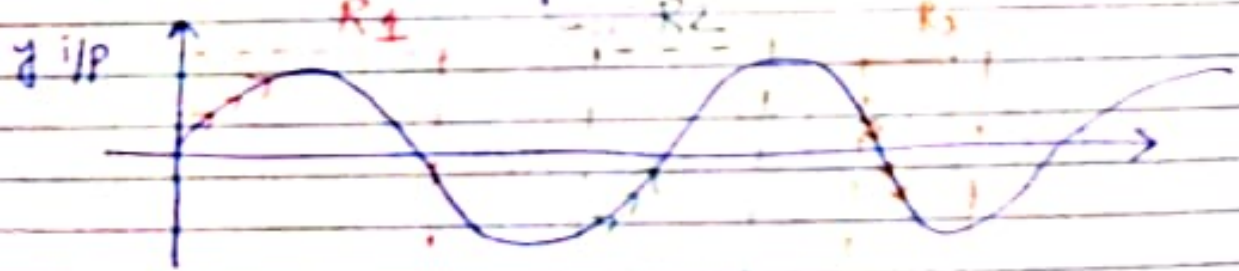


R1 satisfies conditions: i.e. slope is not zero
voltage = 0



R2 has slope +ve but not voltage 0 so it will not be on the display.

R3 does not satisfy any condition

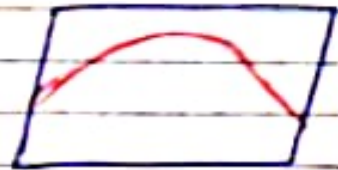So R1 satisfies both conditions and hence it is steady state off to be displayed on the screen.



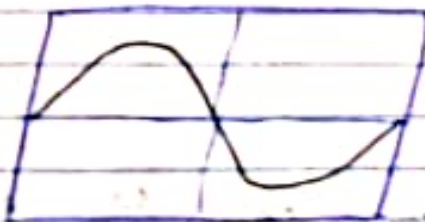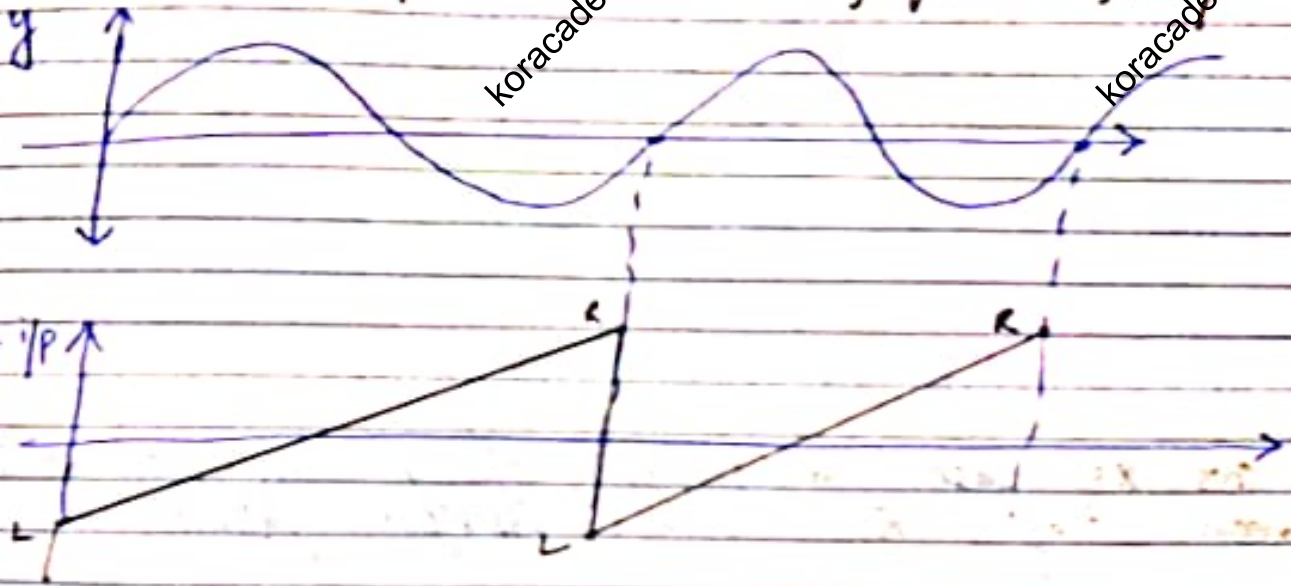3: Trigger settings are made and with this we adjust time/div to make: $f_{\text{signal}} = f_{\text{trigger}}$



Steady state off

slope = +ve
initial voltage level = 0


$f_{\text{sweep}} = f_{\text{signal}}$

→ synchronization

XY mode of operation

Y input : Unknown signal
X input : externally applied known signal.

we know its phase and frequency etc.

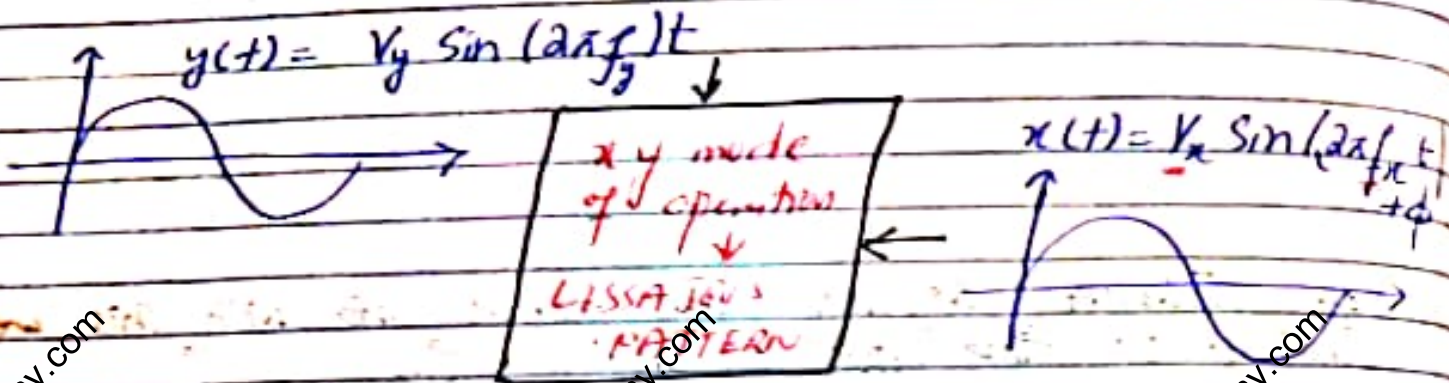

In xy mode we are not using CRO as image plotter.

↳ No ramp on x (sweep signal) → no linear rise → no y signal plot on screen against rise.

V_x and f_x are known.

V_y and f_y are unknown.

In this xy case, a pattern will be generated on the screen of CRO called Lissajous pattern.

With Lissajous pattern, we will carry out;

- (i) Phase measurement.
- (ii) Frequency measurement.

$$V_y > V_x \quad \text{slope} > 45^\circ$$

$$V_y = V_x \quad \text{slope} = 45^\circ$$

$$V_x < V_y \quad \text{slope} < 45^\circ$$


Phase Measurement Using Lissajous Pattern

$y \text{ i/p} \rightarrow V_y(t) = V_y \sin(2\pi f_y t + \phi) \rightarrow \text{unknown}$
 $x \text{ i/p} \rightarrow V_x(t) = V_x \sin(2\pi f_x t) \rightarrow \text{known}$

Case 1 $\phi = 0^\circ$

Assume $V_y = V_x = 2 \text{ V}$
 $f_y = f_x = 50 \text{ Hz}$
 $\omega_y = \omega_x = 2\pi \times 50 = 314 \text{ rad/s}$

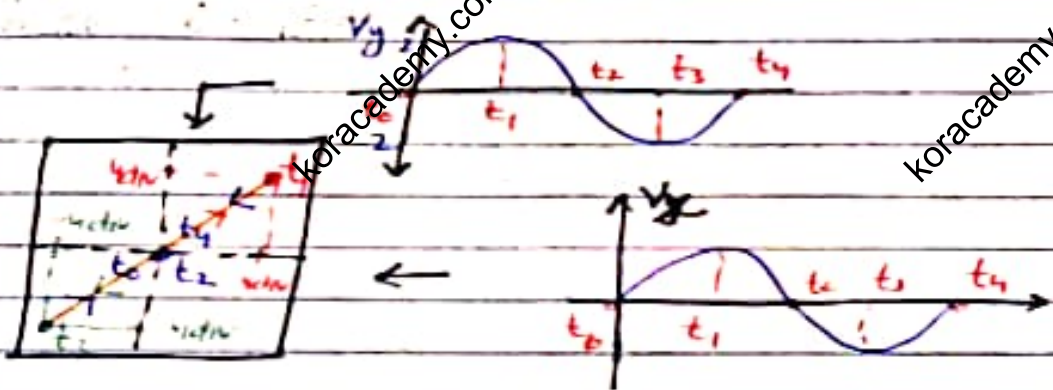$\Rightarrow V_y(t) = 2 \sin 314 t$
 $V_x(t) = 2 \sin 314 t$



Say sensitivity $s = 2 \frac{\text{div}}{\text{V}}$

t	x i/p	y i/p
t_0	0	0
t_1	2	2
t_2	0	0
t_3	-2	-2
t_4	0	0


$\rightarrow 2 \text{ div/Volt} \times 2 \text{ Volt} = 4 \text{ div}$

$\rightarrow 2 \text{ div/Volt} \times -2 \text{ Volt} = -4 \text{ div}$

- Lissajous pattern for $\phi = 0^\circ$
 \hookrightarrow is a straight diagonal line which is in 1st and 3rd quadrant with slope 45°

Case II $\phi = 45^\circ$

$$V_y = 2 \sin(314t + 45^\circ)$$

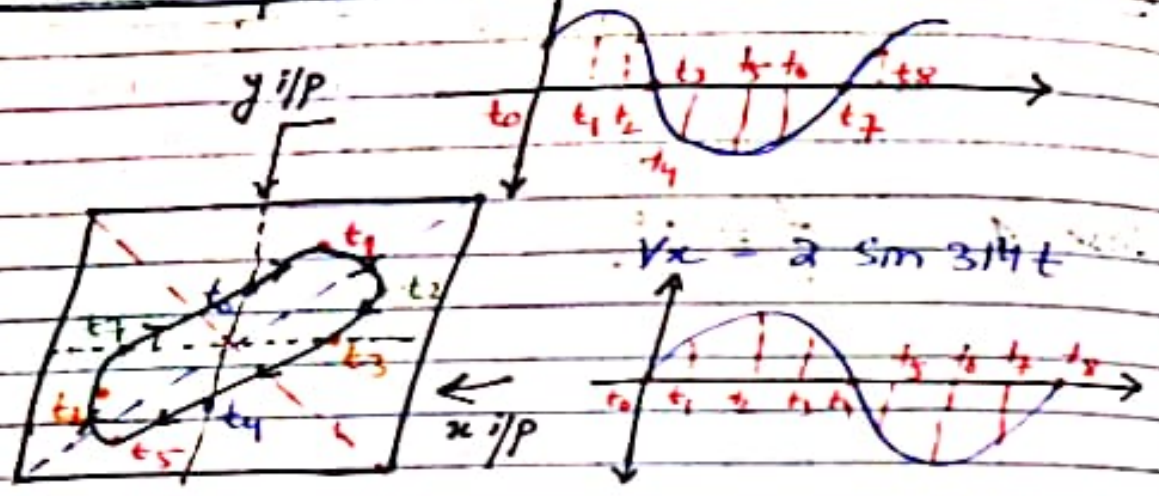

t	V_x	V_y
t_0	0	$2/\sqrt{2}$
t_1	$2\sqrt{2}$	2
t_2	2	$\sqrt{2}$
t_3	$\sqrt{2}$	0
t_4	0	$-\sqrt{2}$
t_5	$-\sqrt{2}$	-2
t_6	-2	$-\sqrt{2}$
t_7	$-\sqrt{2}$	0
t_8	0	$\sqrt{2}$

An ellipse with clockwise rotation is produced.


Major axis \rightarrow I and III quadrant
 Minor axis \rightarrow II and IV quadrant

\rightarrow From this we conclude that phase shift is possible.

$$0 < \phi < 90^\circ$$

Case III $\phi = 90^\circ$

$$2 \sin(314t + 90^\circ) =$$

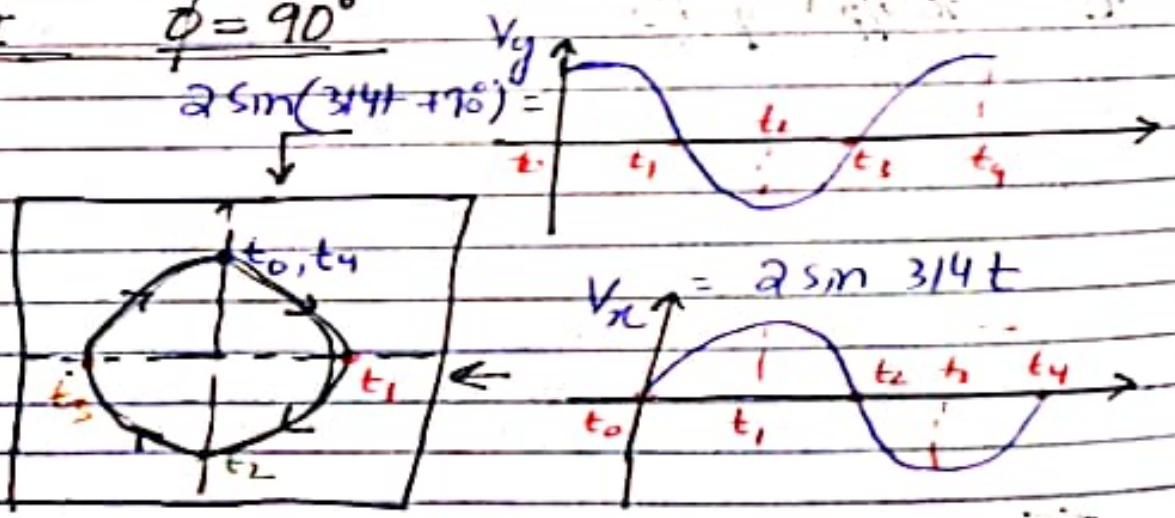

t	V _x	V _y
t ₀	0	2
t ₁	2	0
t ₂	0	-2
t ₃	-2	0
t ₄	0	2

If phase difference is 90°, the Lissajous pattern is a perfect circle with clockwise rotation.


Conclusions From Lissajous pattern



$\phi = 0^\circ$


1st and 3rd quadrant

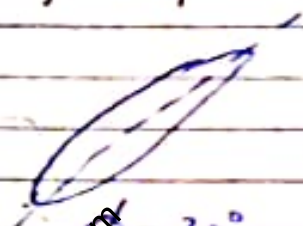$V_x = V_y$ slope = 45°
 $V_y > V_x$ slope $> 45^\circ$
 $V_y < V_x$ slope $< 45^\circ$




$\phi = 30^\circ$

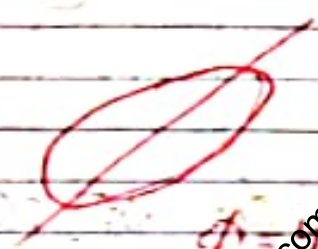major axis in 1st and 3rd quadrant clockwise rotation




$\phi = 45^\circ$

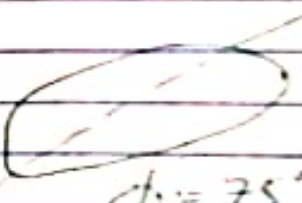

$\phi = 75^\circ$

broader

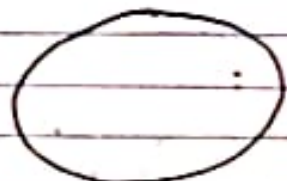


$\phi = 90^\circ$

clockwise rotation
 circle \rightarrow special case of ellipse.

For straight line $y_{\text{min}} = 0$
 For ellipses $0 < y_{\text{min}} < y_{\text{max}}$
 For circle $y_{\text{min}} = y_{\text{max}}$

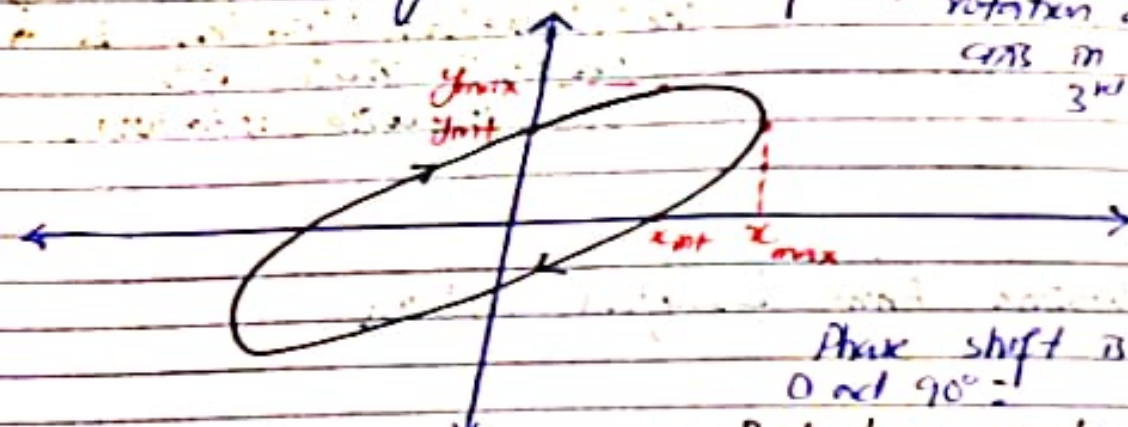Consider a generalized ellipse; with clock wise rotation and major axis in 1st and 3rd quadrant.



Phase shift is $\frac{1}{2}\pi$ or 90°


But how much,

$$\phi = \sin^{-1} \frac{x_{int}}{x_{max}}$$


$$\phi = \sin^{-1} \frac{y_{int}}{y_{max}}$$

Digital Storage Oscilloscope (DSO)

Stores a signal in digital form.

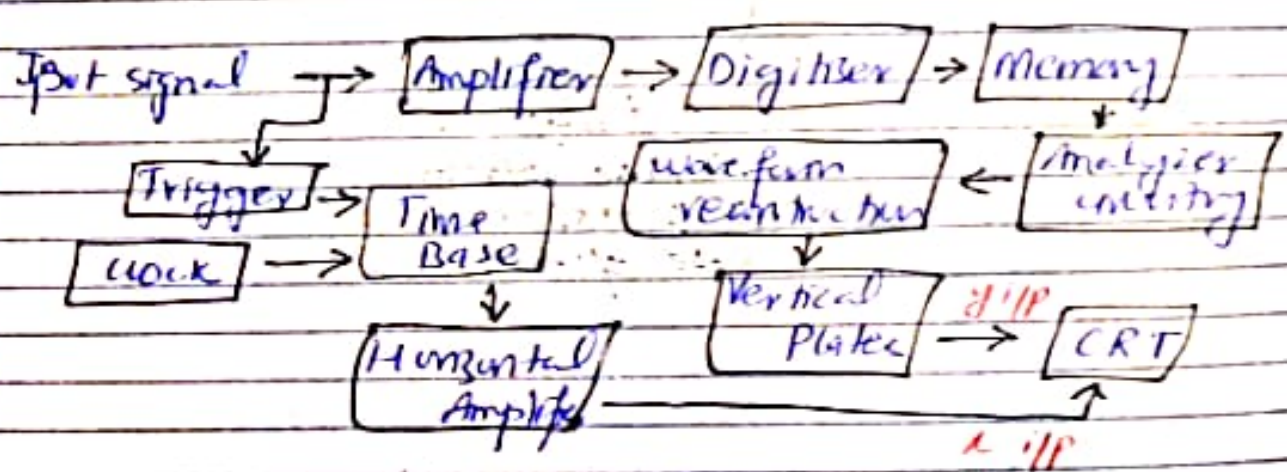

A more detailed block diagram is as;

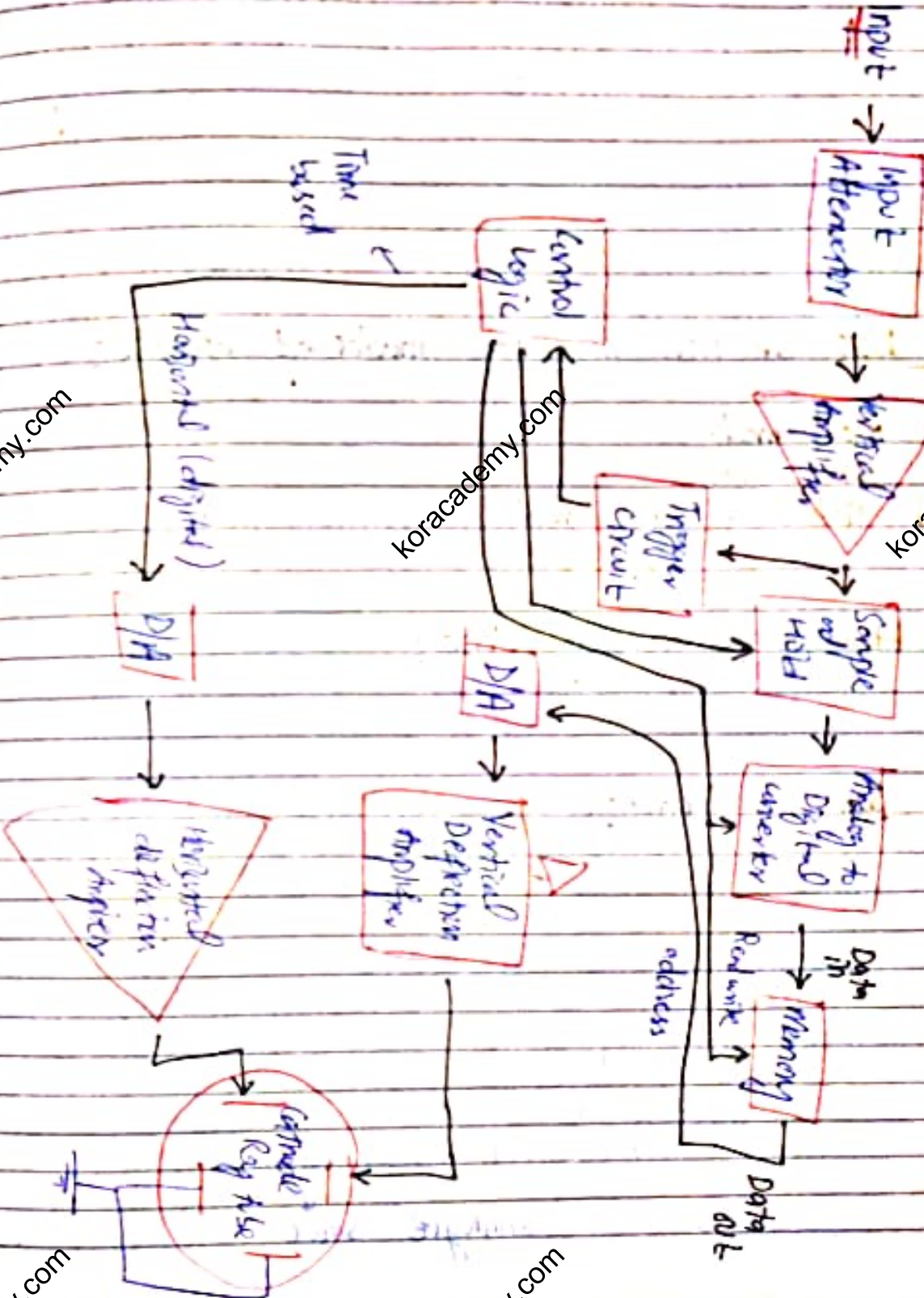

no distortion will be introduced

- The i/p signal is applied to the amplifier and attenuator section.
 - The attenuated signal is then applied to vertical amplifier.
 - Next it is given to Analogy to digital converter.
- Create a data set that is stored in the memory.
- Data set is processed by a microprocessor (control logic) and then sent to the display.

DSO can work in three modes of operation

- (i) Roll mode → very fast varying signals are displayed.
- (ii) Store mode → waveforms are stored in memory.
- (iii) Hold or save mode → some part of waveform is held and then stored in the memory.

How is digitising done?

Digitising occurs by taking a sample of the i/p waveform at periodic intervals.

Sampling Theorem Sampling rate must be at least twice as fast as highest frequency in the i/p signal.

If sampling theorem is not satisfied, an effect called Aliasing occurs → analog signal is not properly converted to digital.

If the condition is satisfied → Resolution of A/D converter is decreased. → to eliminate

We introduce an analogue store.

→ When i/p signals are stored in analogue store register, they can be read out at a much slower rate to the A/D converter and the results are stored in digital store

→ Allows operation at upto 100 mega samples per second.

→ The oscilloscope will not read a signal once it is being digitizing.

↳ disadvantage of analogue store.

Waveform Deconstruction

(i) Linear interpolation -


(ii) Sincoidal interpolation -

line

↳ dots are joined by a straight

Time
range

↳ dots are joined by a sine wave.

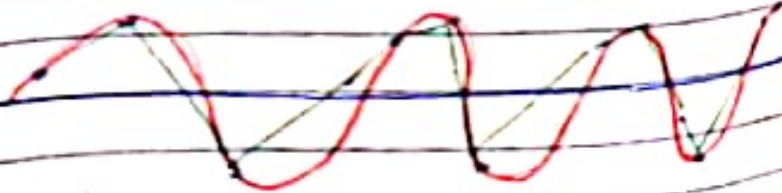

→ A DSO is an instrument which stores a digital copy of the waveform in the digital memory which it analyzes further using digital signal processing techniques.

→ It captures non repetitive signals and displays it on the screen until the device gets reset.

→ In DSO, the signals are received, stored and displayed on the screen.

The maximum frequency measured in the DSO depends on two things:

- (i) Sampling rate of the scope
- (ii) Nature of the converter

The traces in DSO are bright, highly defined, and displayed within seconds.

Advantage: Display visual as well as numerical values by analyzing the stored traces.

The display traces can be magnified and also we can change the brightness of the traces and minute detailing can be done.

→ on the screen the i/p voltage is displayed on the perpendicular axis versus time.

→ DSO can display 3D figure or multiple waveforms for comparison purposes.

→ DSO can capture and store the electronic events.

→ DSO is widely used b/c of its advanced features like storage, display, fast trace rates and remarkable bandwidth.

DSO

→ Shows the graphical representation of the signals for visual diagnosis and it helps to find out the unexpected voltage sources.

Digital Voltmeter

Only records the voltage fluctuations which further require diagnosis.