



Gates and Circuits

(Part A)

By

Nell Dale & John Lewis



Goals

- Identify the basic gates and describe the behavior of each
- Describe how gates are implemented using transistors
- Combine basic gates into circuits



Computers and Electricity

- A **gate** is a device that performs a basic operation on electrical signals
- Gates are combined into **circuits** to perform more complicated tasks



Computers and Electricity

- There are three different, but equally powerful, notational methods for describing the behavior of gates and circuits
 - Boolean expressions
 - logic diagrams
 - truth tables



Computers and Electricity

- **Boolean algebra:** expressions in this algebraic notation are an elegant and powerful way to demonstrate the activity of electrical circuits



Computers and Electricity

- **Logic diagram:** a graphical representation of a circuit
 - Each type of gate is represented by a specific graphical symbol
- **Truth table:** defines the function of a gate by listing all possible input combinations that the gate could encounter, and the corresponding output



NOT Gate

- A NOT gate accepts one input value and produces one output value

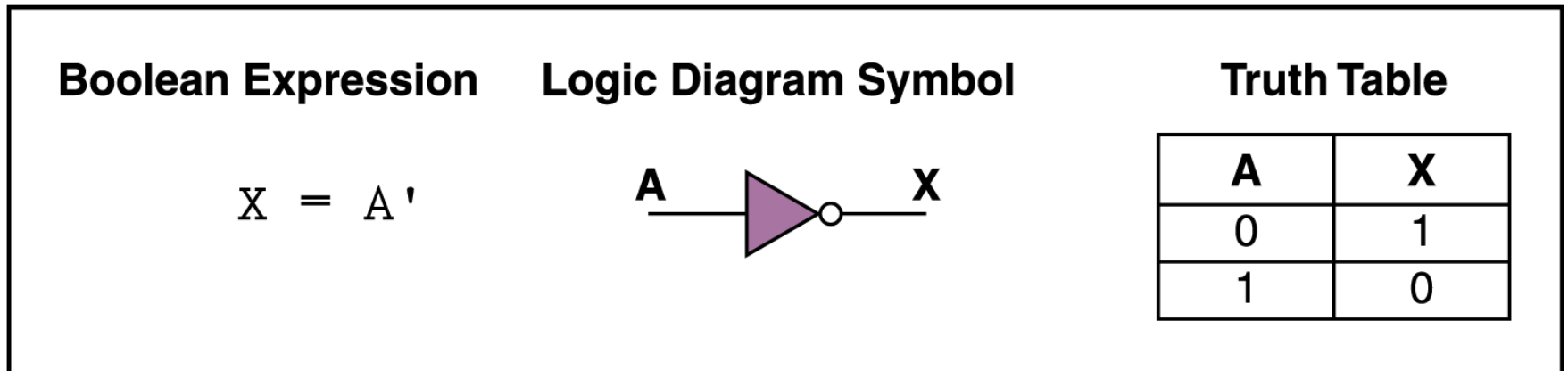


Figure 4.1 Various representations of a NOT gate




NOT Gate

- By definition, if the input value for a NOT gate is 0, the output value is 1, and if the input value is 1, the output is 0
- A NOT gate is sometimes referred to as an *inverter* because it inverts the input value

AND Gate

- An AND gate accepts two input signals
- If the two input values for an AND gate are both 1, the output is 1; otherwise, the output is 0

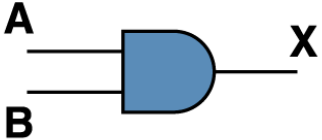
Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = A \cdot B$		<table border="1"><thead><tr><th>A</th><th>B</th><th>X</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></tbody></table>	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1
A	B	X															
0	0	0															
0	1	0															
1	0	0															
1	1	1															

Various representations of an AND gate



OR Gate

- If the two input values are both 0, the output value is 0; otherwise, the output is 1

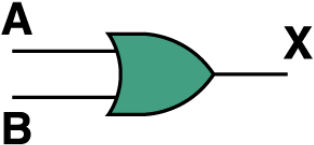Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = A + B$		<table border="1"><thead><tr><th>A</th><th>B</th><th>X</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></tbody></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	1
A	B	X															
0	0	0															
0	1	1															
1	0	1															
1	1	1															

Various representations of a OR gate



XOR Gate


- XOR, or *exclusive* OR, gate
 - An XOR gate produces 0 if its two inputs are the same, and a 1 otherwise
 - Note the difference between the XOR gate and the OR gate; they differ only in one input situation
 - When both input signals are 1, the OR gate produces a 1 and the XOR produces a 0

XOR Gate

Boolean Expression

$$X = A \oplus B$$

Logic Diagram Symbol

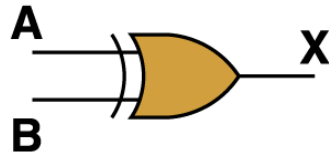

Truth Table


A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

Various representations of an XOR gate


NAND and NOR Gates

- The NAND and NOR gates are essentially the opposite of the AND and OR gates, respectively

Various representations of a NAND gate

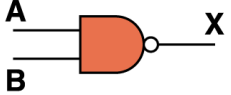Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = (A \cdot B)'$		<table border="1"><thead><tr><th>A</th><th>B</th><th>X</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></tbody></table>	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0
A	B	X															
0	0	1															
0	1	1															
1	0	1															
1	1	0															

Various representations of a NOR gate

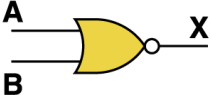Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = (A + B)'$		<table border="1"><thead><tr><th>A</th><th>B</th><th>X</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></tbody></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0
A	B	X															
0	0	1															
0	1	0															
1	0	0															
1	1	0															



Review of Gate Processing

- A NOT gate inverts its single input value
- An AND gate produces 1 if both input values are 1
- An OR gate produces 1 if one or the other or both input values are 1




Review of Gate Processing (cont.)

- An XOR gate produces 1 if one or the other (but not both) input values are 1
- A NAND gate produces the opposite results of an AND gate
- A NOR gate produces the opposite results of an OR gate

Gates with More Inputs

- Gates can be designed to accept three or more input values
- A three-input AND gate, for example, produces an output of 1 only if all input values are 1

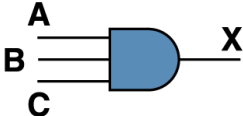Boolean Expression	Logic Diagram Symbol	Truth Table																																				
$X = A \cdot B \cdot C$		<table border="1"><thead><tr><th>A</th><th>B</th><th>C</th><th>X</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>1</td></tr></tbody></table>	A	B	C	X	0	0	0	0	0	0	1	0	0	1	0	0	0	1	1	0	1	0	0	0	1	0	1	0	1	1	0	0	1	1	1	1
A	B	C	X																																			
0	0	0	0																																			
0	0	1	0																																			
0	1	0	0																																			
0	1	1	0																																			
1	0	0	0																																			
1	0	1	0																																			
1	1	0	0																																			
1	1	1	1																																			




Constructing Gates

- A **transistor** is a device that acts, depending on the voltage level of an input signal, either as a wire that conducts electricity or as a resistor that blocks the flow of electricity
 - A transistor has no moving parts, yet acts like a switch
 - It is made of a **semiconductor** material, which is neither a particularly good conductor of electricity, such as copper, nor a particularly good insulator, such as rubber



Constructing Gates

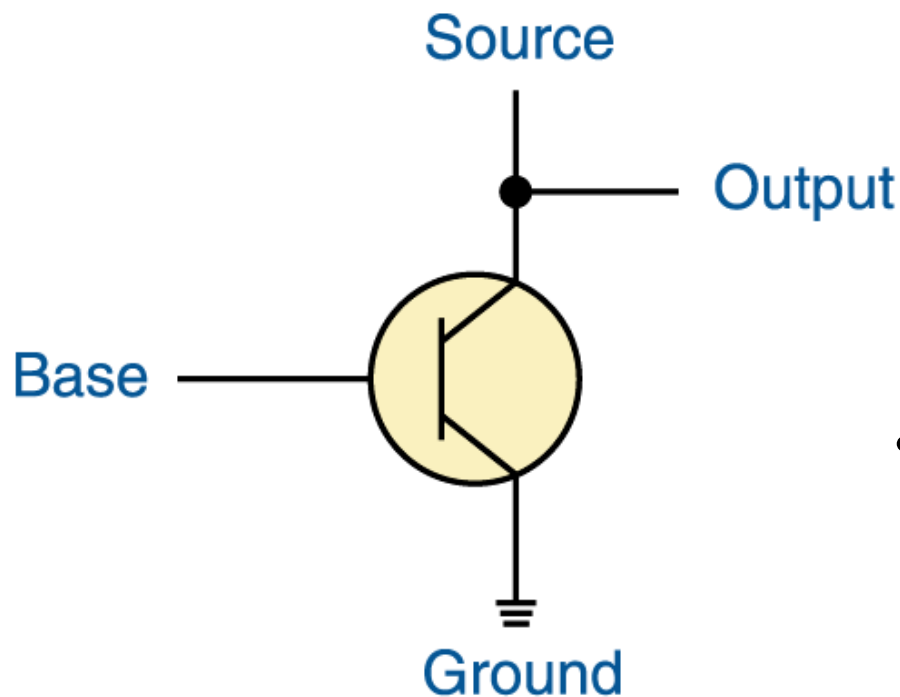


The connections of a transistor

- A transistor has three terminals
 - A source
 - A base
 - An emitter, typically connected to a ground wire
- If the electrical signal is grounded, it is allowed to flow through an alternative route to the ground (literally) where it can do no harm

Constructing Gates

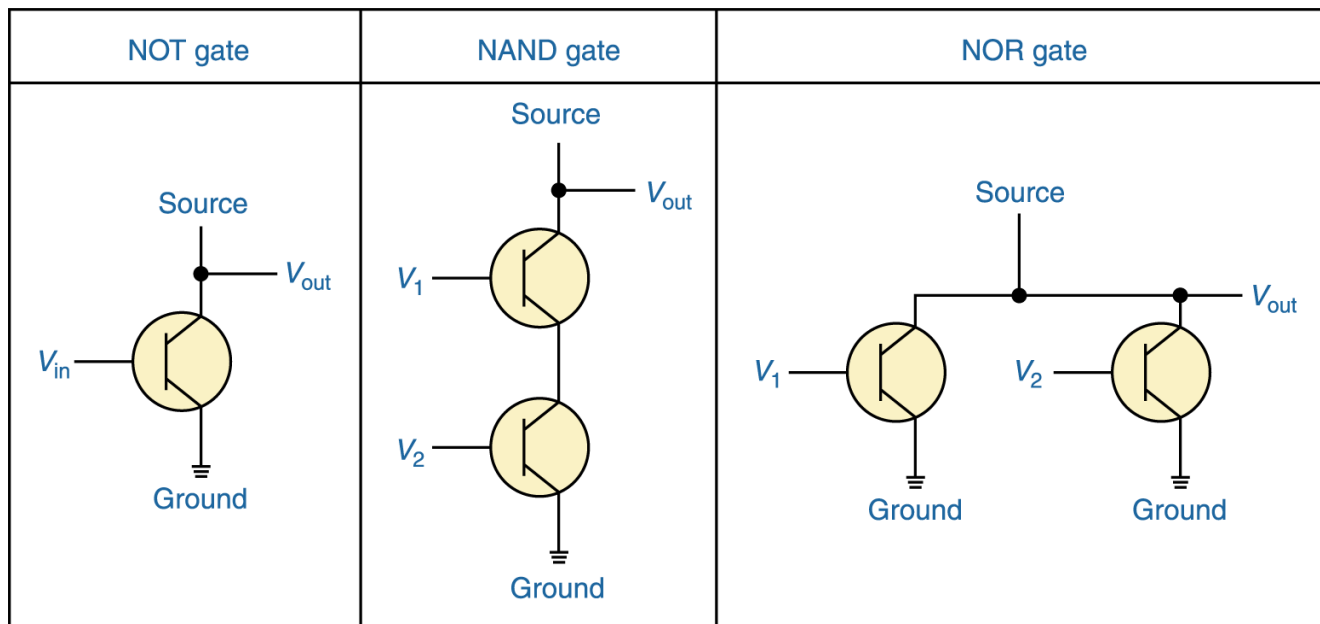- It turns out that, because the way a transistor works, the easiest gates to create are the NOT, NAND, and NOR gates



Constructing gates using transistors